

23S-EC ENGR-3-LEC-1 Homework 5

SANJIT SARDA

TOTAL POINTS

100 / 100

QUESTION 1

1 Q1 100 / 100

✓ - 0 pts *Correct*

- 10 pts Partially Incorrect (Thevenin Voltage / Norton Current)

- 25 pts Mostly Incorrect (Thevenin Voltage / Norton Current)

- 50 pts Incorrect (Thevenin Voltage / Norton Current)

- 10 pts Partially Incorrect (Thevenin Resistance)


- 25 pts Mostly Incorrect (Thevenin Resistance)

- 50 pts Incorrect (Thevenin Resistance)


EE3 Spring 2023

Homework Problem 5

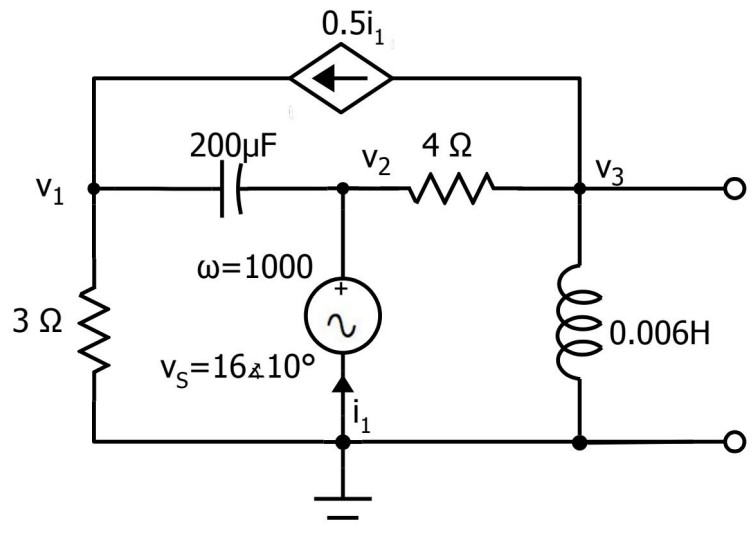
Find the Thévenin Equivalent of this circuit.



Open Circuit Analysis:

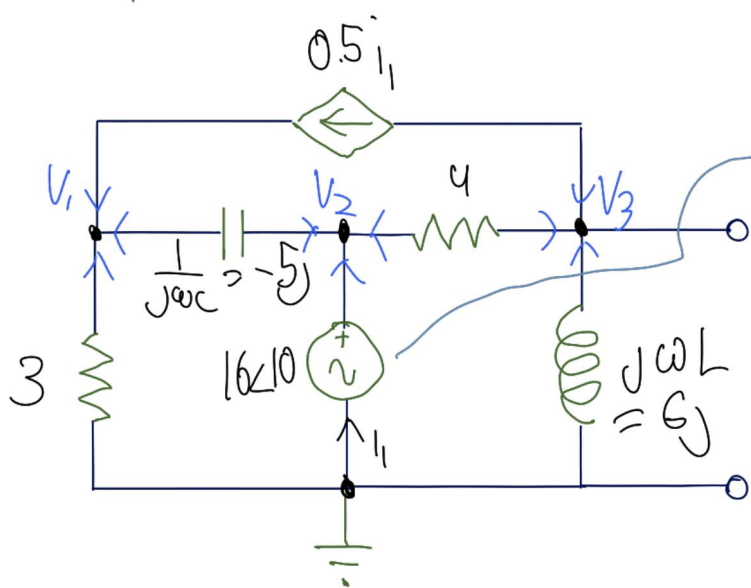
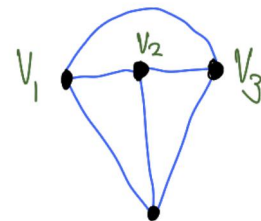
$$v_2 = 16 e^{j\frac{\pi}{18}}, \omega = 1000$$




$$\textcircled{a} V_1: \frac{V_1 - V_2}{5j} + \frac{-V_1}{3} + 0.5i_1 = 0$$

$$\textcircled{a} V_2: i_1 + \frac{V_2 - V_1}{5j} + \frac{V_3 - V_2}{4} = 0$$


$$\textcircled{a} V_3: -0.5i_1 + \frac{V_2 - V_3}{4} + \frac{-V_3}{6j} = 0$$

Solving for V_3

$$V_{Th} = 7.82 e^{0.616j} V$$

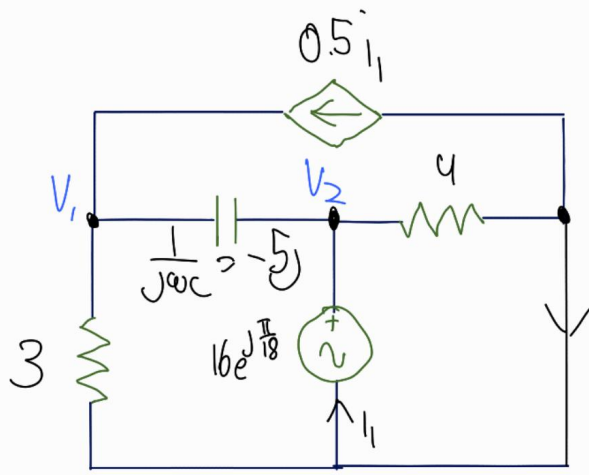
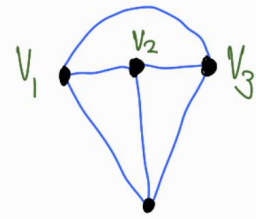
$$V_2 = 16 e^{j\frac{\pi}{18}}, \omega = 1000$$



$$\textcircled{a} V_1: \frac{V_1 - 16e^{j\frac{\pi}{18}}}{-5j} + \frac{-V_1}{3} + 0.5I_1 = 0$$

$$\textcircled{a} V_2: I_1 + \frac{16e^{j\frac{\pi}{18}} - V_1}{-5j} + \frac{-16e^{j\frac{\pi}{18}}}{4} = 0$$

$$\textcircled{a} V_3: I_n = 4e^{j\frac{\pi}{18}} - \frac{1}{2}$$

Solving for I_n ,

$$I_n = 1.6 e^{-0.13j}$$

$$Z_{th} = \frac{V_{th}}{I_n} = \frac{7.82 e^{0.616j}}{1.6 e^{-0.13j}} = 4.88 e^{0.73j}$$

Ther

$$4.88 e^{0.73j} = 3.43 + 3.47j$$

Eq:

$$16e^{j\frac{\pi}{18}}$$



$$= 16 e^{j\frac{\pi}{18}}$$



$$3.43 \Omega \quad 3.47 \text{ mH}$$



cell

1 Q1 100 / 100

✓ - 0 pts Correct

- 10 pts Partially Incorrect (Thevenin Voltage / Norton Current)
- 25 pts Mostly Incorrect (Thevenin Voltage / Norton Current)
- 50 pts Incorrect (Thevenin Voltage / Norton Current)
- 10 pts Partially Incorrect (Thevenin Resistance)
- 25 pts Mostly Incorrect (Thevenin Resistance)
- 50 pts Incorrect (Thevenin Resistance)