

# 23S-EC ENGR-3-LEC-1 Homework 3

SANJIT SARDA

TOTAL POINTS

**100 / 100**

QUESTION 1

1 Q1a: V4 reference 50 / 50

✓ - 0 pts *Correct*

- 50 pts Incorrect/Blank

- 10 pts Partially incorrect

- 25 pts Mostly incorrect

QUESTION 2

2 Q1b: V2 reference 50 / 50

✓ - 0 pts *Correct*

- 10 pts Partially incorrect

- 25 pts Mostly incorrect


- 50 pts Incorrect/Blank

# EE3 Spring 2023

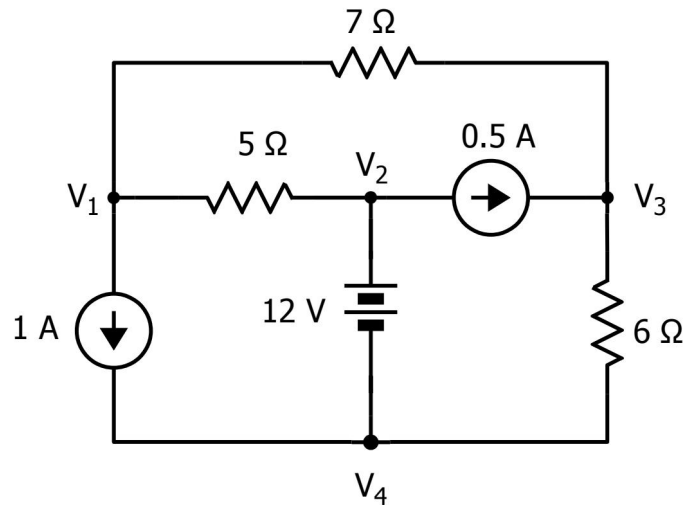
## Homework Problem 3

Find the current magnitude and direction through the battery, two ways:

- with  $V_4$  as the reference node
- with  $V_2$  as the reference node



$V_4$  as Datum

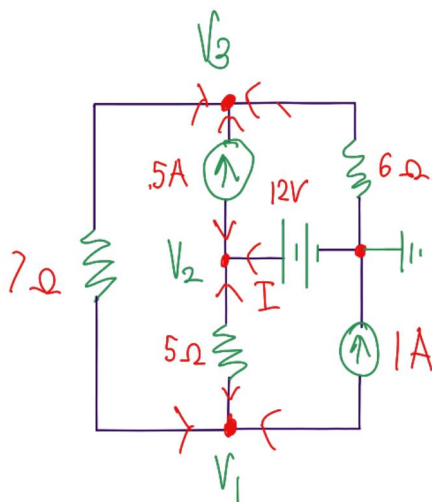

$$V_2 = 12$$

@  $V_2$ :

$$\frac{V_1 - 12}{5} + -\frac{1}{2} + I = 0$$

$$@ V_1: -1 + \frac{12 - V_1}{5} + \frac{V_3 - V_1}{7} = 0$$

$$@ V_3: \frac{1}{2} + \frac{V_1 - V_3}{7} - \frac{V_3}{6} = 0$$

$$I = \frac{31}{8} = 1.72 \text{ A Flowing out of Battery}$$

$$\frac{2V_1}{10} - \frac{24}{10} - \frac{5}{10} + \frac{10I}{10} = 0$$

$$-\frac{35}{35} + \frac{84}{35} - \frac{7V_1}{35} + \frac{5V_3}{35} - \frac{5V_1}{35} = 0$$

$$\frac{21}{42} + \frac{6V_1 - 6V_3}{42} - \frac{7V_3}{42} = 0$$

$$V_1 = \frac{53}{9}, V_3 = \frac{13}{3}$$


$$2V_1 - 29 + 10I = 0$$

$$49 - 12V_1 + 5V_3 = 0$$

$$21 + 6V_1 - 13V_3 = 0$$

Solving

Using  $V_2$  as Datum

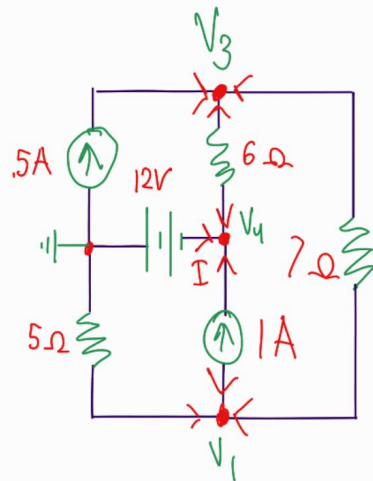

$$V_4 = -12$$

@  $V_1$ :

$$\frac{-V_1}{5} + -1 + \frac{V_2 - V_1}{7} = 0$$

@  $V_4$ :  $I + \frac{V_3 + 12}{6} + 1 = 0$

@  $V_3$ :  $\frac{1}{2} + \frac{V_1 - V_2}{7} - \frac{12 + V_3}{6} = 0$

$$\frac{-2V_1 - 35}{35} + \frac{5V_2 - 5V_4}{35}$$

$$\frac{6I + V_3 + 12}{6} + \frac{6}{6} = 0$$

$$\frac{21}{42} + \frac{6V_1 - 6V_3}{42} - \frac{84 - 7V_3}{42} = 0$$

$$-12V_1 - 35 + 5V_3 = 0$$

$$6I + V_3 + 18 = 0$$

$$-63 + 6V_1 - 13V_3 = 0$$


Solving

$$V_1 = -\frac{55}{9}, V_3 = -\frac{23}{3}$$

$$I = -1.72 \text{ A}$$

Flowing  
Into Battery

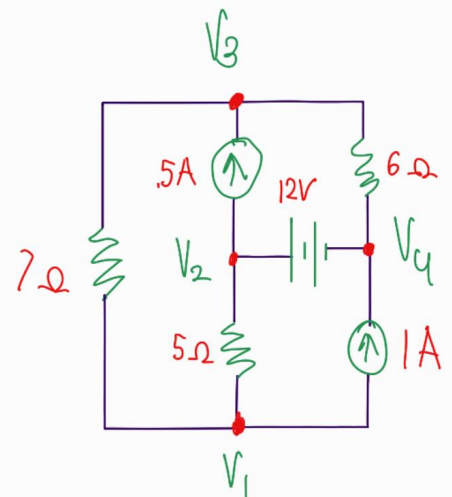$= 1.72 \text{ A}$  Flowing Into  
Battery.



1 Q1a: V4 reference 50 / 50

✓ - **0 pts** *Correct*

- **50 pts** Incorrect/Blank

- **10 pts** Partially incorrect

- **25 pts** Mostly incorrect

2 Q1b: V2 reference 50 / 50

✓ - 0 pts Correct

- 10 pts Partially incorrect

- 25 pts Mostly incorrect

- 50 pts Incorrect/Blank