

23S-EC ENGR-3-LEC-1 Homework 7

SANJIT SARDA

TOTAL POINTS

100 / 100

QUESTION 1

1 Q1 (Power Calculation) 80 / 80

✓ - 0 pts *Correct*

- 5 pts Numerical error
- 15 pts Incorrect Approach
- 80 pts Blank
- 0 pts [Click here to replace this description.](#)

QUESTION 2




2 Q2 (Absorbing or Delivering) 20 / 20

✓ - 0 pts *Correct*

- 10 pts Incorrect but reasonable attempt/explanation
- 20 pts Blank/Missing

EE3 Spring 2023 Homework Problem 6

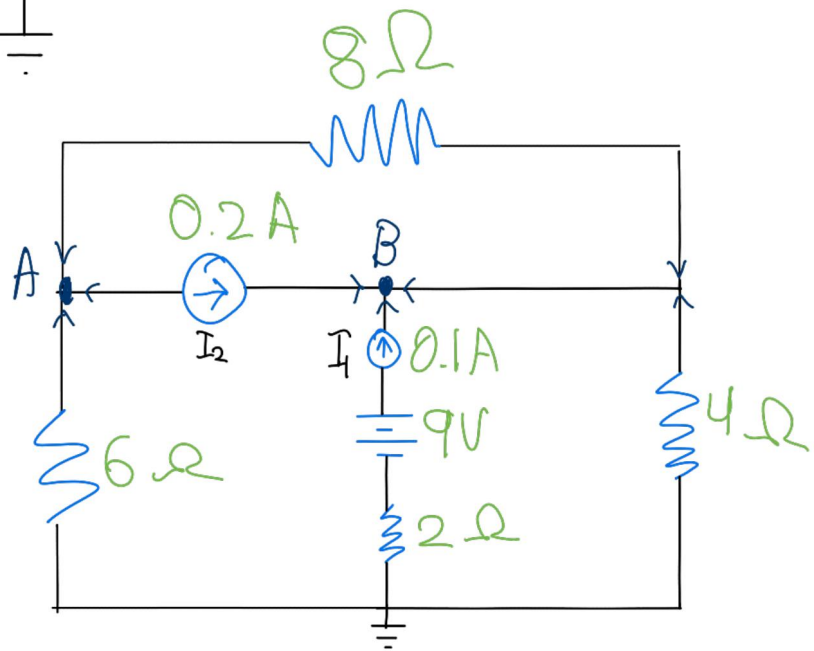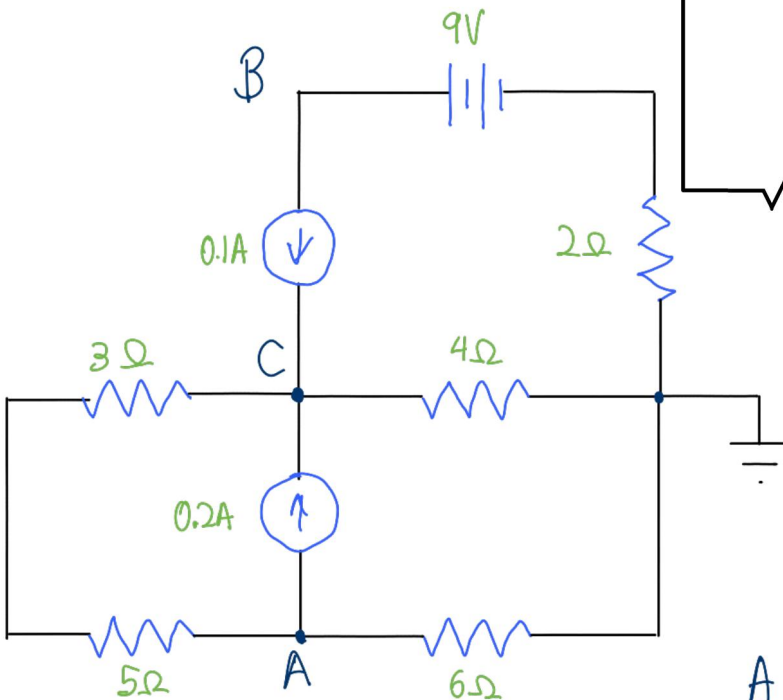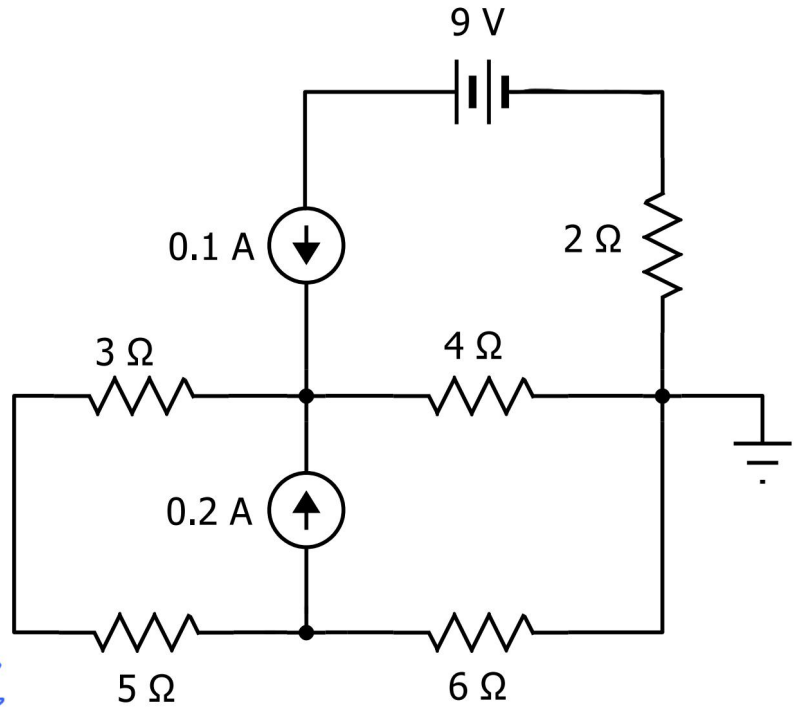Find the power provided or absorbed by the 0.1 A current source. Is it providing or absorbing?



$$\textcircled{a} A: \frac{-V_A}{6} - 0.2 + \frac{V_B - V_A}{8} = 0$$

$$\textcircled{b} B: 0.2 + \frac{V_A - V_B}{8} - \frac{V_B}{4} + 0.1 = 0$$

Solving $V_A = -\frac{2}{5} V$, $V_B = \frac{2}{3} V$

$$I_1 = 0.1 A, V_{I_1} = V_B - 9V + (0.1)(2) = 8.133V$$

$$\therefore \text{Power} = VI = 0.1 \cdot 8.133 = -0.8133W$$

Since power is negative, power is being absorbed.

1 Q1 (Power Calculation) 80 / 80

✓ - **0 pts** Correct

- **5 pts** Numerical error




- **15 pts** Incorrect Approach

- **80 pts** Blank

- **0 pts** [Click here to replace this description.](#)

EE3 Spring 2023 Homework Problem 6

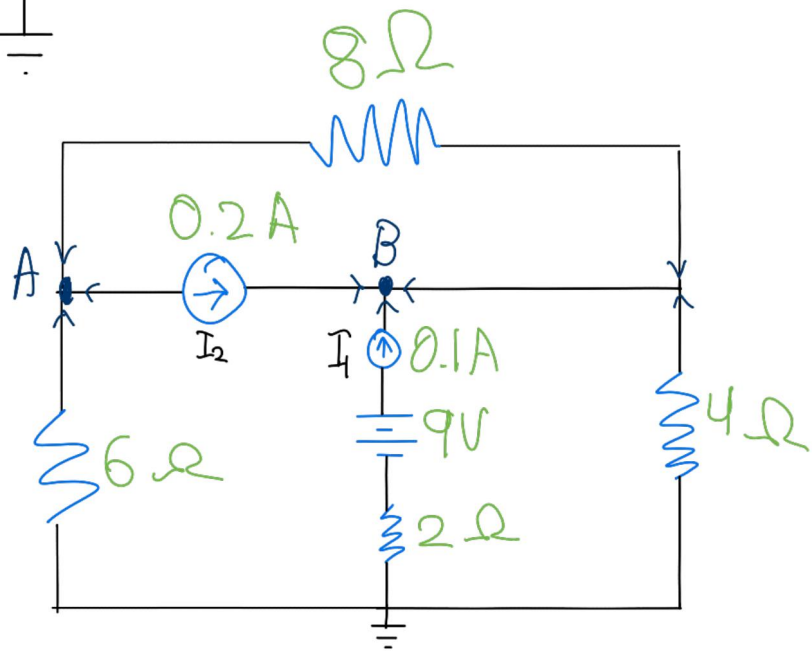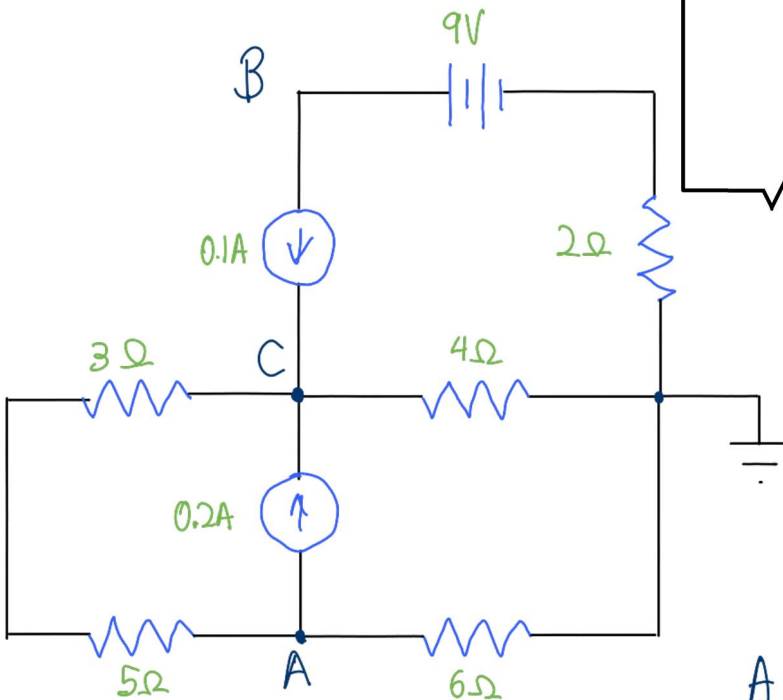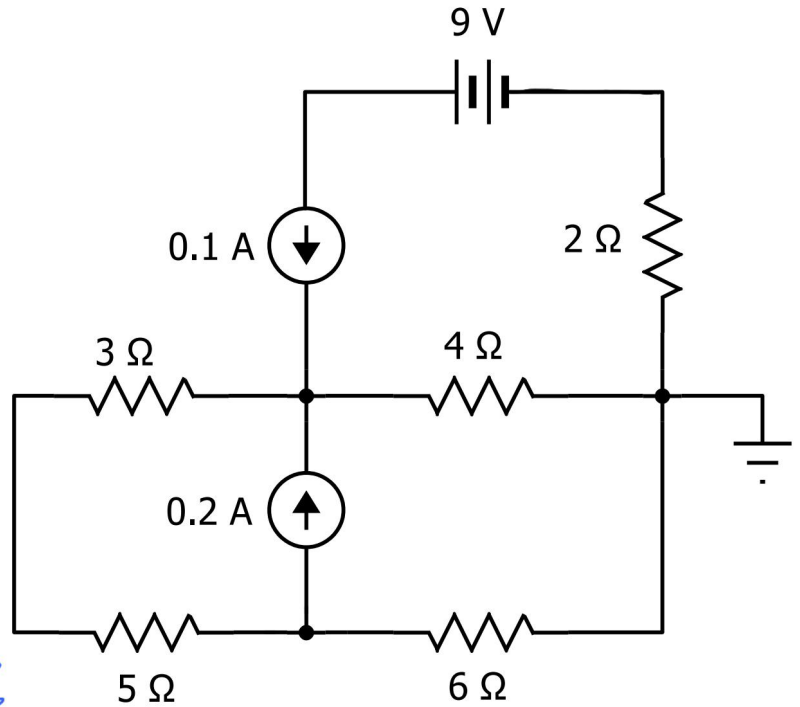Find the power provided or absorbed by the 0.1 A current source. Is it providing or absorbing?



$$\textcircled{a} A: \frac{-V_A}{6} - 0.2 + \frac{V_B - V_A}{8} = 0$$

$$\textcircled{b} B: 0.2 + \frac{V_A - V_B}{8} - \frac{V_B}{4} + 0.1 = 0$$

Solving $V_A = -\frac{2}{5} V$, $V_B = \frac{2}{3} V$

$$I_1 = 0.1 A, V_{I_1} = V_B - 9V + (0.1)(2) = 8.133V$$

$$\therefore \text{Power} = VI = 0.1 \cdot 8.133 = -0.8133W$$

Since power is negative, power is being absorbed.

2 Q2 (Absorbing or Delivering) 20 / 20

✓ - **0 pts** *Correct*

- **10 pts** Incorrect but reasonable attempt/explanation

- **20 pts** Blank/Missing

