

23W-EC ENGR-10-LEC-1 Hw #3

SANJIT SARDA

TOTAL POINTS

97.5 / 100

QUESTION 1

Problem 1 15 pts

1.1 a 4 / 4

✓ - 0 pts Correct

- 1 pts Wrong Answer

1.2 b 7 / 7

✓ - 0 pts Correct

- 1 pts V_a is wrong

- 1 pts V_b is wrong

- 1 pts τ is wrong, which should be $2L/3R$

- 1 pts one or more of these is wrong

calculated. $k_1 = -v/3$, $k_2 = v/3$, $k_3 = -v/2$, $k_4 = 0$

1.3 c 4 / 4

✓ - 0 pts Correct

- 1 pts $V_a(t)$ is wrong

- 1 pts $V_b(t)$ is wrong

QUESTION 2

Problem 2 20 pts

2.1 a 5 / 5

✓ - 0 pts Correct

- 2 pts wrong answer

- 3 pts did not calculate the final answer

2.2 b 5 / 5

✓ - 0 pts Correct

- 2 pts wrong sign

- 3 pts answer should be -2

2.3 c 5 / 5

✓ - 0 pts Correct

- 3 pts answer should be 0.

2.4 d 5 / 5

✓ - 0 pts Correct

- 2 pts wrong sign

- 3 pts answer should be $-2e^{-4t}$

- 5 pts did not answer

QUESTION 3

Problem 3 20 pts

3.1 a 8 / 8

✓ - 0 pts Correct

- 2 pts did not use series calculation formula

- 8 pts did not answer this question

3.2 b 4 / 4

✓ - 0 pts Correct

- 2 pts I_b answer should be 0.075A

- 2 pts $I_a = 0$

- 4 pts did not answer this question

3.3 C 6 / 8

- 0 pts Correct

✓ - 2 pts wrong sign

- 4 pts answer should be -150 V/s

- 8 pts did not answer

QUESTION 4

Problem 4 20 pts

4.1 a 2 / 2

✓ - 0 pts Correct

- 2 pts wrong answer

4.2 b 2 / 2

✓ - 0 pts Correct

- 1 pts answer should be $1.125 \times 10^9 \text{ ns}$

- 2 pts no answer

4.3 C 6 / 6

✓ - 0 pts Correct

- 1 pts $V_1(0^+) = 1600 \text{ V}$

- 1 pts $i(0^+) = 7.11 \text{ A}$

- 1 pts $V_2(0^+) = -533.33 \text{ V}$

- 1 pts $i(\infty) = 0$

- 1 pts $V_1(\infty) = 0$

- 1 pts $V_2(\infty) = 0$

- 6 pts No answer

4.4 d 3 / 3

✓ - 0 pts Correct

- 1 pts answer should be $V_1(t) = 1600e^{-8t/9}$

- 1 pts answer should be $V_2(t) = -533.33e^{-8t/9}$

- 3 pts No answer

4.5 e 2 / 2

✓ - 0 pts Correct

- 1 pts V1

- 1 pts V2

- 2 pts No answer

4.6 f 2 / 2

✓ - 0 pts Correct

- 2 pts No answer

4.7 g 3 / 3

✓ - 0 pts Correct

- 1 pts partially incorrect

- 3 pts did not answer

QUESTION 5

Problem 5 15 pts

5.1 a 5 / 5

✓ - 0 pts Correct

- 1 pts partially incorrect

- 5 pts did not answer

5.2 b 10 / 10

✓ - 0 pts Correct

- 2 pts $2 \times 10^8 \text{ (A/s)}$

- 2 pts $-8 \times 10^{17} \text{ (A/s}^2\text{)}$

- 10 pts did not answer

QUESTION 6

Problem 6 10 pts

6.1 a 4 / 4

✓ - 0 pts Correct

- 1 pts $V_R(t) = -2V$

- 1 pts $i_1(t=0^+) = 6\text{mA}$

- 4 pts did not answer this question

6.2 b 5.5 / 6

- 0 pts Correct

✓ - 0.5 pts wrong sign

- 1 pts answer should be $-6 \times 10^6 \text{ (V/s)}$

- 6 pts No answer

①

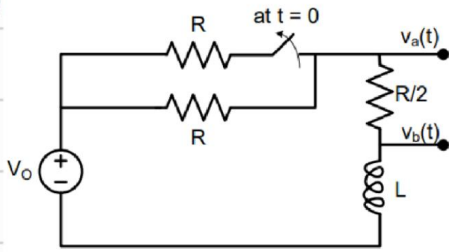
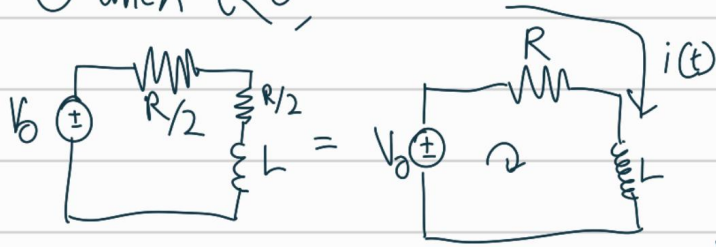


Figure 1.


② When $t < 0$,

@ Steady State, $i(0^-) = V_0/R = \frac{V_0}{R}$

@ $i(0^+)$, there is no jump in current, $i(0^+) = \frac{V_0}{R}$

$$i(t) = \frac{1}{L} \int V_B(t) dt \quad \therefore Li = \int V_B dt$$

$$\therefore Li' = V_B$$

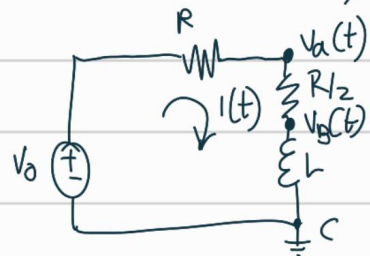③ When $t \geq 0$,

$$KVL \rightarrow i \cdot R + iR/2 + L \frac{di}{dt} = V_0$$

$$V_A = V_B(t) + \frac{i(t) \cdot R}{2} = -\frac{V_0}{2} e^{-\frac{R}{L}t} + \frac{V_0}{3} + \frac{V_0}{6} e^{-\frac{R}{L}t}$$


$$\therefore L \frac{di}{dt} + \frac{3}{2} iR = V_0$$

$$\therefore V_B = Li' = \left(-\frac{V_0}{3} e^{-\frac{3R}{2L}t} + \frac{V_0}{3} \right) = -\frac{V_0}{2} e^{-\frac{3R}{2L}t}$$

$$\therefore i'(t) + \frac{3R}{2L} i = \frac{V_0}{L}$$

$$\text{Solving for } i(t), i(t) = C e^{-\frac{3R}{2L}t} + \frac{2V_0}{3R} = \frac{2V_0}{3R} + \frac{1V_0}{3R} e^{-\frac{3R}{2L}t}$$
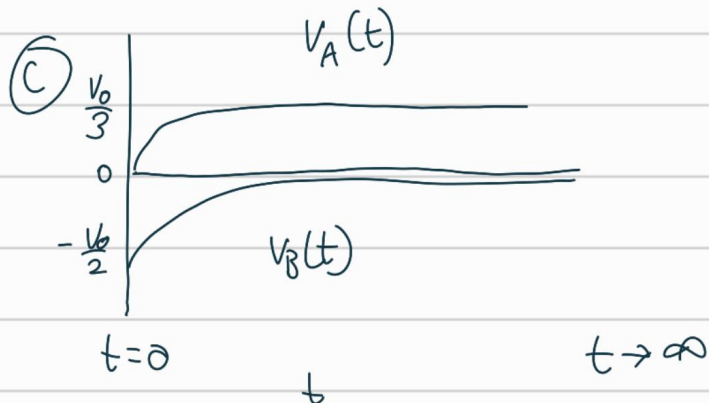
$$\text{from @, } i(0) = \frac{V_0}{R} \therefore \frac{V_0}{R} = C \cdot 1 + \frac{2V_0}{3R} \therefore C = \frac{3-2}{3} \cdot \frac{V_0}{R} = \frac{1}{3} \frac{V_0}{R}$$



1.1 a 4 / 4

✓ - 0 pts Correct

- 1 pts Wrong Answer

①

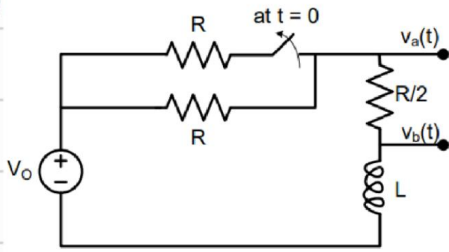
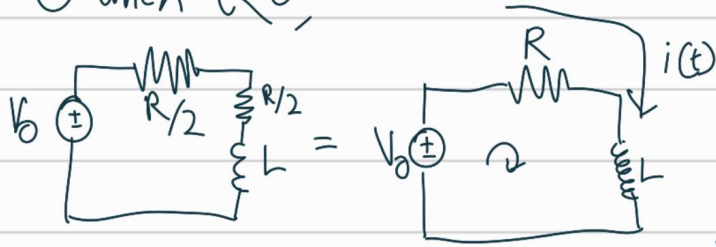
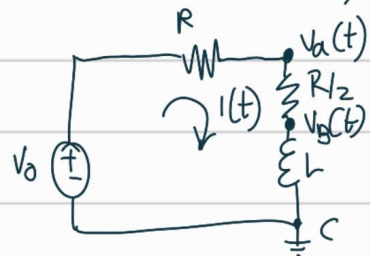


Figure 1.

② When $t < 0$,① Steady State, $i(0^-) = V_0/R = \frac{V_0}{R}$ ② $i(0^+)$, there is no jump in current, $i(0^+) = \frac{V_0}{R}$

$$i(t) = \frac{1}{L} \int V_B(t) dt \quad \therefore Li = \int V_B dt$$

$$\therefore Li' = V_B$$

③ When $t \geq 0$,

$$\text{KVL} \rightarrow i \cdot R + iR/2 + L \frac{di}{dt} = V_0$$

$$V_A = V_B(t) + \frac{i(t) \cdot R}{2} = -\frac{V_0}{2} e^{-\frac{R}{L}t} + \frac{V_0}{3} + \frac{V_0}{6} e^{-\frac{R}{L}t}$$


$$\therefore L \frac{di}{dt} + \frac{3}{2} iR = V_0$$

$$\therefore V_B = Li' = \left(-\frac{V_0}{3} e^{-\frac{3R}{2L}t} + \frac{V_0}{3} \right) = -\frac{V_0}{2} e^{-\frac{3R}{2L}t}$$

$$\therefore i'(t) + \frac{3R}{2L} i = \frac{V_0}{L}$$

$$\text{Solving for } i(t), i(t) = C e^{-\frac{3R}{2L}t} + \frac{2V_0}{3R} = \frac{2V_0}{3R} + \frac{1V_0}{3R} e^{-\frac{3R}{2L}t}$$
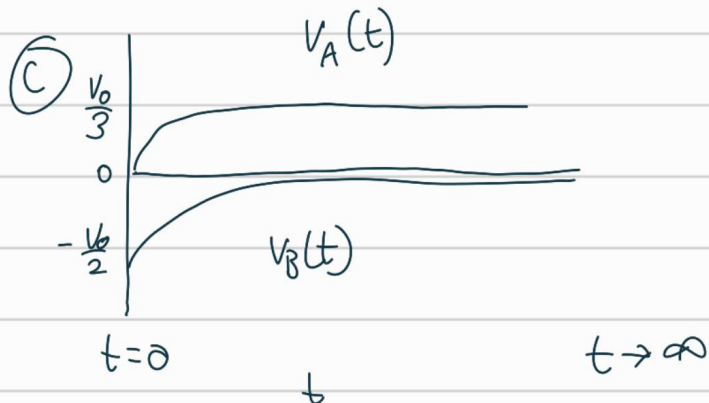
$$\text{from } i(0) = \frac{V_0}{R} \therefore \frac{V_0}{R} = C \cdot 1 + \frac{2V_0}{3R} \therefore C = \frac{3-2}{3} \cdot \frac{V_0}{R} = \frac{1}{3} \frac{V_0}{R}$$



1.2 b 7 / 7

✓ - 0 pts Correct

- 1 pts V_a is wrong

- 1 pts V_b is wrong

- 1 pts τ is wrong, which should be $2L/3R$

- 1 pts one or more of these is wrong calculated. $k_1 = -v/3$, $k_2 = v/3$, $k_3 = -v/2$, $k_4 = 0$

①

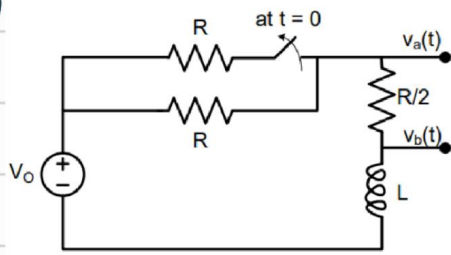
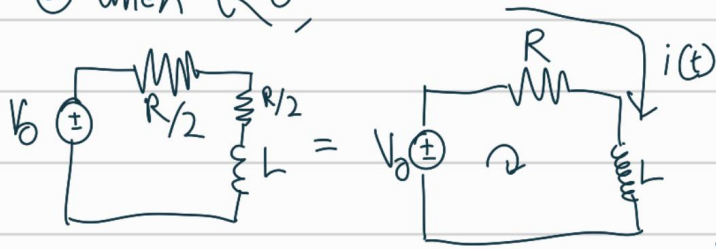
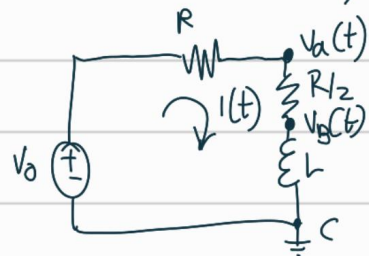


Figure 1.

② When $t < 0$,③ Steady State, $i(0^-) = V_0/R = \frac{V_0}{R}$ ④ $i(0^+)$, there is no jump in current, $i(0^+) = \frac{V_0}{R}$

$$i(t) = \frac{1}{L} \int V_B(t) dt \quad \therefore Li = \int V_B dt$$

$$\therefore Li' = V_B$$

⑤ When $t \geq 0$,

$$KVL \rightarrow i \cdot R + iR/2 + L \frac{di}{dt} = V_0$$

$$V_A = V_B(t) + \frac{i(t) \cdot R}{2} = -\frac{V_0}{2} e^{-\frac{R}{L}t} + \frac{V_0}{3} + \frac{V_0}{6} e^{-\frac{R}{L}t}$$


$$\therefore L \frac{di}{dt} + \frac{3}{2} iR = V_0$$

$$\therefore V_B = Li' = \left(-\frac{V_0}{3} e^{-\frac{3R}{2L}t} + \frac{V_0}{3} \right) = -\frac{V_0}{2} e^{-\frac{3R}{2L}t}$$

$$\therefore i'(t) + \frac{3R}{2L} i = \frac{V_0}{L}$$

$$\text{Solving for } i(t), i(t) = C e^{-\frac{3R}{2L}t} + \frac{2V_0}{3R} = \frac{2V_0}{3R} + \frac{1V_0}{3R} e^{-\frac{3R}{2L}t}$$
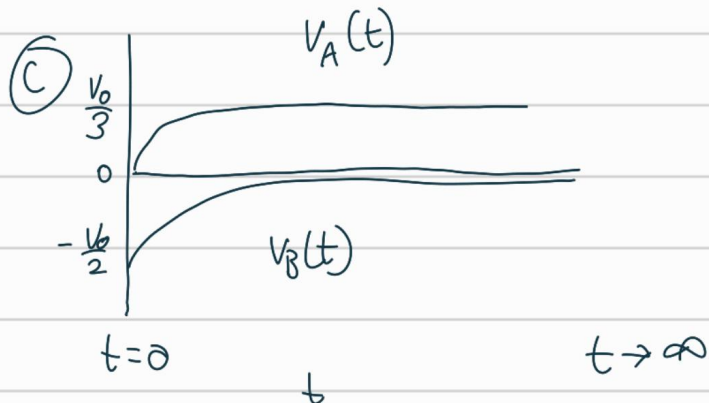
$$\text{from } i(0) = \frac{V_0}{R} \therefore \frac{V_0}{R} = C \cdot 1 + \frac{2V_0}{3R} \therefore C = \frac{3-2}{3} \cdot \frac{V_0}{R} = \frac{1}{3} \frac{V_0}{R}$$






1.3 C 4 / 4

✓ - 0 pts Correct

- 1 pts $V_a(t)$ is wrong

- 1 pts $V_b(t)$ is wrong

②

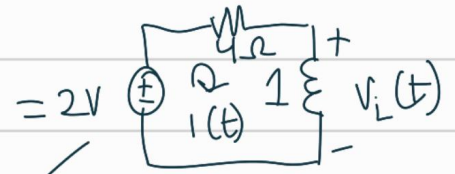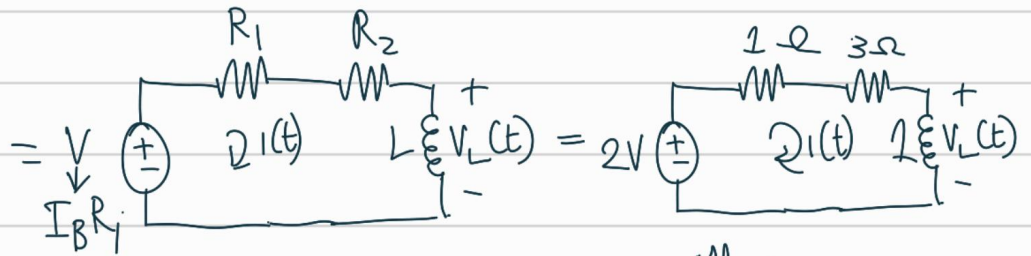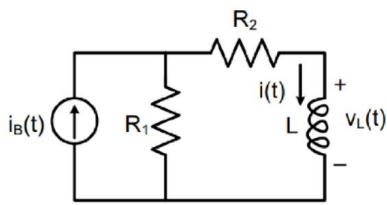

a) $\tau = \frac{L}{R} = \frac{1}{4} = \frac{1}{4} s$

KVL

$i(t) = \frac{1}{L} \int -v_L(t) dt$

b) $v_L(0+)$

$= -2e^0 = -2V$

c) $v_L(\infty) = -2e^\infty = 0V$

d) $v_L(t) = -2e^{-4t}$

$2 = 4 \cdot i(t) + 1 \cdot i'(t)$

solving for $i(t) = Ce^{-4t} + \frac{1}{2}$

$i(0) = 1 \therefore 1 = C \cdot 1 + \frac{1}{2}$

$\therefore C = \frac{1}{2}$

$\therefore i(t) = \frac{1}{2}(e^{-4t} + 1)$

$-v_L(t) = L \cdot i'(t) = -2e^{-4t}$

$\therefore v_L(t) = -2e^{-4t}$




2.1 a 5 / 5

✓ - 0 pts Correct

- 2 pts wrong answer

- 3 pts did not calculate the final answer

②

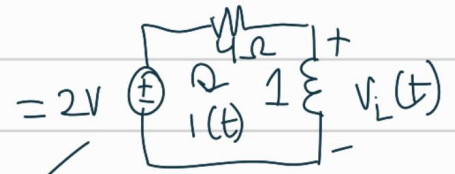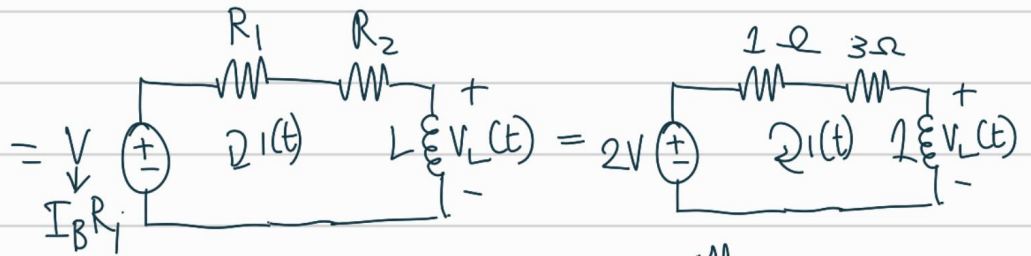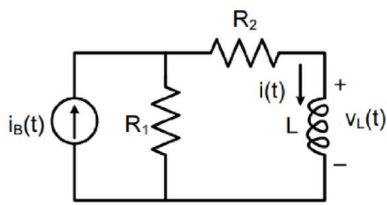

a) $\tau = \frac{L}{R} = \frac{1}{4} = \frac{1}{4} s$

KVL

$i(t) = \frac{1}{L} \int -v_L(t) dt$

b) $v_L(0+)$

$= -2e^0 = -2V$

c) $v_L(\infty) = -2e^\infty = 0V$

d) $v_L(t) = -2e^{-4t}$

$2 = 4 \cdot i(t) + 1 \cdot i'(t)$

solving for $i(t) = Ce^{-4t} + \frac{1}{2}$

$i(0) = 1 \therefore 1 = C \cdot 1 + \frac{1}{2}$

$\therefore C = \frac{1}{2}$

$\therefore i(t) = \frac{1}{2}(e^{-4t} + 1)$

$-v_L(t) = L \cdot i'(t) = -2e^{-4t}$

$\therefore v_L(t) = -2e^{-4t}$




2.2 b 5 / 5

✓ - 0 pts Correct

- 2 pts wrong sign

- 3 pts answer should be -2

②

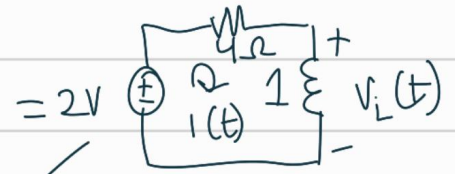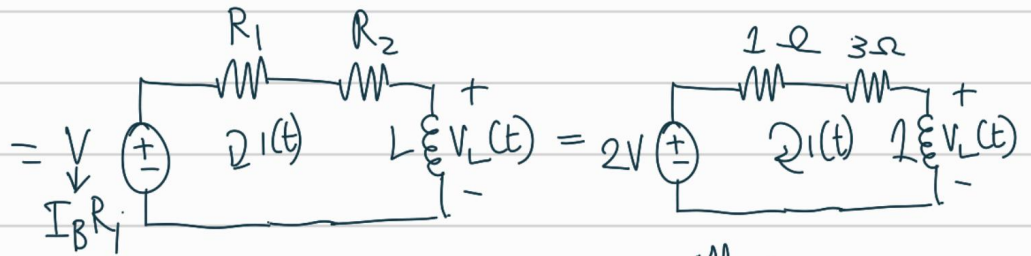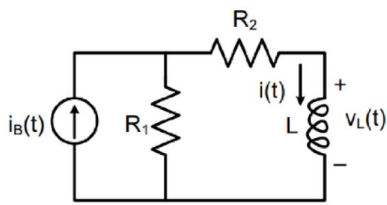

a) $\tau = \frac{L}{R} = \frac{1}{4} = \frac{1}{4} s$

KVL

$i(t) = \frac{1}{L} \int -v_L(t) dt$

b) $v_L(0+)$

$= -2e^0 = -2V$

c) $v_L(\infty) = -2e^\infty = 0V$

d) $v_L(t) = -2e^{-4t}$

$2 = 4 \cdot i(t) + 1 \cdot i'(t)$

solving for $i(t) = Ce^{-4t} + \frac{1}{2}$

$i(0) = 1 \therefore 1 = C \cdot 1 + \frac{1}{2}$

$\therefore C = \frac{1}{2}$

$\therefore i(t) = \frac{1}{2}(e^{-4t} + 1)$

$-v_L(t) = L \cdot i'(t) = -2e^{-4t}$




$\therefore v_L(t) = -2e^{-4t}$

2.3 C 5 / 5

✓ - 0 pts Correct

- 3 pts answer should be 0.

②

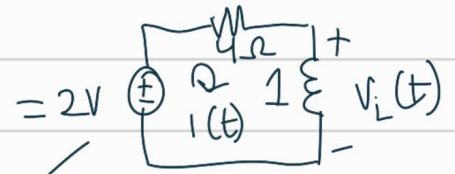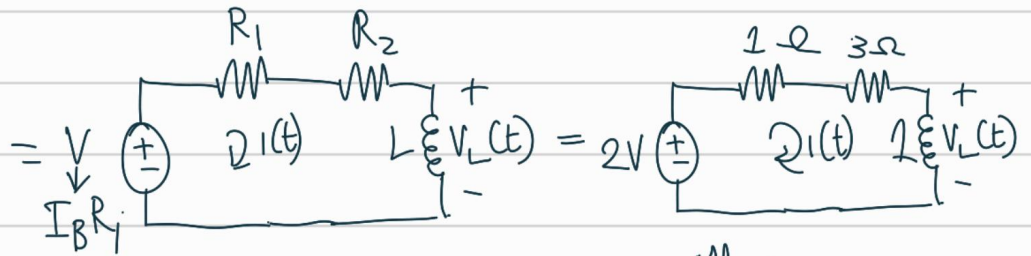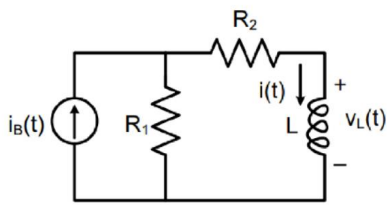

a) $\tau = \frac{L}{R} = \frac{1}{4} = \frac{1}{4} s$

KVL

$$i(t) = \frac{1}{L} \int -v_L(t) dt$$

b) $v_L(0+)$

$$= -2e^0 = -2V$$

c) $v_L(\infty) = -2e^\infty = 0V$

d) $v_L(t) = -2e^{-4t}$

$$2 = 4 \cdot i(t) + 1 \cdot i'(t)$$

solving for $i(t) = Ce^{-4t} + \frac{1}{2}$

$$i(0) = 1 \therefore 1 = C \cdot 1 + \frac{1}{2}$$

$$\therefore C = \frac{1}{2}$$

$$\therefore i(t) = \frac{1}{2}(e^{-4t} + 1)$$

$$-v_L(t) = L \cdot i'(t) = -2e^{-4t}$$

$$\therefore v_L(t) = -2e^{-4t}$$

2.4 d 5 / 5



✓ - 0 pts Correct

- 2 pts wrong sign

- 3 pts answer should be $-2e^{-4t}$

- 5 pts did not answer

③

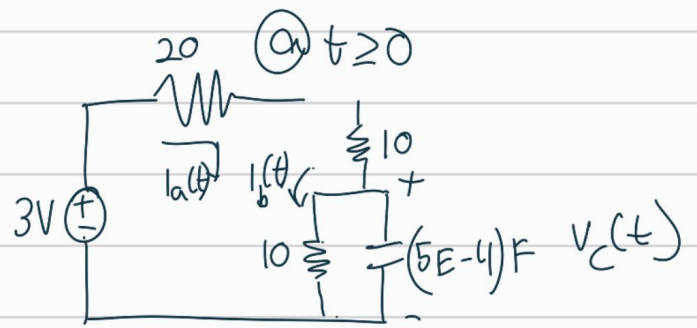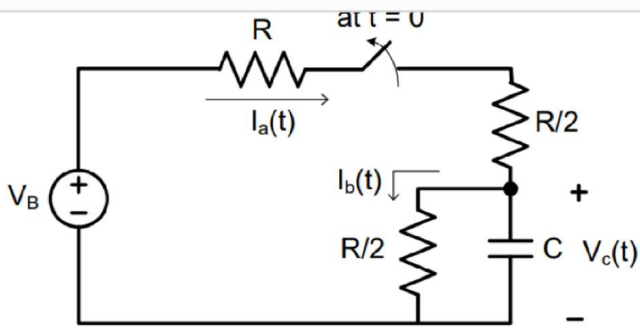

① Given $V_c(0^-) = \frac{3}{4} V$

$V_c(0^+) = V_c(0^-) = \frac{3}{4} V$
since there is a resistor
no impulse.

@ $t \geq 0$, $V_c(t) = i_B(t) \cdot 10$

$i_B(t) = C V_c'$

$\therefore V_c(t) = -10 C V_c'$

Solving for V_c , $V_c = C e^{-\frac{t}{10 \cdot (5E-4)}}$

$V_c(0) = \frac{3}{4} \therefore \frac{3}{4} = C e^0 = C$

$\therefore V_c(t) = \frac{3}{4} e^{-\frac{t}{10(5E-4)}}$

$i_B(t) = (5E-4) \cdot \frac{3}{4} \cdot \frac{1}{10(5E-4)} e^{-\frac{t}{10(5E-4)}}$

$= \frac{3}{40} e^{-\frac{t}{5E-4}}$

② $I_a(0^+) = 0$ since there is no closed loop

$I_b(0^+) = \frac{3}{40} A$

③ $\frac{dV_c(t)}{dt} = \frac{1}{C} \cdot C \frac{dV_c(t)}{dt} = \frac{1}{C} \cdot i_B(t) = \frac{3 e^{-\frac{t}{5E-4}}}{40 \cdot (5E-4)} \Big|_{t=0} = \frac{3}{40(5E-4)} = 150 V s^{-1}$



3.1 a 8 / 8

✓ - 0 pts Correct

- 2 pts did not use series calculation formula

- 8 pts did not answer this question

③

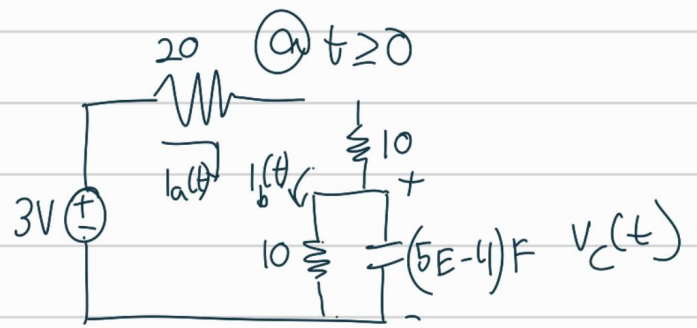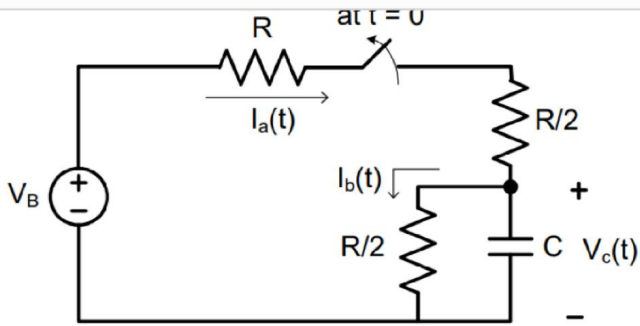

① Given $V_c(0^-) = \frac{3}{4} V$

$V_c(0^+) = V_c(0^-) = \frac{3}{4} V$
since there is a resistor
no impulse.

@ $t \geq 0$, $V_c(t) = i_b(t) \cdot 10$

$i_b(t) = C V_c'$

$\therefore V_c(t) = -10 C V_c'$

Solving for V_c , $V_c = C e^{-\frac{t}{10 \cdot (5E-4)}}$

$V_c(0) = \frac{3}{4} \therefore \frac{3}{4} = C e^0 = C$

$\therefore V_c(t) = \frac{3}{4} e^{-\frac{t}{10(5E-4)}}$

$i_b(t) = (5E-4) \cdot \frac{3}{4} \cdot \frac{1}{10(5E-4)} e^{-\frac{t}{10(5E-4)}}$

$= \frac{3}{40} e^{-\frac{t}{5E-4}}$

② $I_a(0^+) = 0$ since there is no closed loop

$I_b(0^+) = \frac{3}{40} A$

③ $\frac{dV_c(t)}{dt} = \frac{1}{C} \cdot C \frac{dV_c(t)}{dt} = \frac{1}{C} \cdot i_b(t) = \frac{3e^{-\frac{t}{5E-4}}}{40 \cdot (5E-4)} \Big|_{t=0} = \frac{3}{40(5E-4)} = 150 V s^{-1}$

3.2 b 4 / 4



✓ - 0 pts Correct

- 2 pts Ib answer should be 0.075A

- 2 pts Ia = 0

- 4 pts did not answer this question

③

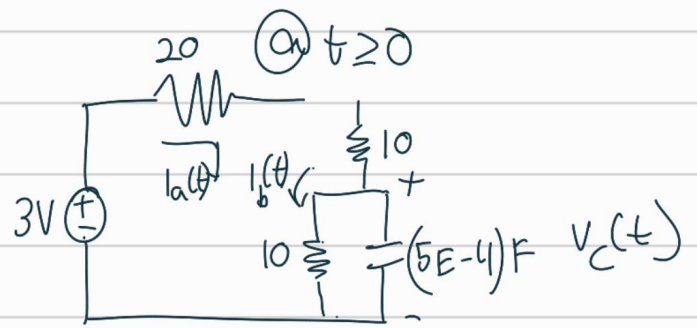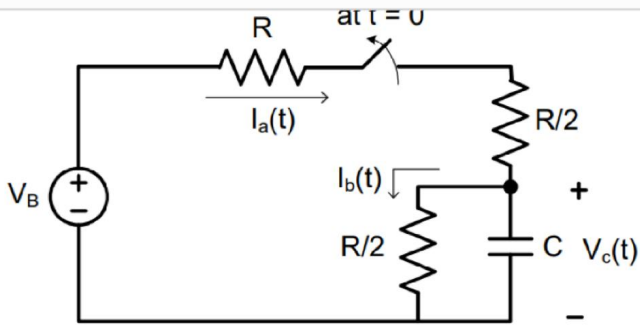

① Given $V_c(0^-) = \frac{3}{4} V$

$V_c(0^+) = V_c(0^-) = \frac{3}{4} V$
since there is a resistor
no impulse.

@ $t \geq 0$, $V_c(t) = i_b(t) \cdot 10$

$i_b(t) = C V_c'$

$\therefore V_c(t) = -10 C V_c'$

Solving for V_c , $V_c = C e^{-\frac{t}{10 \cdot (5E-4)}}$

$V_c(0) = \frac{3}{4} \therefore \frac{3}{4} = C e^0 = C$

$\therefore V_c(t) = \frac{3}{4} e^{-\frac{t}{10(5E-4)}}$

$i_b(t) = (5E-4) \cdot \frac{3}{4} \cdot \frac{1}{10(5E-4)} e^{-\frac{t}{10(5E-4)}}$

$= \frac{3}{40} e^{-\frac{t}{5E-4}}$

② $I_a(0^+) = 0$ since there is no closed loop

$I_b(0^+) = \frac{3}{40} A$

③ $\frac{dV_c(t)}{dt} = \frac{1}{C} \cdot C \frac{dV_c(t)}{dt} = \frac{1}{C} \cdot i_b(t) = \frac{3e^{-\frac{t}{5E-4}}}{40 \cdot (5E-4)} \Big|_{t=0} = \frac{3}{40(5E-4)} = 150 V s^{-1}$

3.3 C 6 / 8


- 0 pts Correct

✓ - 2 pts *wrong sign*

- 4 pts answer should be $-150 \text{ } \$/\text{s}$

- 8 pts did not answer

③

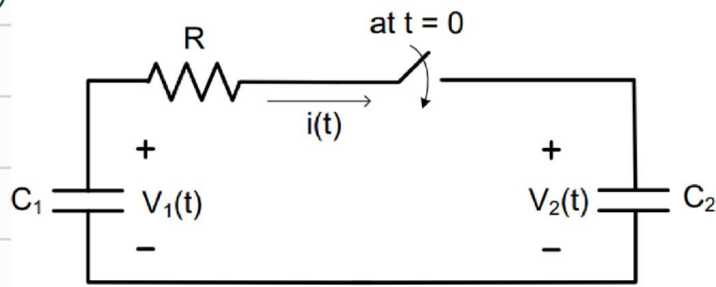

$$Q = CV$$

$$\begin{aligned} @ t = 0^- \\ Q_1 \& Q_2 \\ \therefore Q_1 = C_1 V_1(0^-) \\ \& Q_2 = C_2 V_2(0^-) \end{aligned}$$

$$\text{KVL @ } t \geq 0, \quad -V_1 + iR + V_2 = 0$$

$$\therefore V_1 = V_2 + iR$$

$$\therefore \frac{1}{C_1} \int i dt + \frac{1}{C_2} \int i dt = iR$$

$$\therefore \frac{1}{C_1} \cdot i + \frac{1}{C_2} \cdot i = i'R$$



$$a) \quad \therefore 0 = \frac{800}{3} + 3i'$$

$$b) \quad \therefore \text{Time constant} = R \cdot \frac{C_1 C_2}{C_1 + C_2} = 1.125 \text{ E } 9 \text{ ns}$$

$$\begin{aligned} c) \quad V_1(0^+) = V_1(0^-) = \frac{8}{5 \text{ E } -3} = 1600 \text{ V} \quad V_1(\infty) = 0 \\ V_2(0^+) = V_2(0^-) = \frac{-8}{15 \text{ E } -3} = -\frac{1600}{3} \text{ V} \quad V_2(\infty) = 0 \\ i(0^+) = \frac{V_1 - V_2}{R} = 7.11 \text{ A} \quad i(\infty) = 0 \end{aligned}$$

⑨ Like an Imple.
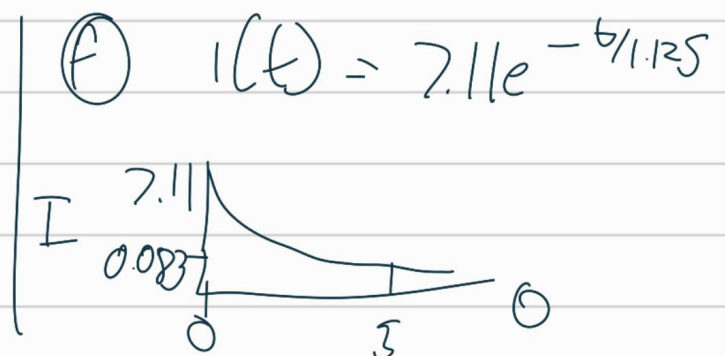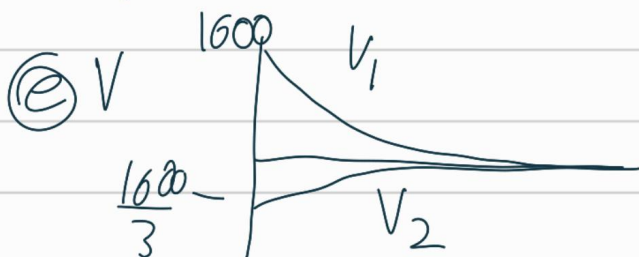
$$d) \quad V_1(t) = 1600 e^{-t/1.125} \quad V_2(t) = -\frac{1600}{3} e^{-t/1.125}$$




4.1 a 2 / 2

✓ - 0 pts Correct

- 2 pts wrong answer

③

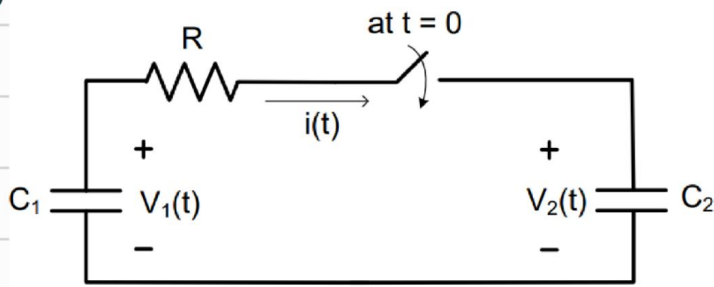

$$Q = CV$$

@ $t = 0^-$,
 $Q_1 \& Q_2$
 $\therefore Q_1 = C_1 V_1(0^-)$
 $\& Q_2 = C_2 V_2(0^-)$

KVL @ $t \geq 0$, $-V_1 + iR + V_2 = 0$
 $\therefore V_1 = V_2 + iR$

$$\therefore \frac{1}{C_1} \int i dt + \frac{1}{C_2} \int i dt = iR$$

$$\therefore \frac{1}{C_1} \cdot i + \frac{1}{C_2} \cdot i = i'R$$



a) $\therefore 0 = \frac{800}{3} + 3i'$

b) \therefore Time constant $= R \cdot \frac{C_1 C_2}{C_1 + C_2} = 1.125 \text{ E } 9 \text{ ns}$

c) $V_1(0^+) = V_1(0^-) = \frac{8}{5 \text{ E } -3} = 1600 \text{ V}$ $V_1(\infty) = 0$
 $V_2(0^+) = V_2(0^-) = \frac{-8}{15 \text{ E } -3} = -\frac{1600}{3} \text{ V}$ $V_2(\infty) = 0$
 $i(0^+) = \frac{V_1 - V_2}{R} = 7.11 \text{ A}$ $i(\infty) = 0$

⑨ Like an Imple.

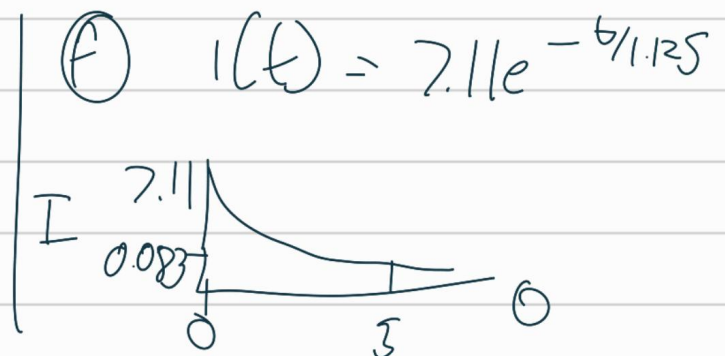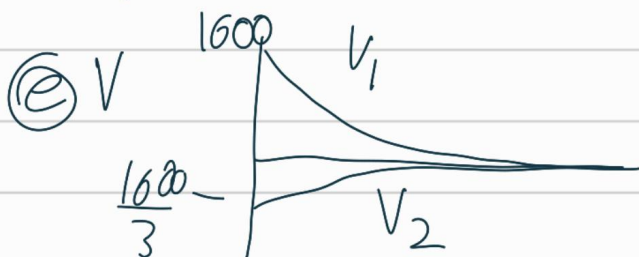d) $V_1(t) = 1600 e^{-t/1.125}$ $V_2(t) = -\frac{1600}{3} e^{-t/1.125}$




4.2 b 2 / 2

✓ - 0 pts Correct

- 1 pts answer should be $\$1.125 \times 10^9$ ns

- 2 pts no answer

③

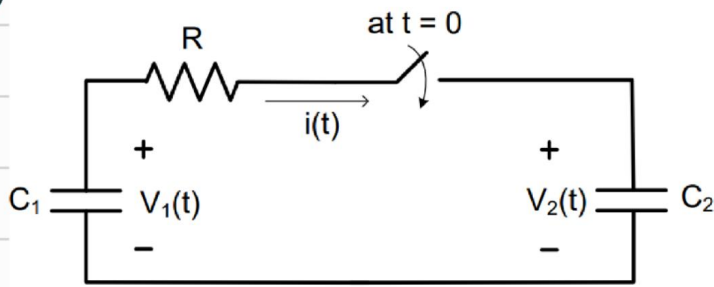

$$Q = CV$$

@ $t = 0^-$,
 $Q_1 \& Q_2$
 $\therefore Q_1 = C_1 V_1(0^-)$
 $\& Q_2 = C_2 V_2(0^-)$

KVL @ $t \geq 0$, $-V_1 + iR + V_2 = 0$
 $\therefore V_1 = V_2 + iR$

$$\therefore \frac{1}{C_1} \int i dt + \frac{1}{C_2} \int i dt = iR$$

$$\therefore \frac{1}{C_1} \cdot i + \frac{1}{C_2} \cdot i = i'R$$



a) $\therefore 0 = \frac{800}{3} + 3i'$

b) \therefore Time constant $= R \cdot \frac{C_1 C_2}{C_1 + C_2} = 1.125 \text{ E } 9 \text{ ns}$

c) $V_1(0^+) = V_1(0^-) = \frac{8}{5 \text{ E } -3} = 1600 \text{ V}$ $V_1(\infty) = 0$
 $V_2(0^+) = V_2(0^-) = \frac{-8}{15 \text{ E } -3} = -\frac{1600}{3} \text{ V}$ $V_2(\infty) = 0$
 $i(0^+) = \frac{V_1 - V_2}{R} = 7.11 \text{ A}$ $i(\infty) = 0$

⑨ Like an Imple.

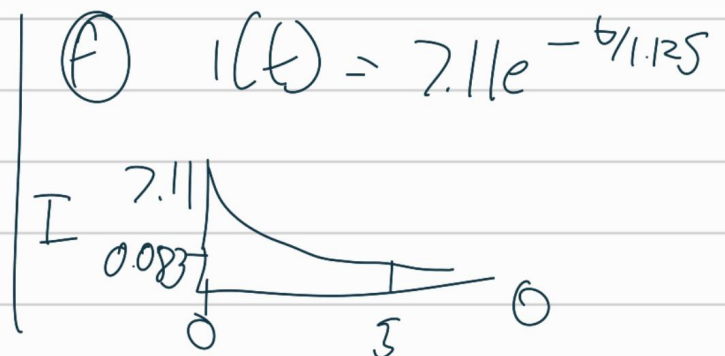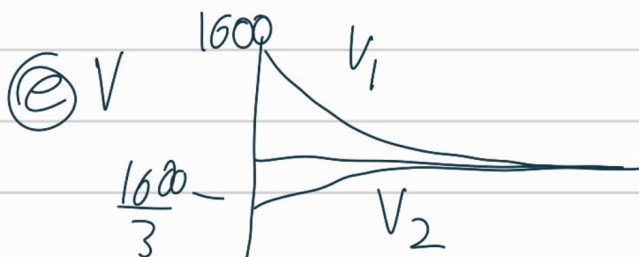d) $V_1(t) = 1600 e^{-t/1.125}$ $V_2(t) = -\frac{1600}{3} e^{-t/1.125}$



4.3 C 6 / 6

✓ - 0 pts Correct

- 1 pts $V_1(0^+) = 1600\text{V}$

- 1 pts $i(0^+) = 7.11\text{A}$

- 1 pts $V_2(0^+) = -533.33\text{V}$


- 1 pts $i(\infty) = 0$

- 1 pts $V_1(\infty) = 0$

- 1 pts $V_2(\infty) = 0$

- 6 pts No answer

③

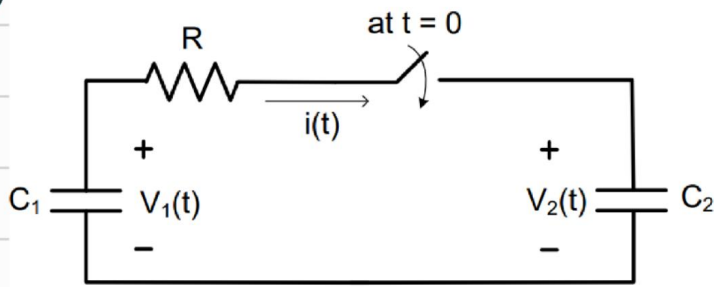

$$Q = CV$$

@ $t = 0^-$,
 $Q_1 \& Q_2$
 $\therefore Q_1 = C_1 V_1(0^-)$
 $\& Q_2 = C_2 V_2(0^-)$

KVL @ $t \geq 0$, $-V_1 + iR + V_2 = 0$
 $\therefore V_1 = V_2 + iR$

$$\therefore \frac{1}{C_1} \int i dt + \frac{1}{C_2} \int i dt = iR$$

$$\therefore \frac{1}{C_1} \cdot i + \frac{1}{C_2} \cdot i = i'R$$



a) $\therefore 0 = \frac{800}{3} + 3i'$

b) \therefore Time constant $= R \cdot \frac{C_1 C_2}{C_1 + C_2} = 1.125 \text{ E } 9 \text{ ns}$

c) $V_1(0^+) = V_1(0^-) = \frac{8}{5 \text{ E } -3} = 1600 \text{ V}$ $V_1(\infty) = 0$
 $V_2(0^+) = V_2(0^-) = \frac{-8}{15 \text{ E } -3} = -\frac{1600}{3} \text{ V}$ $V_2(\infty) = 0$
 $i(0^+) = \frac{V_1 - V_2}{R} = 7.11 \text{ A}$ $i(\infty) = 0$

⑨ Like an Imple.

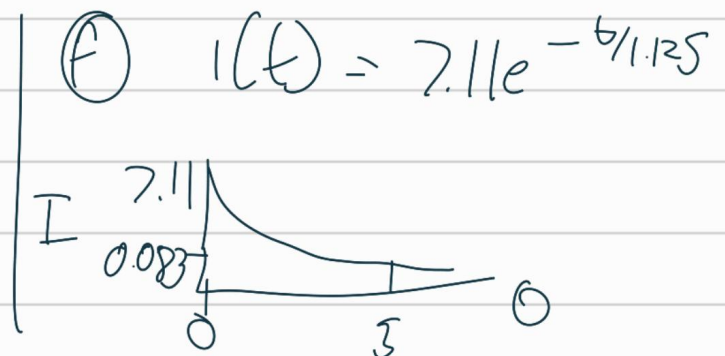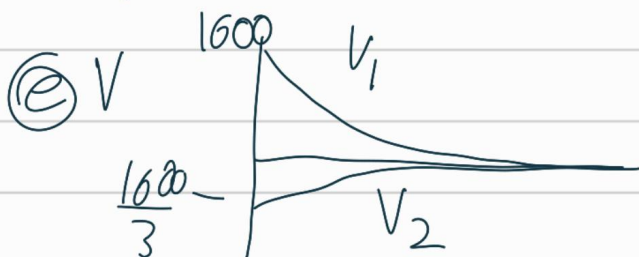d) $V_1(t) = 1600 e^{-t/1.125}$ $V_2(t) = -\frac{1600}{3} e^{-t/1.125}$



4.4 d 3 / 3


✓ - 0 pts Correct

- 1 pts answer should be $V_1(t) = 1600e^{-8t/9}$

- 1 pts answer should be $V_2(t) = -533.33e^{-8t/9}$

- 3 pts No answer

③

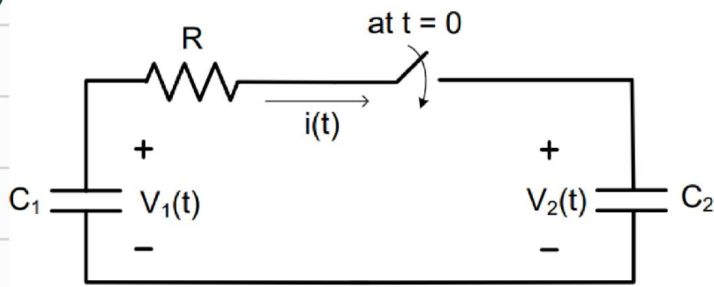

$$Q = CV$$

@ $t = 0^-$,
 $Q_1 \& Q_2$
 $\therefore Q_1 = C_1 V_1(0^-)$
 $\& Q_2 = C_2 V_2(0^-)$

KVL @ $t \geq 0$, $-V_1 + iR + V_2 = 0$
 $\therefore V_1 = V_2 + iR$

$$\therefore \frac{1}{C_1} \int i dt + \frac{1}{C_2} \int i dt = iR$$

$$\therefore \frac{1}{C_1} \cdot i + \frac{1}{C_2} \cdot i = i'R$$



a) $\therefore 0 = \frac{800}{3} + 3i'$

b) \therefore Time constant $= R \cdot \frac{C_1 C_2}{C_1 + C_2} = 1.125 \text{ E } 9 \text{ ns}$

c) $V_1(0^+) = V_1(0^-) = \frac{8}{5 \text{ E } -3} = 1600 \text{ V}$ $V_1(\infty) = 0$
 $V_2(0^+) = V_2(0^-) = \frac{-8}{15 \text{ E } -3} = -\frac{1600}{3} \text{ V}$ $V_2(\infty) = 0$
 $i(0^+) = \frac{V_1 - V_2}{R} = 7.11 \text{ A}$ $i(\infty) = 0$

⑨ Like an Imple.

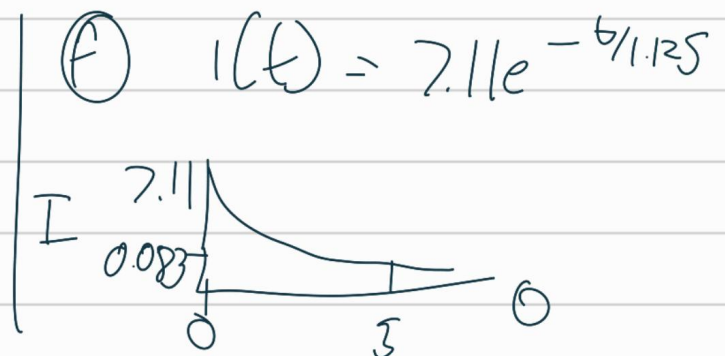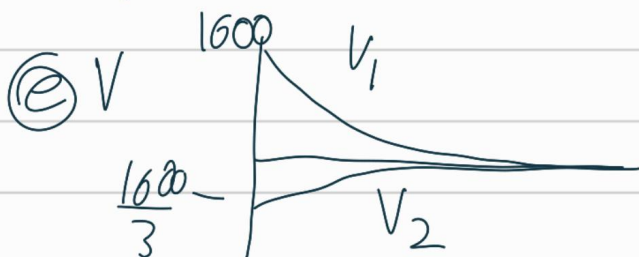d) $V_1(t) = 1600 e^{-t/1.125}$ $V_2(t) = -\frac{1600}{3} e^{-t/1.125}$



4.5 e 2 / 2


✓ - 0 pts Correct

- 1 pts V1

- 1 pts V2

- 2 pts No answer

③

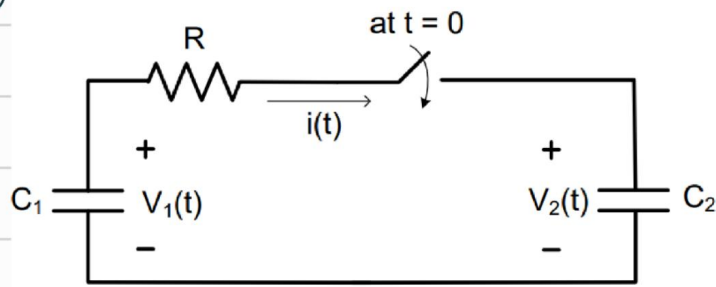

$$Q = CV$$

$$\begin{aligned} @ t=0^- \\ Q_1 \& Q_2 \\ \therefore Q_1 = C_1 V_1(0^-) \\ \& Q_2 = C_2 V_2(0^-) \end{aligned}$$

$$\text{KVL @ } t \geq 0, \quad -V_1 + iR + V_2 = 0 \\ \therefore V_1 = V_2 + iR$$

$$\therefore \frac{1}{C_1} \int i dt + \frac{1}{C_2} \int i dt = iR$$

$$\therefore \frac{1}{C_1} i + \frac{1}{C_2} i = i'R$$



$$a) \quad \therefore 0 = \frac{800}{3} + 3i'$$

$$b) \quad \therefore \text{Time constant} = R \frac{C_1 C_2}{C_1 + C_2} = 1.125 \text{ E } 9 \text{ ns}$$

$$\begin{aligned} c) \quad V_1(0^+) = V_1(0^-) = \frac{8}{5 \text{ E } -3} = 1600 \text{ V} \quad V_1(\infty) = 0 \\ V_2(0^+) = V_2(0^-) = \frac{-8}{15 \text{ E } -3} = -\frac{1600}{3} \text{ V} \quad V_2(\infty) = 0 \\ i(0^+) = \frac{V_1 - V_2}{R} = 7.11 \text{ A} \quad i(\infty) = 0 \end{aligned}$$

⑨ Like an Imple.
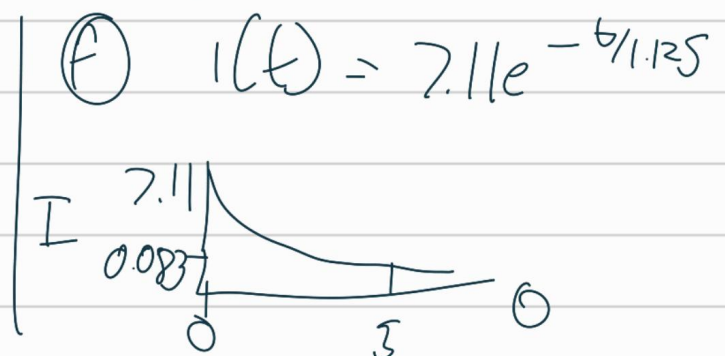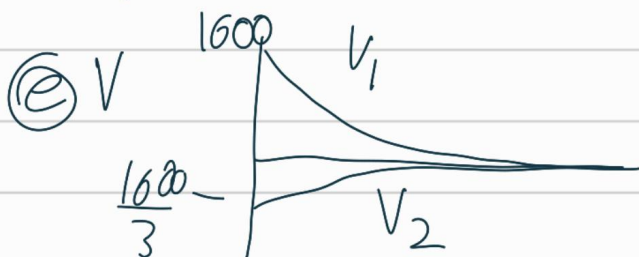
$$d) \quad V_1(t) = 1600 e^{-t/1.125} \quad V_2(t) = -\frac{1600}{3} e^{-t/1.125}$$




4.6 f 2 / 2

✓ - 0 pts Correct

- 2 pts No answer

③

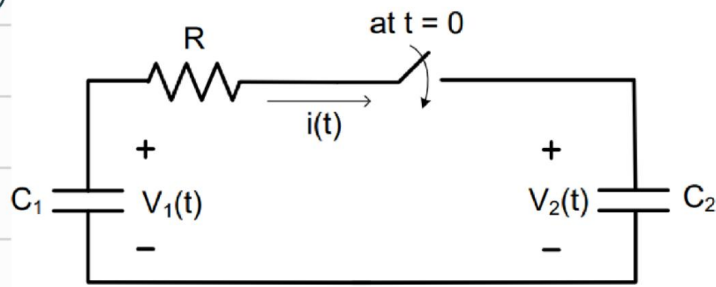

$$Q = CV$$

$$\begin{aligned} @ t=0^- \\ Q_1 \& Q_2 \\ \therefore Q_1 = C_1 V_1(0^-) \\ \& Q_2 = C_2 V_2(0^-) \end{aligned}$$

$$\text{KVL @ } t \geq 0, \quad -V_1 + iR + V_2 = 0 \\ \therefore V_1 = V_2 + iR$$

$$\therefore \frac{1}{C_1} \int i dt + \frac{1}{C_2} \int i dt = iR$$

$$\therefore \frac{1}{C_1} \cdot i + \frac{1}{C_2} \cdot i = i'R$$



$$a) \quad \therefore 0 = \frac{800}{3} + 3i'$$

$$b) \quad \therefore \text{Time constant} = R \cdot \frac{C_1 C_2}{C_1 + C_2} = 1.125 \text{ E } 9 \text{ ns}$$

$$\begin{aligned} c) \quad V_1(0^+) &= V_1(0^-) = \frac{8}{5 \text{ E } -3} = 1600 \text{ V} & V_1(\infty) &= 0 \\ V_2(0^+) &= V_2(0^-) = \frac{-8}{15 \text{ E } -3} = -\frac{1600}{3} \text{ V} & V_2(\infty) &= 0 \\ i(0^+) &= \frac{V_1 - V_2}{R} = 7.11 \text{ A} & i(\infty) &= 0 \end{aligned}$$

⑨ Like an Imple.
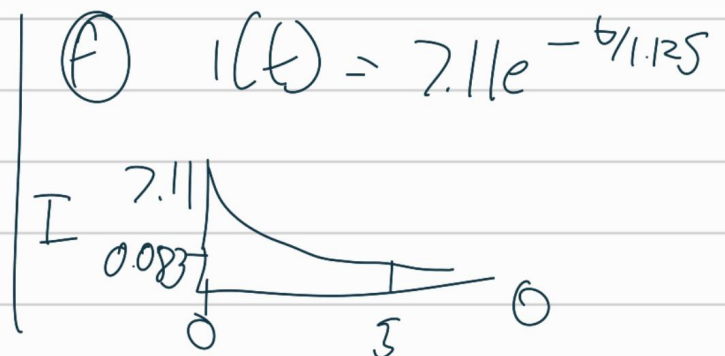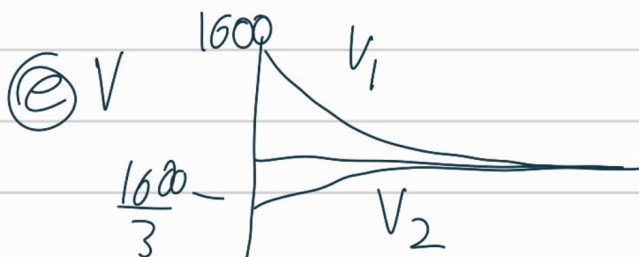
$$d) \quad V_1(t) = 1600 e^{-t/1.125} \quad V_2(t) = -\frac{1600}{3} e^{-t/1.125}$$




4.7 g 3 / 3

✓ - 0 pts Correct

- 1 pts partially incorrect

- 3 pts did not answer

⑤

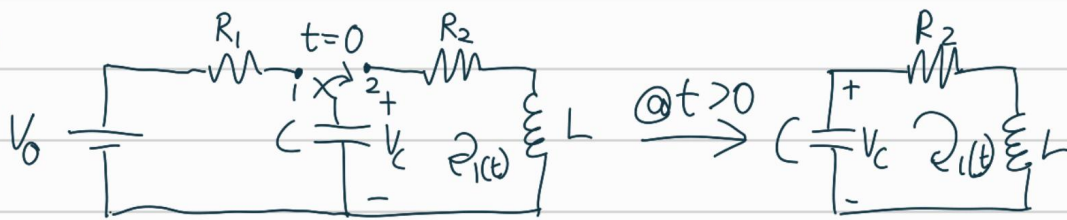

$$L i' = V$$

$$C V' = i$$

$$V = \frac{1}{C} \int i dt$$

@ Steady State: $V_c = V_0$

@ $V_c(0^-) = V_0$, & $V_c(0^+) = V_c$

$$0 = \frac{1}{C} \int i dt + i R_2 + L \frac{di}{dt}$$

$$0 = \frac{1}{C} i' + i' R_2 + L i''$$

① $i(0^+) = i(0^-) = 0$

$$\left. \frac{di(t)}{dt} \right|_{t=0} = \frac{V_c(0^+)}{L} = 2 \text{ E } 8$$

$$0 = \frac{1}{C} i(0^+) + R_2 \left. \frac{di}{dt} \right|_{t=0} + L \left. \frac{d^2 i}{dt^2} \right|_{t=0}$$

$$0 + 40(2 \text{ E } 8) + 10 \text{ E } -9 i'' = 0$$

$$\therefore i'' = -80 \text{ E } 16$$


5.1 a 5 / 5

✓ - 0 pts Correct

- 1 pts partially incorrect

- 5 pts did not answer

⑤

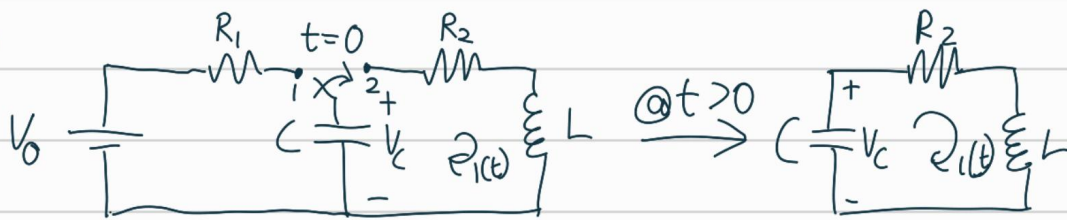

$$L i' = V$$

$$C V' = i$$

$$V = \frac{1}{C} \int i dt$$

@ Steady State: $V_c = V_0$

@ $V_c(0^-) = V_0$, & $V_c(0^+) = V_c$

$$0 = \frac{1}{C} \int i dt + i R_2 + L \frac{di}{dt}$$

$$0 = \frac{1}{C} i' + i' R_2 + L i''$$

① $i(0^+) = i(0^-) = 0$

$$\left. \frac{di(t)}{dt} \right|_{t=0} = \frac{V_c(0^+)}{L} = 2 \text{ E } 8$$

$$0 = \frac{1}{C} i(0^+) + R_2 \left. \frac{di}{dt} \right|_{t=0} + L \left. \frac{d^2 i}{dt^2} \right|_{t=0}$$

$$0 + 40(2 \text{ E } 8) + 10 \text{ E } -9 i'' = 0$$

$$\therefore i'' = -80 \text{ E } 16$$

5.2 b 10 / 10

✓ - 0 pts Correct

- 2 pts $2 \times 10^8 \text{ (A/s)}$

- 2 pts $8 \times 10^{17} \text{ (A/s}^2\text{)}$

- 10 pts did not answer

6


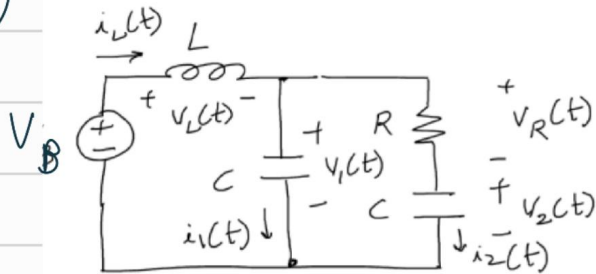


Figure 6.

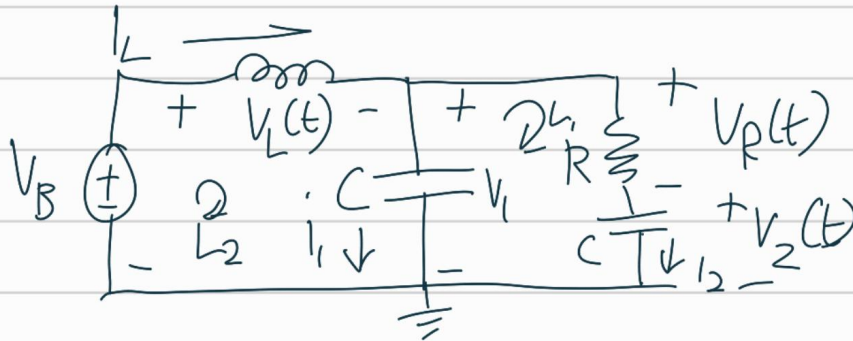

$$V = \frac{1}{C} \int i dt$$

$$i = V$$

$$I = \frac{1}{L} \int V dt$$

@ L₁ : $V_R(t) + V_2(t) = V_1(t) \rightarrow i_2 R + \frac{1}{C} \int i_2 dt = \frac{1}{C} \int i_1 dt$

@ L₂ : $V_B(t) = V_L(t) + V_1(t) \rightarrow V_B = L i_L' + R i_2(t) + \frac{1}{C} \int i_2 dt$

@ K(L : $i_L(t) = i_1(t) + i_2(t)$

@ $i_1(0^+) = i_L(0^+) - i_R(0^+) = 4 \text{ mA} - \frac{-2}{1000} = 6 \text{ mA}$

$$V_B = V_L + V_1$$

$$-\frac{dV_L}{dt} = \frac{i}{C} = \frac{6 \text{ mA}}{1 \text{ nF}} = 6 \text{ E6 V s}^{-1}$$

6.1 a 4 / 4

✓ - 0 pts Correct

- 1 pts $V_R(t) = -2V$

- 1 pts $i_1(t=0^+) = 6\text{mA}$

- 4 pts did not answer this question

⑥


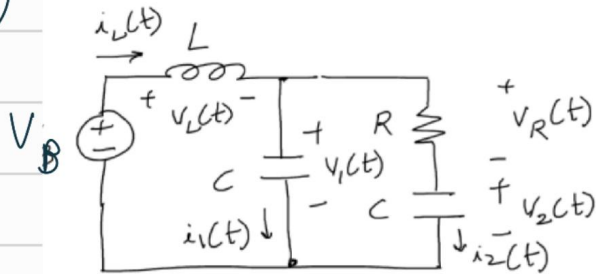


Figure 6.

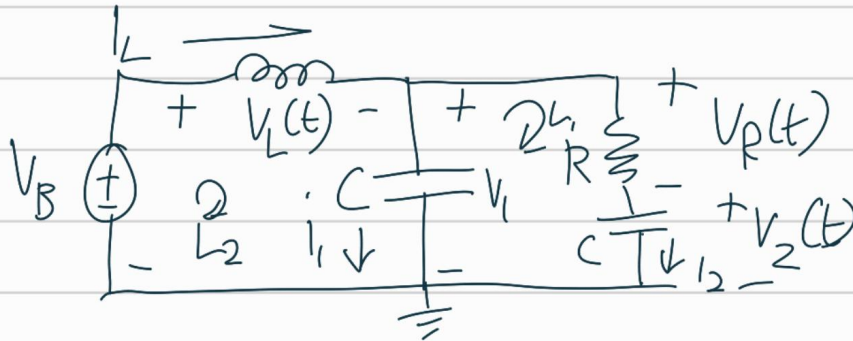

$$V = \frac{1}{C} \int i dt$$

$$i = V$$

$$I = \frac{1}{L} \int V dt$$

@ L₁ : $V_R(t) + V_2(t) = V_1(t) \rightarrow i_2 R + \frac{1}{C} \int i_2 dt = \frac{1}{C} \int i_1 dt$

@ L₂ : $V_B(t) = V_L(t) + V_1(t) \rightarrow V_B = L i_L' + R i_2(t) + \frac{1}{C} \int i_2 dt$

@ K(L) : $i_L(t) = i_1(t) + i_2(t)$

@ $i_1(0^+) = i_L(0^+) - i_R(0^+) = 4 \text{ mA} - \frac{-2}{1000} = 6 \text{ mA}$

$$V_B = V_L + V_1 \quad -\frac{dV_L}{dt} = \frac{i}{C} = \frac{6 \text{ mA}}{1 \text{ nF}} = 6 \text{ E6 V s}^{-1}$$

6.2 b 5.5 / 6

- 0 pts Correct

✓ - 0.5 pts *wrong sign*

- 1 pts answer should be $-\$6 \times 10^6 \text{ (V/s)}$

- 6 pts No answer