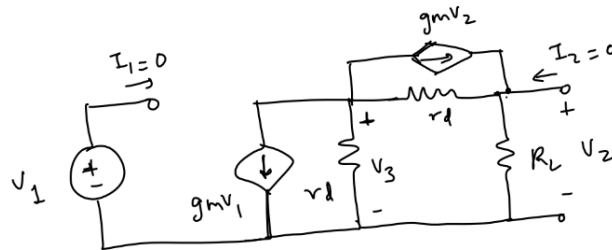


## ECE 10, Winter 2023, Homework #2, Due February 3, 2023, 11:59 pm PST


**Problem 1:** You will analyze the network shown in the figure below using the node voltage analysis method. Assume  $I_2 = 0$ .



Node voltage analysis

- Mark the datum node and unknown node-to-datum voltages on the figure above.
  - Write your appropriate equations to solve for the unknown node-to-datum voltages.
  - Collect them into a matrix form but do not solve them.
- (3 + 5 + 4 = 12 points)**

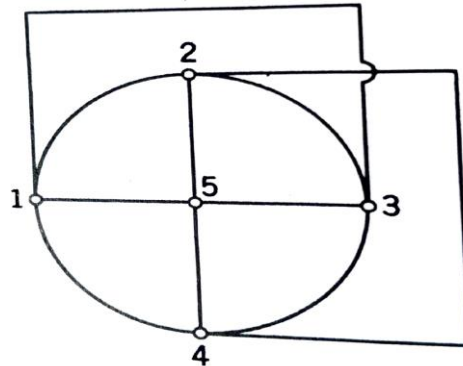
**Problem 2:** Refer to the figure below. Assume that every edge in this circuit is a 2 Ohm resistor except for the edge between the nodes 1 and 4, which is a 2V voltage source, positive at node 1. The goal is to analyze this circuit using loop current analysis method.



- Mark your loop current unknowns clearly on the circuit
  - Write the minimum number of appropriate KVL equations needed to solve for the unknowns
  - Collect them into a matrix form
  - Solve the equations from part (c) and obtain numerical values for the loop currents. **Note:** Feel free to use calculators or computers or on-line software or apps for any required matrix inversions.
- (6 + 12 + 3 + 4 = 25 points)**

**Problem 3:** Refer to the circuit schematic shown in the below figure. Assume that the independent voltage source is  $v_s(t) = 5\cos(t)$  Volts and the independent current source is  $I = 5A$ . Use superposition to determine  $v_X(t)$  for all time  $t$ .


**(15 points)**

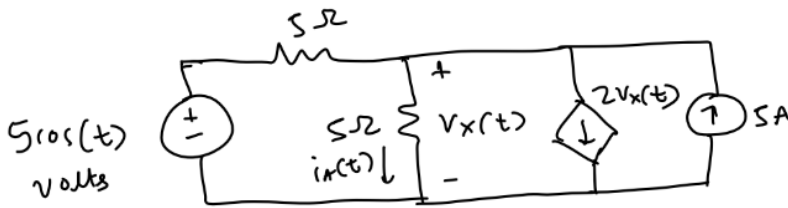

**Problem 4:** Refer again to the above figure. However, this time, ignore (remove) the dependent current source,  $2v_X(t)$ . Determine  $i_A(t)$  for all time  $t$ , but using a series of source transformations. (10 points)


**Problem 5:**

- Derive Norton's equivalent of the circuit shown in the below figure.
- Use Norton's equivalent derived from part a) to determine the value of  $v_X$  if a 200 Ohm resistor is connected across 1 and 1'. If you are unsure of your answer from part a), leave your answer in terms of  $I_N$  and  $R_N$  for partial credit. (10 + 10 = 20 points)

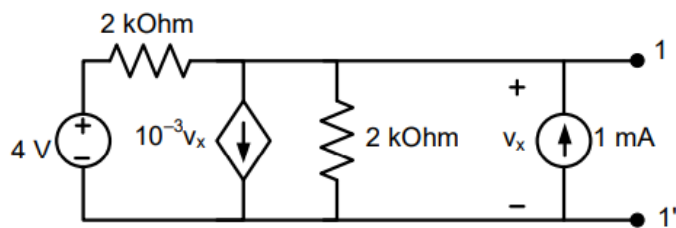

**Figure 2**

**Problem 6:** The circuit shown in Figure 3 is called a Wheatstone bridge. Derive Thevenin's equivalent of the circuit shown in Figure 3 looking into the "+" and "-" pair of terminals labeled  $V_O$ . Make sure to draw a schematic of your Thevenin's equivalent circuit. (5 + 5 + 5 = 15 points)

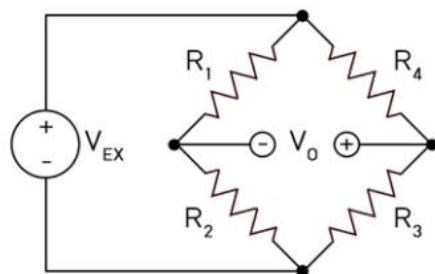

**Figure 3**