

## ECE 10, Winter 2023, Homework #1

**Problem 1:** The current (in Amperes) in a circuit varies in time as

$$i(t) = \begin{cases} \frac{1}{2}e^{-5t}, & t \geq 6 \\ 0, & t < 6 \end{cases}.$$

What is the total charge that passes through the circuit, over all time, in Coulombs? **(5 points)**

**Problem 2:** A 2.5F capacitor, charged to 10 Volts is connected across a 2 Ohm resistor at time  $t = 0$ , by closing a switch, as shown in Figure 1. The current in the circuit is shown to be of the form

$$i(t) = \begin{cases} 5e^{-t/5}, & t \geq 0 \\ 0, & t < 0 \end{cases}.$$

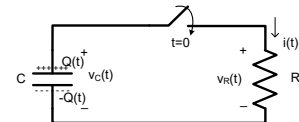


Figure 1

At a certain time,  $t = t_0$ , the current has a value 2 Amperes. The switch behaves like a wire of zero resistance when closed. At  $t = t_0$ ,

- (a) at what rate is the voltage across the capacitor,  $v_C(t)$  changing? Don't forget the correct units.
- (b) what is the voltage across the resistor,  $v_R(t)$ ?
- (c) what is the value of the charge on the capacitor,  $Q(t)$ ?

**(3 + 3 + 3 = 9 points)**

**Problem 3:** A parallel plate capacitor is connected to an ideal 5V voltage source. Suppose that the plates of the capacitor are slowly moved in time such that the capacitance decreases linearly from  $C = 10\text{pF}$  to  $C = 5\text{pF}$  in 5 seconds.

- (a) Sketch the current coming from the positive terminal of the battery and flowing into the capacitor as a function of time while the plates were being moved.
- (b) How much energy was stored in the capacitor before the plates started to move?
- (c) How much energy is stored in the capacitor after the plates have finished their movement?
- (d) How much total energy was delivered to (or removed from) the capacitor during the 5 seconds of movement?
- (e) How much energy was delivered by (or delivered to) the ideal voltage source during the 5 seconds of movement?
- (f) Do your answers to (e) and (f) indicate that energy is conserved? Explain.

**(3 + 3 + 3 + 3 + 3 + 5 = 18 points)**

**Problem 4:** Starting at time  $t = 0$ , a battery is applied across an inductor of 3H. The battery voltage increases linearly from 0 to 10V in time 5s after which, it stays at 10V.


- (a) Derive an expression for the current through the inductor as a function of time  $t$ .
- (b) Derive an expression for the energy delivered to the inductor as a function of time  $t$ .

**(10 points)**

**Problem 5:** Figure 3 shows a common, realistic model for a battery. The resistance,  $R_s$ , is often referred to as the source resistance. Derive an expression for the voltage across the battery's terminals,  $V_{ab}$  as a function of the current flowing through it,  $I$ .

**(6 points)**

**Solution:**

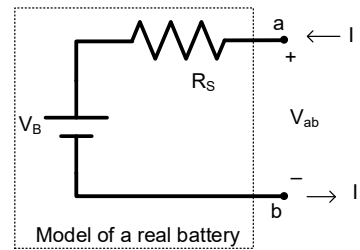

**Figure 2**