
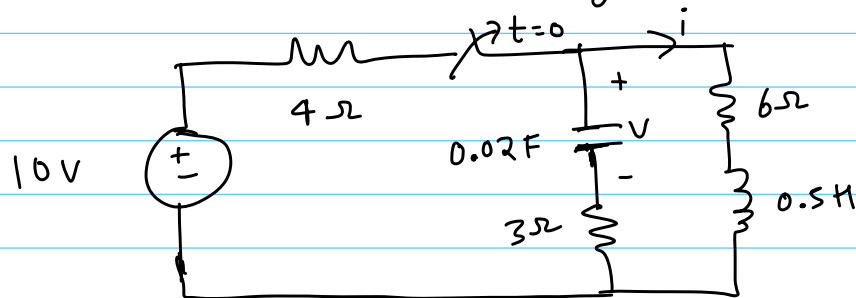


Discussion 7

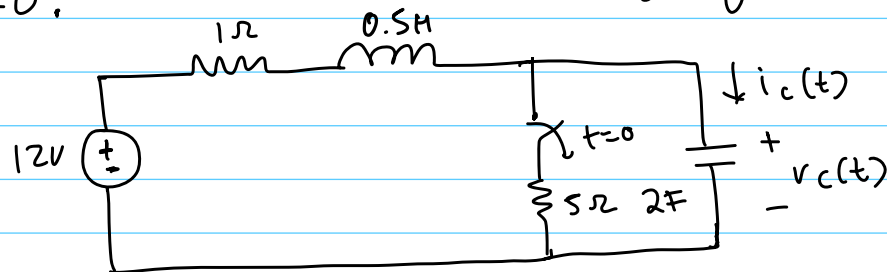
- Q1. Find current $i(t)$ in the circuit shown in the following figure assuming that the circuit reached the steady state at time $t=0^-$.



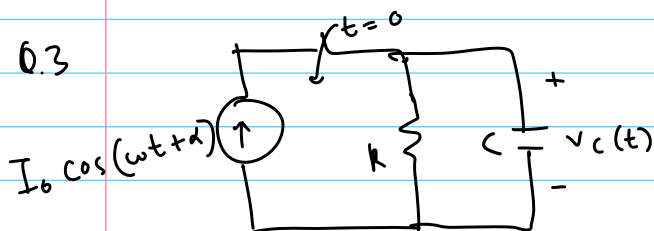- Q2. The switch has been closed for a sufficiently long time and it is opened at $t=0$.



Find the expression for a) $v_c(t)$ b) $i_c(t)$ for $t > 0$.



Assuming $v_c(t) = V_0 \cos(\omega t + \beta)$ is

Solution, find V_0 & β .

Ans.1

$$\xi \Rightarrow \frac{R}{2\sqrt{\frac{L}{C}}} \Rightarrow \frac{9}{2 \times 5} \Rightarrow 0.9 \quad \text{--- underdamped}$$

$$\sqrt{\frac{L}{C}} \Rightarrow \sqrt{\frac{50}{2}} \Rightarrow 5$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 10$$

$$i(0) \Rightarrow \frac{10}{6+4} = 1 \text{ A}$$

$$V_L(0) = 6 \text{ V}$$

$$\zeta = \xi \omega_0 \Rightarrow 9$$

Since the circuit is underdamped

$$i(t) = e^{-\sigma t} (A \cos \omega t + B \sin \omega t) + k$$


$$i(\infty) = 0 \Rightarrow k = 0$$

$$\omega = (\sqrt{1-\xi^2}) \omega_0 \Rightarrow (\sqrt{1-0.9^2}) \times 10 \Rightarrow 4.358$$

$$i(t) = e^{-\sigma t} (A \cos 4.358t + B \sin 4.358t)$$

$$i(0) = 1 \text{ A} \Rightarrow \underline{A = 1}$$

@ $t = 0$

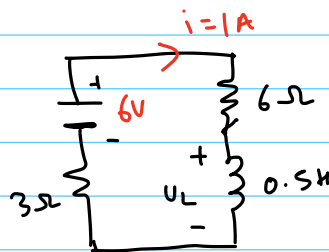

$$V_L(0) = -3$$

$$V_L = L \frac{di}{dt} \Big|_{t=0^+} = -3$$

$$-6 = \frac{di}{dt} \Big|_{t=0^+} \Rightarrow e^{-\sigma t} (-A \times 4.358 \sin(4.358t) + B(4.358) \cos(4.358t))$$

$$-6 e^{-\sigma t} (A \cos 4.358t + B \sin 4.358t) \Big|_{t=0^+}$$


$$-6 = (4.358B) - 6A$$

$$-6 = 4.358B - 9$$

$$3 = 4.358B \quad ; \quad \boxed{B = 0.688}$$

$$\boxed{i(t) \Rightarrow e^{-9t} (\cos 4.358t + 0.688 \sin 4.358t)}$$

Ans. 2

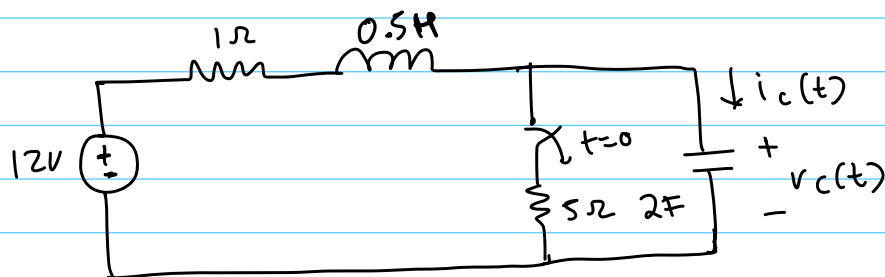

$$V_c(0) \Rightarrow \frac{5}{5+1} \times 12 \Rightarrow 10V$$

$$i_c(0^+) \Rightarrow 2A$$

$$V_c(\infty) = 12$$

$$\sqrt{\frac{L}{C}} \Rightarrow \sqrt{\frac{0.5}{2}} \Rightarrow \frac{1}{2} \quad ; \quad \alpha = \frac{R}{2\sqrt{\frac{L}{C}}} \Rightarrow 1$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow \frac{1}{1} \Rightarrow 1$$

critically damped \rightarrow 2 roots @ $\pm \omega_0 \Rightarrow -1$

$$V_c(t) = K_1 e^{-\omega_0 t} + K_2 t e^{-\omega_0 t} + K_3$$

$$v_c(t) = k_1 e^{-t} + k_2 t e^{-t} + k_3$$

$$v_c(\infty) = \boxed{k_3 = 12}$$

$$v_c(0) = k_1 + k_3 = 10 ; \quad \boxed{k_1 = -2}$$

$$i_c = \left(\frac{dv_c}{dt} \right) \Big|_{t=0} \Rightarrow 2$$

$$i_c(t) = C \left[-k_1 e^{-t} - k_2 t e^{-t} + k_2 e^{-t} \right]$$


$$i_c(0) \Rightarrow C \left[-k_1 + k_2 \right] = 2$$

$$k_2 - k_1 = 1 ; \quad \boxed{k_2 = -1}$$

$$\boxed{v_c(t) = -2e^{-t} - t e^{-t} + 12}$$

$$\boxed{i_c(t) = C \frac{dv_c}{dt} \Rightarrow 2 \times \left[(t+2)e^{-t} - e^{-t} \right] = 2(t+1)e^{-t}}$$


Ans. 3

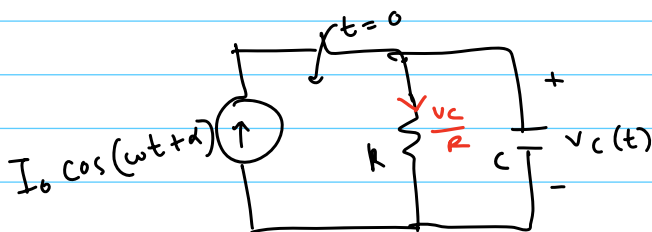

$$v_c = v_0 \cos(\omega t + \beta)$$

$$I_0 \cos(\omega t + \alpha) = \frac{v_c}{R} + C \frac{dv_c}{dt}$$
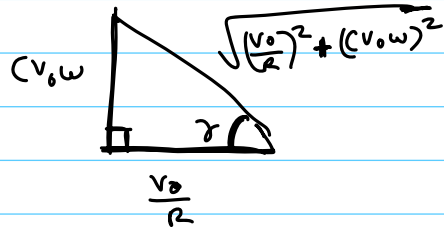
$$I_0 \cos(\omega t + \alpha) = \frac{V_0}{R} \cos(\omega t + \beta) - C V_0 \omega \sin(\omega t + \beta)$$



$$I_0 \cos(\omega t + \alpha) \Rightarrow \left[\cos \gamma \cos(\omega t + \beta) - \sin \gamma \sin(\omega t + \beta) \right] \sqrt{\left(\frac{V_0}{R}\right)^2 + (C V_0 \omega)^2}$$

$$I_0 \cos(\omega t + \alpha) \Rightarrow \sqrt{\left(\frac{V_0}{R}\right)^2 + (C V_0 \omega)^2} \cos(\omega t + \beta + \gamma)$$

$$\alpha = \beta + \gamma \quad ; \quad \underline{\underline{\beta = \alpha - \gamma \Rightarrow \alpha - \tan^{-1}(C \omega R)}}$$

$$\left(\frac{V_0}{R}\right)^2 + (C V_0 \omega)^2 = I_0^2$$

$$\boxed{V_0 = R \sqrt{I_0^2 - (C V_0 \omega)^2}}$$