

# 23S-EC ENGR-3-LEC-1 Homework 8

SANJIT SARDA

TOTAL POINTS

**100 / 100**

QUESTION 1

1 Q1 : Expression for  $V_0$  **100 / 100**

✓ - **0 pts** Correct

- **10 pts** Almost correct

- **25 pts** Partially Incorrect

- **40 pts** Mostly Incorrect



- **100 pts** Incorrect

# EE3 Spring 2023
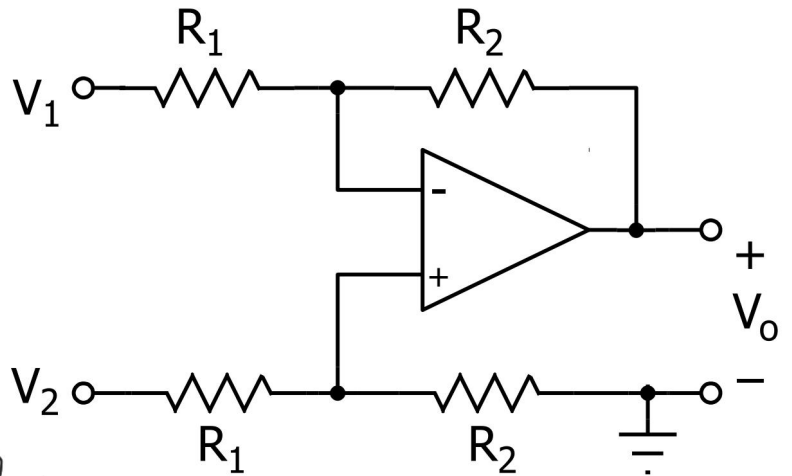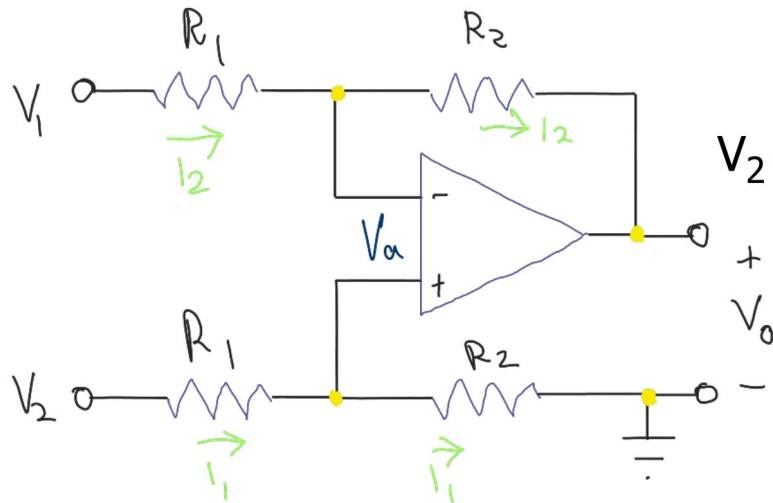
## Homework Problem 8

Find  $V_o = f(V_1, V_2, R_1, R_2)$ .

Remember the Summing Point Constraints and KCL equations!



Differential Amplifier.

$$\textcircled{a} V_- \quad \frac{V_a - V_1}{R_1} + \frac{V_a - V_o}{R_2} = 0$$

$$\textcircled{a} V_+ \quad \frac{V_a - V_2}{R_1} + \frac{V_a}{R_2} = 0$$

Solving:

$$V_a \left( \frac{R_1 + R_2}{R_1 R_2} \right) = \frac{V_2}{R_1}$$

$$\therefore V_a = V_2 \left( \frac{R_2}{R_1 + R_2} \right)$$

$$V_a \left( \frac{R_1 + R_2}{R_1 R_2} \right) - \frac{V_1}{R_1} - \frac{V_o}{R_2} = 0$$

$$\therefore \frac{V_o}{R_2} = V_2 \left( \frac{R_2}{R_1 + R_2} \right) \left( \frac{R_1 + R_2}{R_1 R_2} \right) - \frac{V_1}{R_1}$$

$$\therefore \frac{V_o}{R_2} = \frac{1}{R_1} (V_2 - V_1) \quad \therefore V_o = \frac{R_2}{R_1} (V_2 - V_1)$$

1 Q1 : Expression for  $V_0$  100 / 100

✓ - 0 pts Correct

- 10 pts Almost correct

- 25 pts Partially Incorrect

- 40 pts Mostly Incorrect

- 100 pts Incorrect

