

# 23S-EC ENGR-3-LEC-1 Homework 4

SANJIT SARDA

TOTAL POINTS

**100 / 100**

QUESTION 1

1 Thevenin Voltage 50 / 50

✓ - 0 pts Correct

- 10 pts Partially incorrect

- 25 pts Mostly incorrect

- 50 pts Incorrect/Blank

QUESTION 2

2 Thevenin Resistance 50 / 50

✓ - 0 pts Correct

- 10 pts Partially incorrect

- 25 pts Mostly incorrect


- 50 pts Incorrect/Blank

EE3 Spring 2023  
Homework Problem 4

Open:  $A-B = 742.857$

$I = \frac{26}{3}$

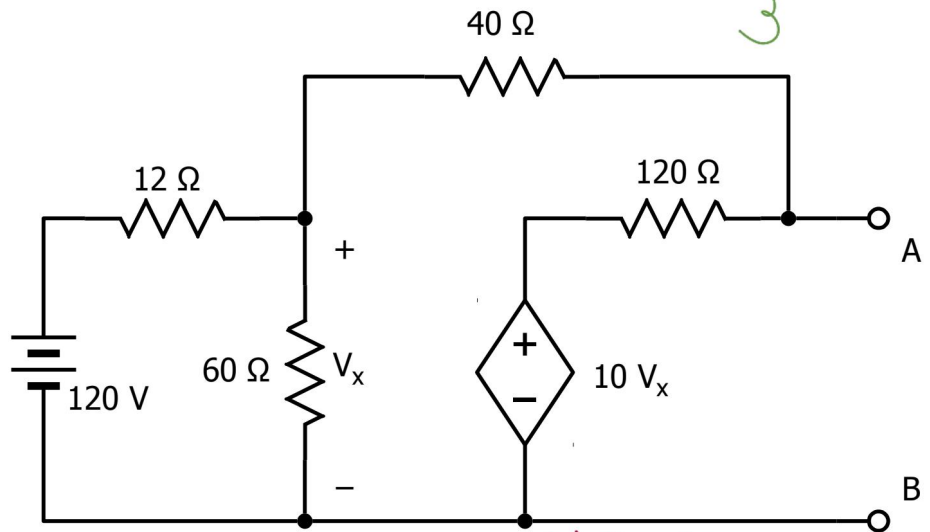Find the Thévenin  
Equivalent voltage and  
resistance of this circuit.



Open Voltage:

① C:  $\frac{C-120}{12} + \frac{C-A}{40} + \frac{C}{60} = 0$

② A:  $\frac{A-C}{40} + \frac{A-10C}{120} = 0$

Solving

Thévenin Voltage =  $A = 743V$

Short Current

① C:  $\frac{C-120}{12} + \frac{C}{40} + \frac{C}{60} = 0$

② A:  $\frac{C}{40} + \frac{10C}{120} + I = 0$

Solving for  $I$ , the short circuit  
current,  $I = \frac{26}{3} = \text{Norton}$   
Current

$V = 742V, I = \frac{26}{3} \therefore R = \frac{V}{I} = 85.6\Omega$



1 Thevenin Voltage 50 / 50

✓ - 0 pts Correct

- 10 pts Partially incorrect

- 25 pts Mostly incorrect

- 50 pts Incorrect/Blank

## 2 Thevenin Resistance 50 / 50

✓ - **0 pts** *Correct*

- **10 pts** Partially incorrect

- **25 pts** Mostly incorrect

- **50 pts** Incorrect/Blank