

### Discussion3


Analyze the networks shown in the figure below using the node voltage analysis method and the loop current analysis method.

#### Node voltage analysis

- (a) Mark the datum node and unknown node-to-datum voltages in the figure below.
- (b) Write your appropriate equations to solve for the unknown node-to-datum voltages.
- (c) Collect them into a matrix form but do not solve them.


#### Loop current analysis

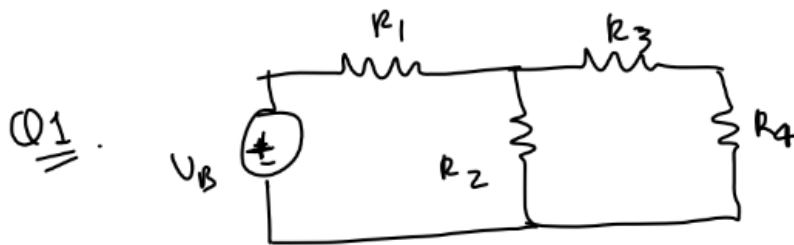- (d) Mark your loop current unknowns clearly in the circuit.
- (e) Write the appropriate KVL equations needed to solve for the unknown.
- (f) Collect them into a matrix form but do not solve them.



Q2.

Example:

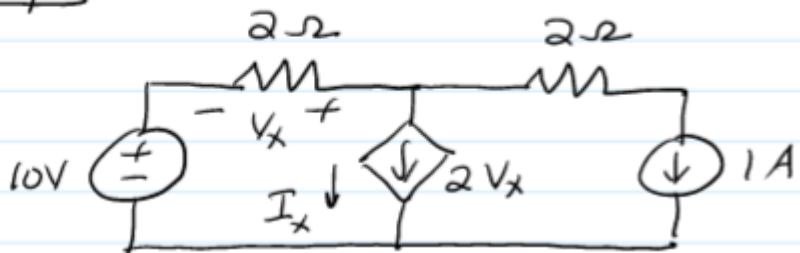

Q3. Using source transformation, find the effective voltage and output impedance of a set of “n” batteries connected in parallel.

