

# 23S-EC ENGR-3-LEC-1 Homework 6

SANJIT SARDA

TOTAL POINTS

**100 / 100**

QUESTION 1

1 Q1 25 / 25

- ✓ - 0 pts *Correct*
- 5 pts Minor Mistake
- 10 pts Major Mistake
- 25 pts Incorrect

QUESTION 2

2 Q2 25 / 25

- ✓ - 0 pts *Correct*
- 5 pts Minor mistake
- 10 pts Major mistake
- 25 pts Incorrect

QUESTION 3

3 Q3 25 / 25

- ✓ - 0 pts *Correct*
- 25 pts Incorrect

QUESTION 4


4 Q4 25 / 25

- ✓ - 0 pts *Correct*
- 5 pts Repeat mistake
- 5 pts Minor mistake
- 10 pts Major mistake
- 25 pts Incorrect

# EE3 Spring 2023

## Homework Problem 6

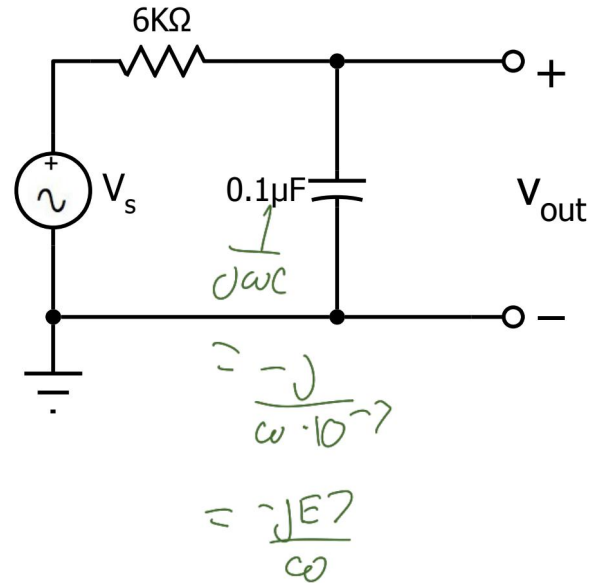- 1) Derive the expression for the capacitive impedance, keeping  $\omega$  as an unknown.
- 2) Derive the expression for  $v_{out} / v_s$ . Treat this as a voltage divider, with  $\omega$  as an unknown.
- 3) Using your favorite analysis code, Compute the magnitude and phase angle of the resulting expression over a range of frequencies from 100 Hz to 100KHz.
- 4) Plot the resulting two curves as a Bode Plot as shown on Slide 23 of the Week 6 Lecture. Keep the log scaling on the frequency axis and the linear scales on the vertical axes. Express the magnitude in dB.



①  $Z_C = \frac{-j \cdot 1E7}{\omega}$

②  $V_{out} = \frac{Z_C}{Z_R + Z_C} V_s \rightarrow \frac{V_o}{V_s} = \frac{(-j \cdot 1E7)/\omega}{(6000 + (-j \cdot 1E7)/\omega)} = \frac{2.5E7}{9\omega^2 + 2.5E7} - j \frac{15000}{9\omega^2 + 2.5E7}$

③

```
# freq_in is from 100Hz to 100kHz
freq_in = np.linspace(100, 100000, 10000)
# convert to omega
omega = 2 * np.pi * freq_in
def vout(omega):
    # voltage divider with Z1 = 6000, Z2 = 1/(j*omega*10e-7)
    # return (-1j*1e7)/(omega*(6000-(1j*1e7)/omega)) # ? this does the same thing but eh is less adventurous
    return (2.5e7)/(9*omega**2 + 2.5e7) - 1j*(omega*15000)/(9*omega**2 + 2.5e7)

# plot the magnitude and phase of vout in a Bode plot
plt.figure(figsize=(10, 5))
plt.subplot(121)
plt.semilogx(freq_in, 20*np.log10(np.abs(vout(omega))))
plt.xlabel('Frequency (Hz)')
plt.title('Magnitude of Bode plot of the voltage divider')
plt.ylabel('Magnitude (dB)')
plt.subplot(122)
plt.semilogx(freq_in, np.angle(vout(omega)))
plt.xlabel('Frequency (Hz)')
plt.ylabel('Phase (rad)')
plt.title('Phase shift of Bode plot of the voltage divider')
plt.show()
```

✓ 0.5s

Python Python Python

1 Q1 25 / 25

✓ - **0 pts** *Correct*

- **5 pts** Minor Mistake


- **10 pts** Major Mistake

- **25 pts** Incorrect

# EE3 Spring 2023

## Homework Problem 6

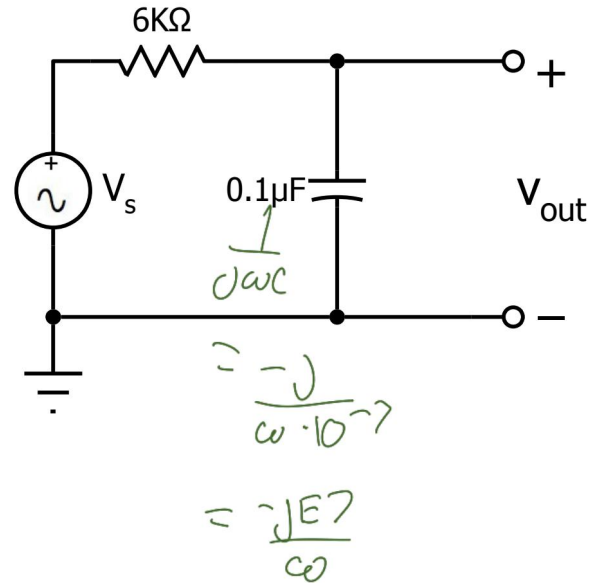- 1) Derive the expression for the capacitive impedance, keeping  $\omega$  as an unknown.
- 2) Derive the expression for  $v_{out} / v_s$ . Treat this as a voltage divider, with  $\omega$  as an unknown.
- 3) Using your favorite analysis code, Compute the magnitude and phase angle of the resulting expression over a range of frequencies from 100 Hz to 100KHz.
- 4) Plot the resulting two curves as a Bode Plot as shown on Slide 23 of the Week 6 Lecture. Keep the log scaling on the frequency axis and the linear scales on the vertical axes. Express the magnitude in dB.



①  $Z_C = \frac{-j \cdot 1E7}{\omega}$

②  $V_{out} = \frac{Z_C}{Z_R + Z_C} V_s \rightarrow \frac{V_o}{V_s} = \frac{(-j \cdot 1E7)/\omega}{(6000 + (-j \cdot 1E7)/\omega)} = \frac{2.5E7}{9\omega^2 + 2.5E7} - j \frac{15000}{9\omega^2 + 2.5E7}$

③

```
# freq_in is from 100Hz to 100kHz
freq_in = np.linspace(100, 100000, 10000)
# convert to omega
omega = 2 * np.pi * freq_in
def vout(omega):
    # voltage divider with Z1 = 6000, Z2 = 1/(j*omega*10e-7)
    # return (-1j*1e7)/(omega*(6000-1j*1e7)/omega) # ? this does the same thing but eh is less adventurous
    return (2.5e7)/(9*omega**2 + 2.5e7) - 1j*(omega*15000)/(9*omega**2 + 2.5e7)

# plot the magnitude and phase of vout in a Bode plot
plt.figure(figsize=(10, 5))
plt.subplot(121)
plt.semilogx(freq_in, 20*np.log10(np.abs(vout(omega))))
plt.xlabel('Frequency (Hz)')
plt.title('Magnitude of Bode plot of the voltage divider')
plt.ylabel('Magnitude (dB)')
plt.subplot(122)
plt.semilogx(freq_in, np.angle(vout(omega)))
plt.xlabel('Frequency (Hz)')
plt.ylabel('Phase (rad)')
plt.title('Phase shift of Bode plot of the voltage divider')
plt.show()
```

✓ 0.5s

Python Python Python

2 Q2 25 / 25

✓ - **0 pts** *Correct*

- **5 pts** Minor mistake


- **10 pts** Major mistake

- **25 pts** Incorrect

# EE3 Spring 2023

## Homework Problem 6

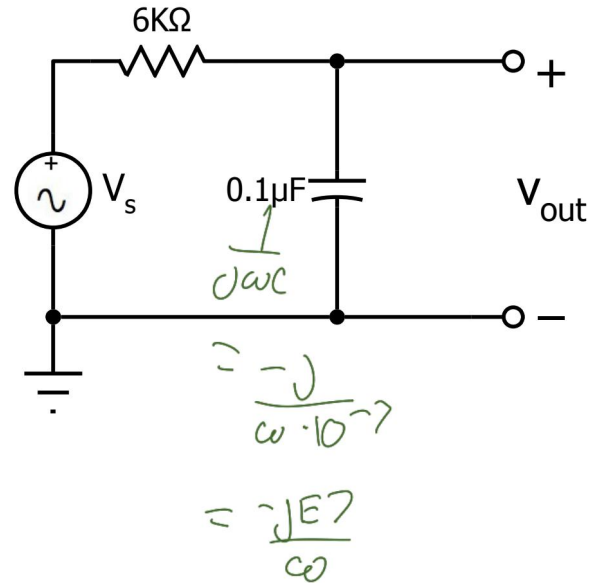- 1) Derive the expression for the capacitive impedance, keeping  $\omega$  as an unknown.
- 2) Derive the expression for  $v_{out} / v_s$ . Treat this as a voltage divider, with  $\omega$  as an unknown.
- 3) Using your favorite analysis code, Compute the magnitude and phase angle of the resulting expression over a range of frequencies from 100 Hz to 100kHz.
- 4) Plot the resulting two curves as a Bode Plot as shown on Slide 23 of the Week 6 Lecture. Keep the log scaling on the frequency axis and the linear scales on the vertical axes. Express the magnitude in dB.



①  $Z_c = \frac{-j \cdot 1E7}{\omega}$

②  $V_{out} = \frac{Z_c}{Z_R + Z_c} V_s \rightarrow \frac{V_o}{V_s} = \frac{(-j \cdot 1E7) / \omega}{(6000 + (-j \cdot 1E7) / \omega)} = \frac{2.5E7}{9\omega^2 + 2.5E7} - j \frac{15000}{9\omega^2 + 2.5E7}$

③

```
# freq_in is from 100Hz to 100kHz
freq_in = np.linspace(100, 100000, 10000)
# convert to omega
omega = 2 * np.pi * freq_in
def vout(omega):
    # voltage divider with Z1 = 6000, Z2 = 1/(j*omega*10e-7)
    # return (-1j*1e7)/(omega*(6000-(1j*1e7)/omega)) # ? this does the same thing but eh is less adventurous
    return (2.5e7)/(9*omega**2 + 2.5e7) - 1j*(omega*15000)/(9*omega**2 + 2.5e7)

# plot the magnitude and phase of vout in a Bode plot
plt.figure(figsize=(10, 5))
plt.subplot(121)
plt.semilogx(freq_in, 20*np.log10(np.abs(vout(omega))))
plt.xlabel('Frequency (Hz)')
plt.title('Magnitude of Bode plot of the voltage divider')
plt.ylabel('Magnitude (dB)')
plt.subplot(122)
plt.semilogx(freq_in, np.angle(vout(omega)))
plt.xlabel('Frequency (Hz)')
plt.ylabel('Phase (rad)')
plt.title('Phase shift of Bode plot of the voltage divider')
plt.show()
```

✓ 0.5s

Python Python Python


3 Q3 25 / 25

✓ - 0 pts Correct


- 25 pts Incorrect

9

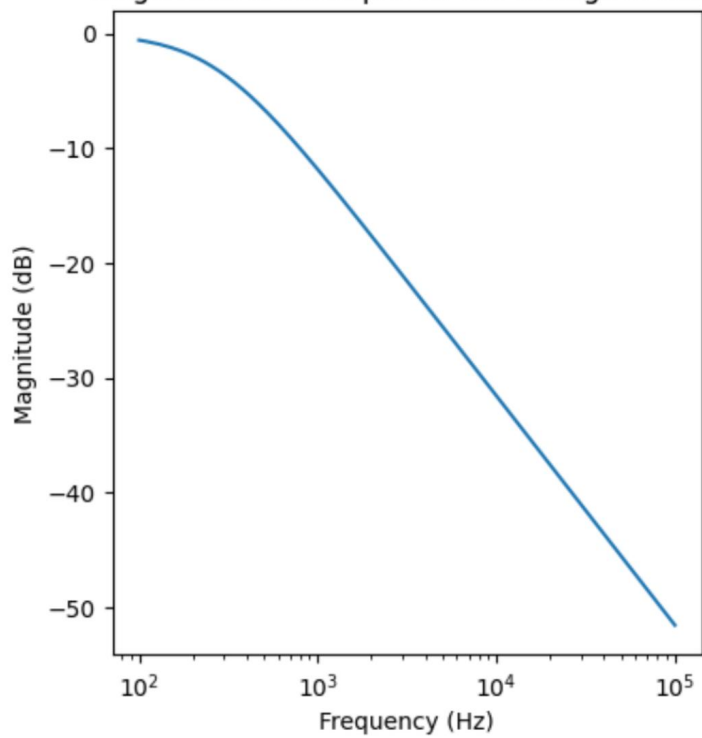Magnitude of Bode plot of the voltage divider



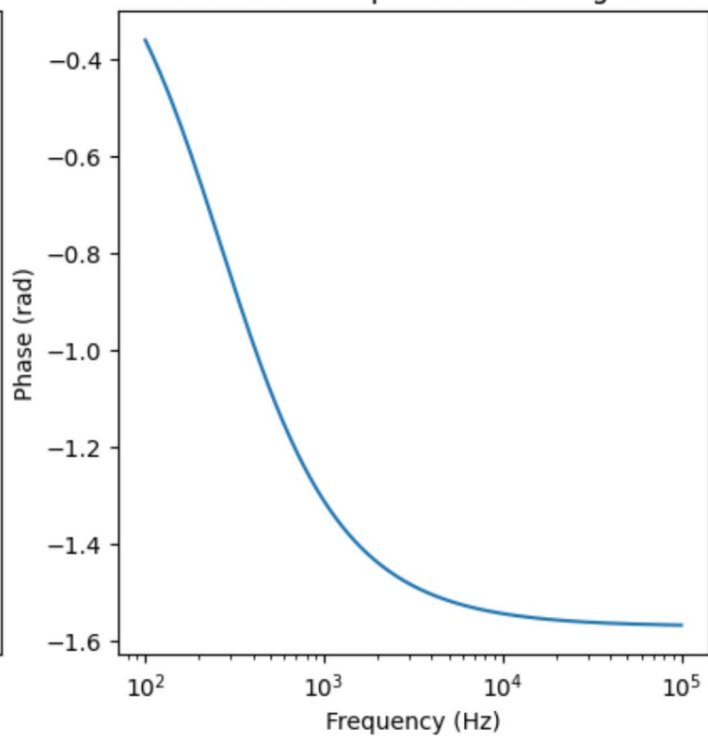Phase shift of Bode plot of the voltage divider





4 Q4 25 / 25

✓ - 0 pts Correct

- 5 pts Repeat mistake

- 5 pts Minor mistake

- 10 pts Major mistake

- 25 pts Incorrect