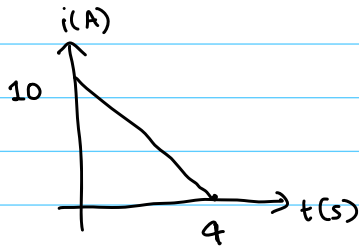


Discussion 1 Solutions


Ans 1.



$q = \int i dt$; Area under the graph (i versus t) will give us net charge flow.

Hence, $\Delta q = \text{Area} \Rightarrow \frac{1}{2} \times \text{base} \times \text{height} = \frac{1}{2} \times 4 \times 10 = \underline{20C}$

Ans. 2

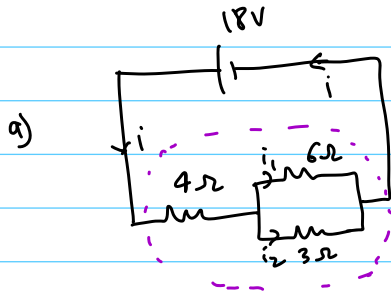


6Ω & 3Ω resistors are in parallel. Their equivalent resistance is

$$\frac{1}{R_{eq}} = \frac{1}{6} + \frac{1}{3} ; R_{eq} = 2\Omega$$

Now this 2Ω and 4Ω resistances are in series and their equivalent resistance is $4+2=6\Omega$.

Find equivalent circuit

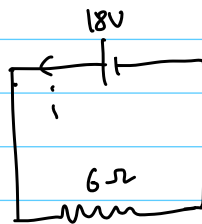

$$i = \frac{18V}{6\Omega} = \underline{3A}$$

b) Current i splits between 3Ω & 6Ω resistors in the inverse ratio of the resistances since they are in parallel.

$$i_1 = \frac{3}{3+6} \times 3A \Rightarrow \underline{1A}$$


$$i_2 = \frac{6}{3+6} \times 3A \Rightarrow \underline{2A}$$

c) Ideal voltage source has zero resistance.
Ideal current source has ∞ resistance

It can also be understood from the slope of ($V-I$) characteristic.



Ideal current slope

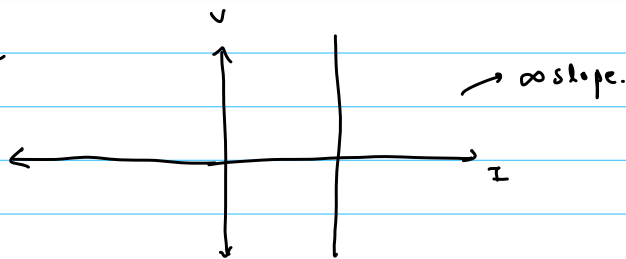

Ans 3.

$$\frac{dy}{dt} = 2(25-y)$$

$$\int \frac{dy}{25-y} = \int 2 dt \Rightarrow -\ln(y-25) = 2t + c$$

$$y-25 = e^{-2t-c}$$

$$y = 25 + e^{-c} e^{-2t} ; \text{ Assume } e^{-c} = k$$

$$y(t) = 25 + k e^{-2t} ; \text{ Since } y(0) = 40$$

$$y(0) = 25 + k = 40 \Rightarrow (k = 15)$$

$$y(t) = 25 + 15 e^{-2t}$$

Ans. 4

$$Y = 3 \cos \theta + 4 \sin \theta$$


$$Y = \sqrt{3^2+4^2} \cdot \left[\frac{3}{\sqrt{3^2+4^2}} \cos \theta + \frac{4}{\sqrt{3^2+4^2}} \sin \theta \right] \Rightarrow 5 \cdot \left[\frac{3}{5} \cos \theta + \frac{4}{5} \sin \theta \right]$$

$$\begin{matrix} \downarrow & \downarrow \\ \sin x & \cos x \end{matrix}$$

$$\text{Identity: } \sin(\theta_1 + \theta_2) = \sin \theta_1 \cos \theta_2 + \sin \theta_2 \cos \theta_1$$


$$5 \sin \left(\theta + \tan^{-1} \left(\frac{3}{4} \right) \right)$$

$$A = 5, \beta = \tan^{-1} \left(\frac{3}{4} \right)$$

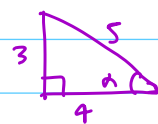


Ans.5

a)

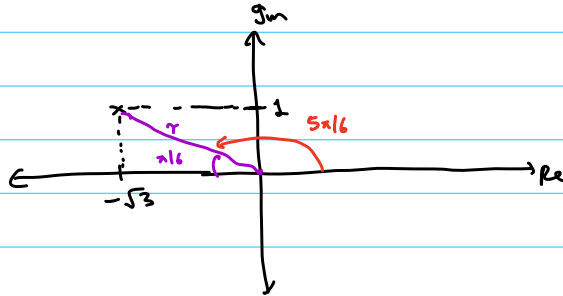

$$r = \sqrt{(\sqrt{3})^2 + 1} \Rightarrow 2 ; \theta = 5\pi/6 \Rightarrow \text{Polar form} = 2e^{i5\pi/6}$$

b)

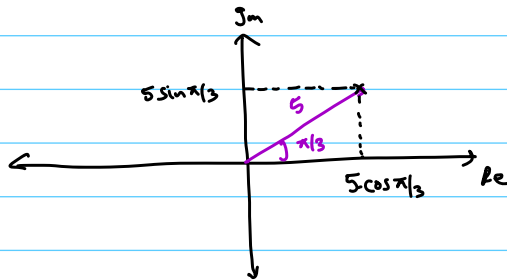

real component $\Rightarrow 5\cos(\pi/3)$

imaginary component $\Rightarrow 5\sin(\pi/3)$

$$z = 5\cos(\pi/3) + i5\sin(\pi/3)$$

$$z = \frac{5}{2} + i\frac{5\sqrt{3}}{2}$$

Rectangular form

Ans.6

Substituting i as $A_1 e^{s_1 t}$ in the equation, we get

$$A_1 s_1 e^{s_1 t} + \frac{R}{L} A_1 e^{s_1 t} = 0$$

$$s_1 + \frac{R}{L} = 0 ; s_1 = -\frac{R}{L}$$


$$i(t) = A_1 e^{-\frac{R}{L}t} ; \text{since } i(0) = I_0, A_1 = I_0$$

$$\underline{i(t) = I_0 e^{-\frac{R}{L}t}}$$

Ans.7

$$P = VI, \text{ Energy dissipated} = \int P dt$$
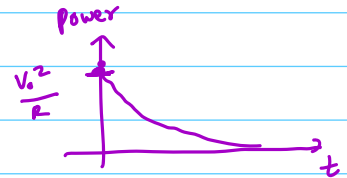
$$V(\text{across } R) = V_0 e^{-2t}, I(\text{across } R) = \frac{V_0}{R} e^{-2t}$$



$$\text{Energy dissipated} = \int_0^{\infty} \frac{V_0^2}{R} e^{-4t} dt \Rightarrow -\frac{V_0^2}{4R} \int_0^{\infty} e^{-4t} dt \Rightarrow \underline{\underline{\frac{V_0^2}{4R}}}$$