

23W-EC ENGR-11L-LEC-1 Module 2: Simple Resistive Networks

SANJIT SARDA

TOTAL POINTS

64 / 65

QUESTION 1

Superposition 15 pts

1.1 Sample Setup Image 1 / 1

✓ - 0 pts *Correct*

1.2 Theoretical Analysis 5 / 5

✓ - 0 pts *Correct*

- 4 pts Incorrect Values
- 5 pts Major analytical error
- 2 pts Slightly incorrect
- 5 pts Missing

1.3 Voltage and Current Measurement 5 / 6

✓ - 0 pts *Correct*

- 3 pts Partially Incorrect
- 6 pts Fully Incorrect

✓ - 1 pts *Small Mistake*

- 1 pts Multiple wrong values

💬 +5 and -5 values has been interchanged

1.4 Discussion 3 / 3

✓ - 0 pts *Correct*

- 1 pts Slightly incorrect
- 3 pts Incorrect

QUESTION 2

Thevenin/Norton Equivalent 30 pts

2.1 Sample Setup Image 1 / 1

✓ - 0 pts *Correct*

- 1 pts Image Missing

2.2 Impedance Measurement 5 / 5

✓ - 0 pts *Correct*

- 1 pts Minor Mistake
- 5 pts Missing

2.3 Theoretical Analysis 6 / 6

✓ - 0 pts *Correct*

- 1 pts Minor Mistake
- 2 pts Minor Mistake
- 3 pts Major Mistake
- 6 pts Missing

2.4 Voltage and Eq. Resistance in Original Circuit 6 / 6

✓ - 0 pts *Correct*

- 1 pts Minor Mistake
- 2 pts Minor Mistake
- 3 pts Major Mistake
- 6 pts Missing

2.5 Voltage in Thevenin Equivalent Circuit 6 / 6

- ✓ - 0 pts Correct
- 1 pts Minor Mistake
- 2 pts Minor Mistake
- 3 pts Major Mistake

2.6 Discussion 1 3 / 3

- ✓ - 0 pts Correct
- 1 pts Minor Mistake
- 2 pts Wrong Interpretation.
- 3 pts Missing

2.7 Discussion 2 3 / 3

- ✓ - 0 pts Correct
- 1 pts Minor Mistake
- 2 pts Wrong Interpretation
- 3 pts Missing

QUESTION 3

Wheatstone Bridge 20 pts

3.1 Sample Setup Image 1 / 1

- ✓ - 0 pts Correct
- 1 pts Missing

3.2 Theoretical Derivation of Output Voltage 6 / 6

- ✓ - 0 pts Correct
- 6 pts Incorrect
- 6 pts Missing
- 3 pts Partially wrong
- 2 pts Final ratio not given


3.3 Wheatstone Bridge Resistor Values 10 / 10

- ✓ - 0 pts Correct
- 2 pts Slightly incorrect
- 10 pts Missing
- 5 pts Partial answer
- 5 pts Partially incorrect
- 7 pts Major value mismatch
- 3 pts Values interchanged



3.4 Discussion 3 / 3

- ✓ - 0 pts Correct
- 2 pts Partially wrong
- 3 pts Missing
- 1 pts Minor mistake
- 1 pts Partial explanation

1. Superposition

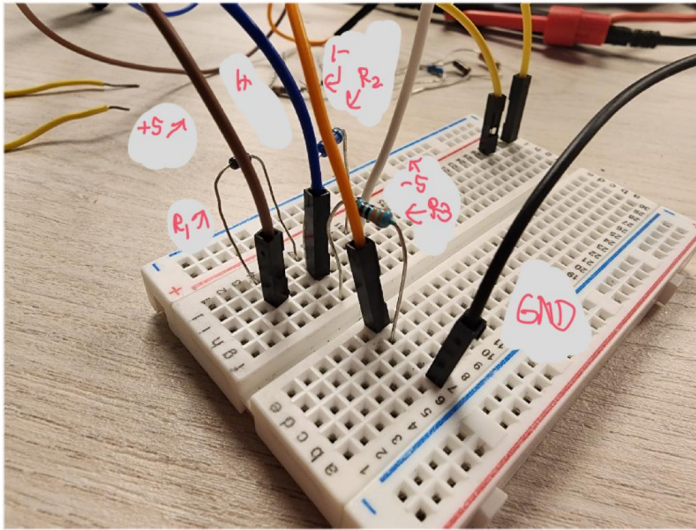

Theoretical Analysis:

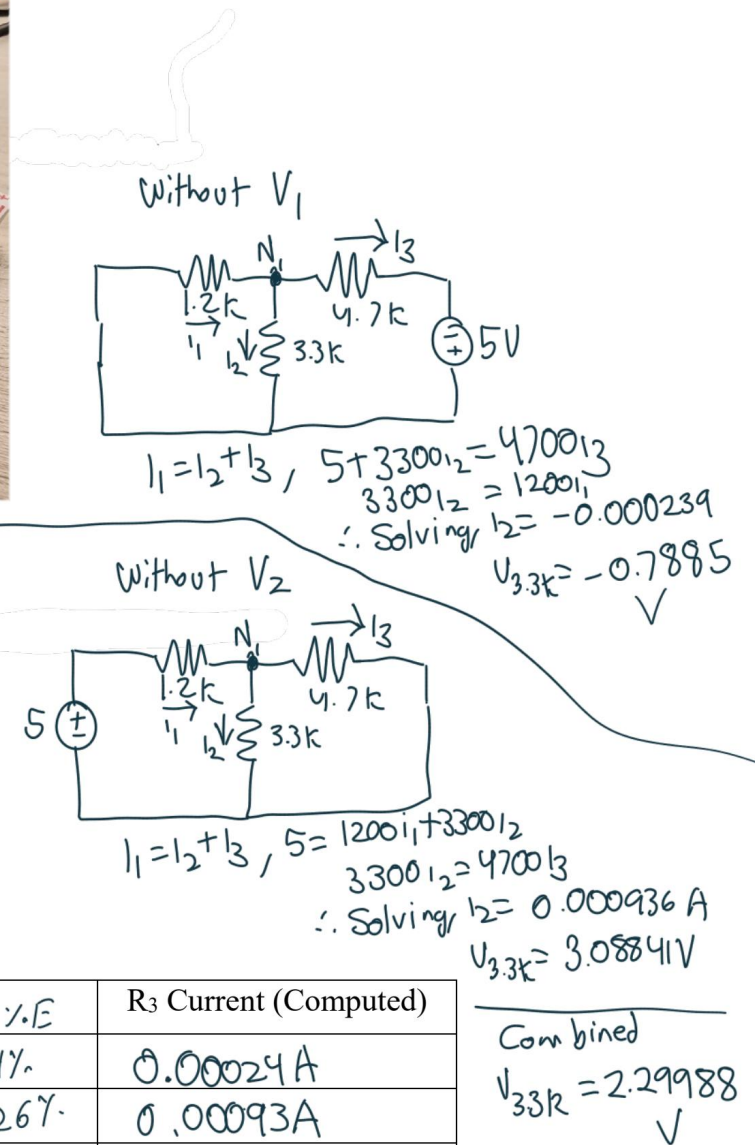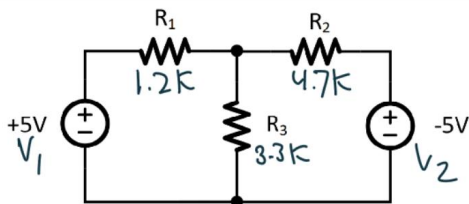

Observed Results:

Sources	R ₃ Voltage %E		R ₃ Current (Computed)
+5V only	-0.792V	.44%	0.00024 A
-5V only	3.08 V	.26%	0.00093 A
Sum of above	2.288V	.52%	0.00069 A
Both sources	2.296V	.35%	0.00070 A

Discussion


- How did the theoretical results compare with experimental values?

The theoretical values were all within $\pm 1\%$ thus showing that the experimental values hold with the theoretical values.



1.1 Sample Setup Image 1 / 1

✓ - 0 pts Correct

1. Superposition

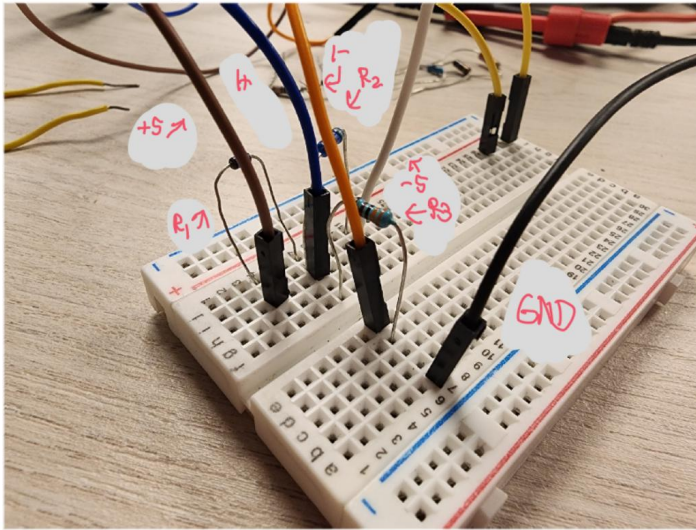

Theoretical Analysis:

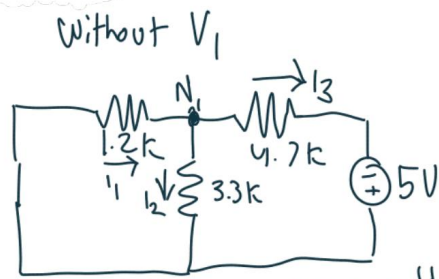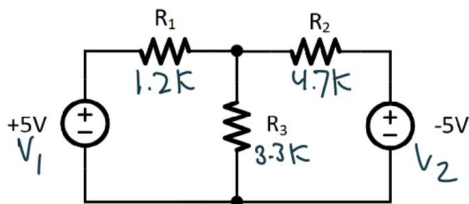


Without V_1

$$I_1 = I_2 + I_3, \quad 5 + 3300I_2 = 4700I_3$$

$$3300I_2 = 1200I_1$$

$$\therefore \text{Solving } I_2 = -0.000239$$

$$V_{3.3k} = -0.7885 \text{ V}$$

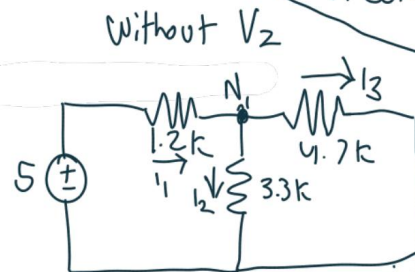

Without V_2

$$I_1 = I_2 + I_3, \quad 5 = 1200I_1 + 3300I_2$$

$$3300I_2 = 4700I_3$$

$$\therefore \text{Solving } I_2 = 0.000936 \text{ A}$$

$$V_{3.3k} = 3.08841 \text{ V}$$

Observed Results:

Sources	R ₃ Voltage %E		R ₃ Current (Computed)
+5V only	-0.792V	.44%	0.00024 A
-5V only	3.08 V	.26%	0.00093 A
Sum of above	2.288V	.52%	0.00069 A
Both sources	2.296V	.35%	0.00070 A

Combined

$$V_{3.3k} = 2.29988 \text{ V}$$

Discussion

- How did the theoretical results compare with experimental values?

The theoretical values were all within $\pm 1\%$ thus showing that the experimental values hold with the theoretical values.

1.2 Theoretical Analysis 5 / 5

✓ - **0 pts** *Correct*


- **4 pts** Incorrect Values

- **5 pts** Major analytical error



- **2 pts** Slightly incorrect

- **5 pts** Missing

1. Superposition

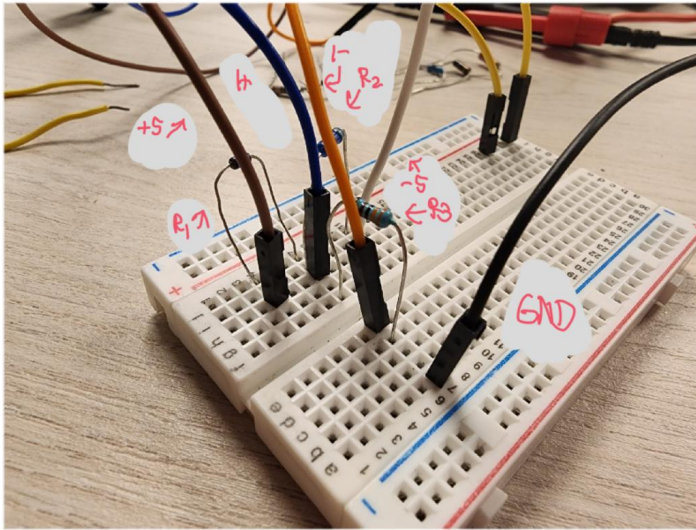

Theoretical Analysis:

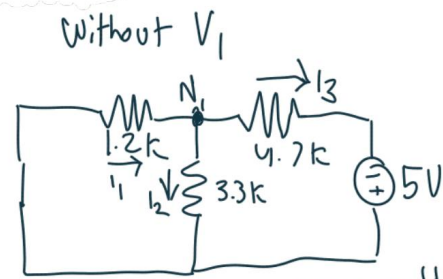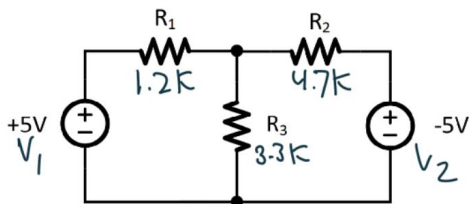


$$I_1 = I_2 + I_3, \quad 5 + 3300I_2 = 4700I_3$$

$$3300I_2 = 1200I_1$$

$$\therefore \text{Solving } I_2 = -0.000239$$

$$V_{3.3k} = -0.7885 \text{ V}$$

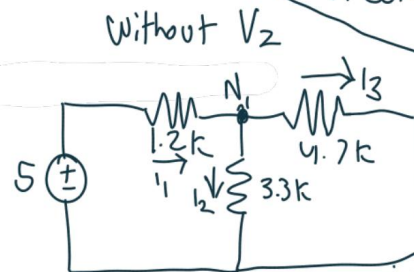

$$I_1 = I_2 + I_3, \quad 5 = 1200I_1 + 3300I_2$$

$$3300I_2 = 4700I_3$$

$$\therefore \text{Solving } I_2 = 0.000936 \text{ A}$$

$$V_{3.3k} = 3.08841 \text{ V}$$

Observed Results:

Sources	R ₃ Voltage %E		R ₃ Current (Computed)
+5V only	-0.792V	.44%	0.00024 A
-5V only	3.08 V	.26%	0.00093 A
Sum of above	2.288V	.52%	0.00069 A
Both sources	2.296V	.35%	0.00070 A

Combined

$$V_{3.3k} = 2.29988 \text{ V}$$

Discussion

- How did the theoretical results compare with experimental values?

The theoretical values were all within $\pm 1\%$ thus showing that the experimental values hold with the theoretical values.

1.3 Voltage and Current Measurement 5 / 6

✓ - 0 pts *Correct*

- 3 pts Partially Incorrect


- 6 pts Fully Incorrect

✓ - 1 pts *Small Mistake*



- 1 pts Multiple wrong values

💬 +5 and -5 values has been interchanged

1. Superposition

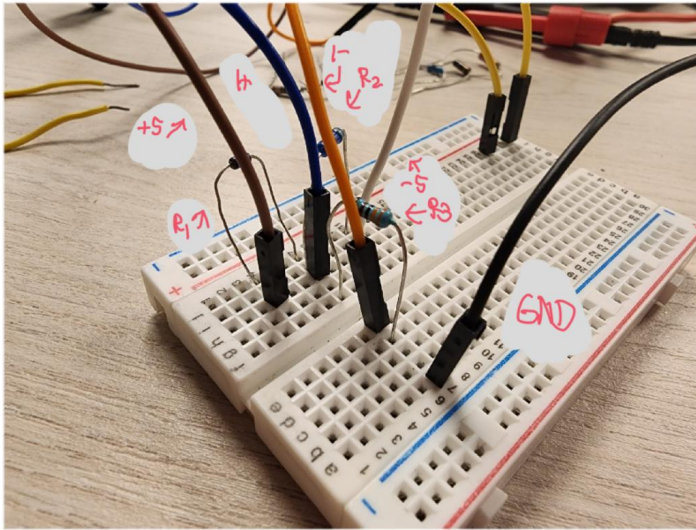

Theoretical Analysis:

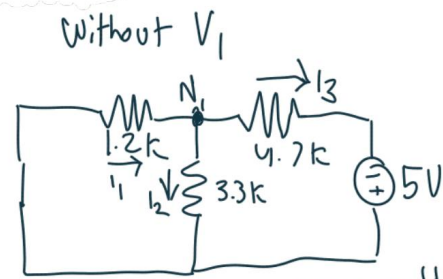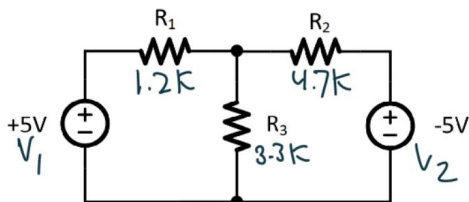


Without V_1

$$I_1 = I_2 + I_3, \quad 5 + 3300I_2 = 4700I_3$$

$$3300I_2 = 1200I_1$$

$$\therefore \text{Solving } I_2 = -0.000239$$

$$V_{3.3k} = -0.7885 \text{ V}$$

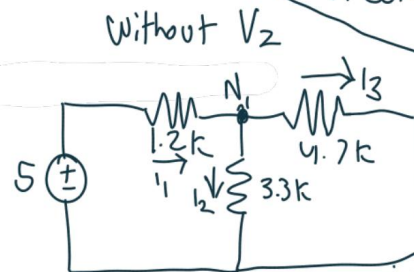

Without V_2

$$I_1 = I_2 + I_3, \quad 5 = 1200I_1 + 3300I_2$$

$$3300I_2 = 4700I_3$$

$$\therefore \text{Solving } I_2 = 0.000936 \text{ A}$$

$$V_{3.3k} = 3.08841 \text{ V}$$

Observed Results:

Sources	R ₃ Voltage %E		R ₃ Current (Computed)
+5V only	-0.792V	.44%	0.00024 A
-5V only	3.08 V	.26%	0.00093 A
Sum of above	2.288V	.52%	0.00069 A
Both sources	2.296V	.35%	0.00070 A

Combined

$$V_{3.3k} = 2.29988 \text{ V}$$

Discussion

- How did the theoretical results compare with experimental values?

The theoretical values were all within $\pm 1\%$ thus showing that the experimental values hold with the theoretical values.


1.4 Discussion 3 / 3

✓ - **0 pts** Correct

- **1 pts** Slightly incorrect

- **3 pts** Incorrect

2. Thevenin/Norton Equivalent


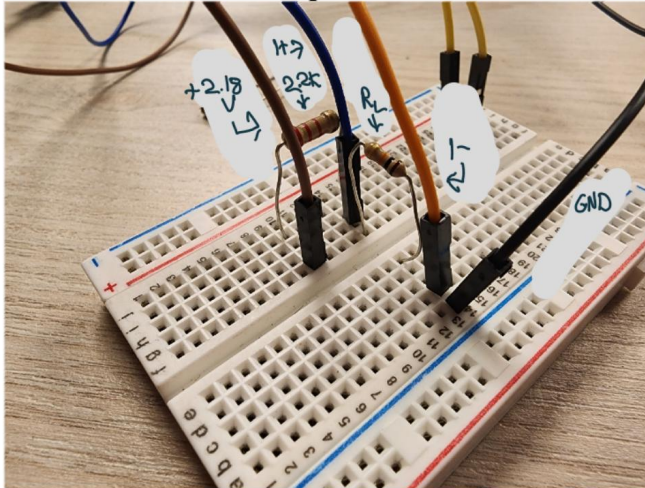


Impedance Measurement

Theoretical Resistance (Ω)	Measured Resistance (Ω)
$R_1 = 5.6k\Omega$	5601 Ω
$R_2 = 680\Omega$	67.5 Ω
$R_3 = 2.2k\Omega$	2164 Ω

Theoretical Analysis:

V_{TH} , V	I_N , mA	$R_{TH/N}$, Ω
2.18 V	0.000965A	2259.07 Ω

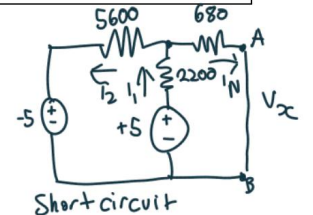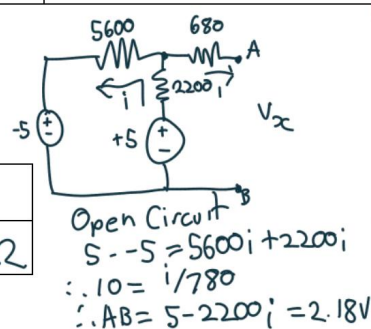

$$5 - 5 = 5600i_2 + 2200i_1$$

$$i_1 = i_2 + i_N$$

$$5 = 2200i_1 + 680i_N$$

Solving for i_N ,

$$I_N = 0.000965A$$

$$\therefore R_{eq} = \frac{V_{TH}}{I_N} = 2259.07\Omega$$


$\approx 2200\Omega$
which is what i will use

Practical Open Circuit Voltage, Equivalent Resistance in Original Circuit:

V_{OC} , V	I_{SC} , mA	R_{eq} , Ω
2.2 V	0.000983A	2238 Ω

Practical Observations in Thevenin Equivalent Circuit:

Voltage across Load Resistor	1.798V 1.789V
	E_q Original

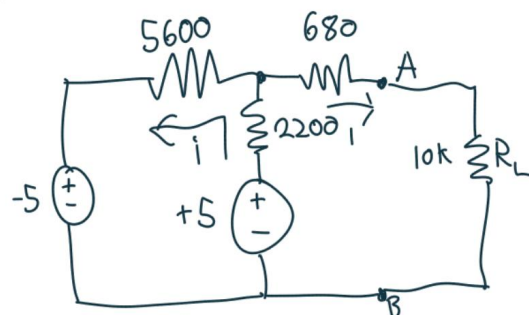


2.1 Sample Setup Image 1 / 1

✓ - **0 pts** *Correct*

- **1 pts** Image Missing

2. Thevenin/Norton Equivalent


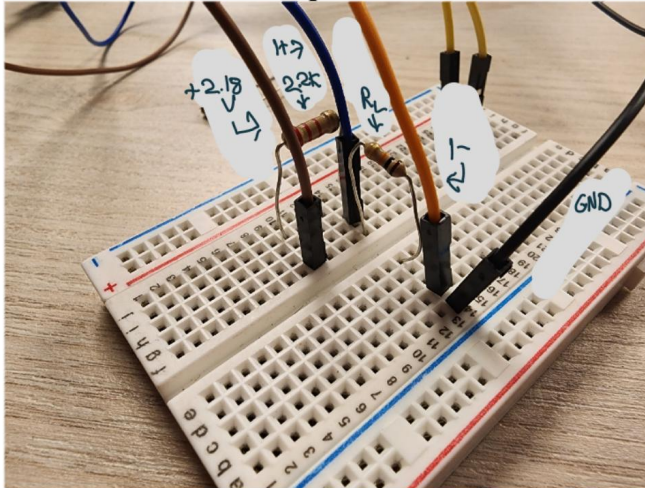


Impedance Measurement

Theoretical Resistance (Ω)	Measured Resistance (Ω)
$R_1 = 5.6k\Omega$	5601 Ω
$R_2 = 680\Omega$	67.5 Ω
$R_3 = 2.2k\Omega$	2164 Ω

Theoretical Analysis:

V_{TH} , V	I_N , mA	$R_{TH/N}$, Ω
2.18 V	0.000965A	2259.07 Ω

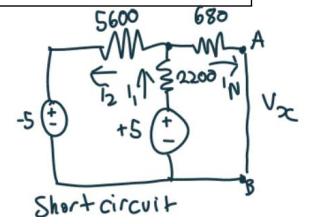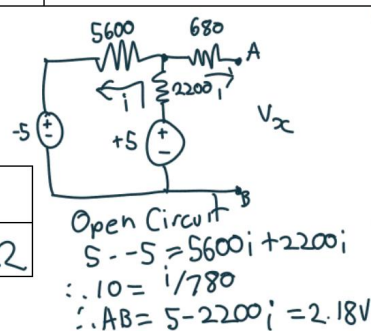

$$5 - 5 = 5600i_2 + 2200i_1$$

$$i_1 = i_2 + i_N$$

$$5 = 2200i_1 + 680i_N$$

Solving for i_N ,

$$I_N = 0.000965A$$

$$\therefore R_{eq} = \frac{V_{TH}}{I_N} = 2259.07\Omega$$


$\approx 2200\Omega$
which is what i will use

Practical Open Circuit Voltage, Equivalent Resistance in Original Circuit:

V_{OC} , V	I_{SC} , mA	R_{eq} , Ω
2.2 V	0.000983A	2238 Ω

Practical Observations in Thevenin Equivalent Circuit:

Voltage across Load Resistor	1.798V 1.789V
	E_q Original

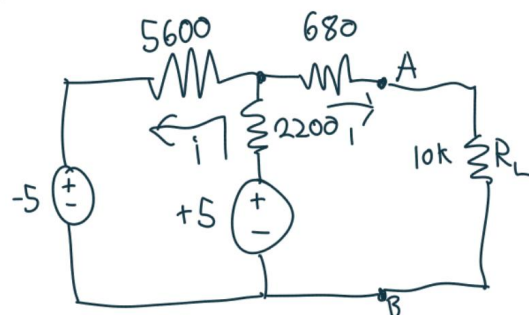


2.2 Impedance Measurement 5 / 5

✓ - **0 pts** *Correct*

- **1 pts** Minor Mistake

- **5 pts** Missing

2. Thevenin/Norton Equivalent


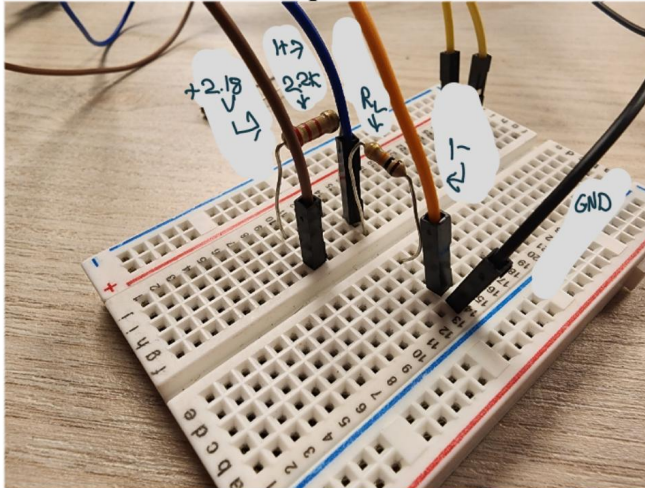


Impedance Measurement

Theoretical Resistance (Ω)	Measured Resistance (Ω)
$R_1 = 5.6k\Omega$	5601 Ω
$R_2 = 680\Omega$	67.5 Ω
$R_3 = 2.2k\Omega$	2164 Ω

Theoretical Analysis:

V_{TH} , V	I_N , mA	$R_{TH/N}$, Ω
2.18 V	0.000965A	2259.07 Ω

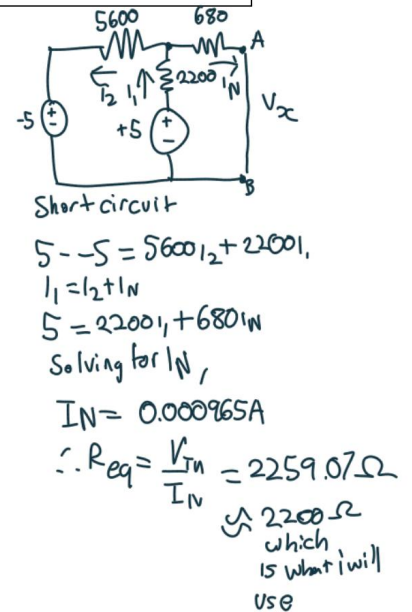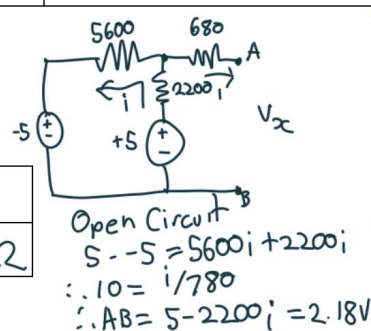


Practical Open Circuit Voltage, Equivalent Resistance in Original Circuit:

V_{OC} , V	I_{SC} , mA	R_{eq} , Ω
2.2 V	0.000983A	2238 Ω

Practical Observations in Thevenin Equivalent Circuit:

Voltage across Load Resistor	1.798V 1.789V
	E_q Original

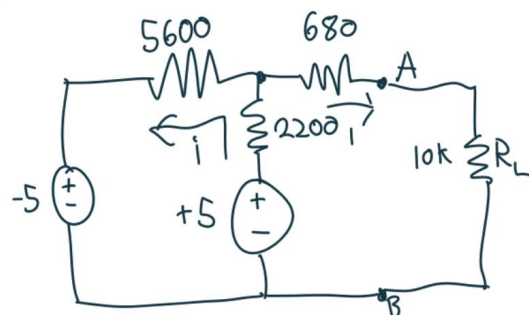

2.3 Theoretical Analysis 6 / 6

✓ - **0 pts** *Correct*


- **1 pts** Minor Mistake

- **2 pts** Minor Mistake

- **3 pts** Major Mistake

- **6 pts** Missing

2. Thevenin/Norton Equivalent


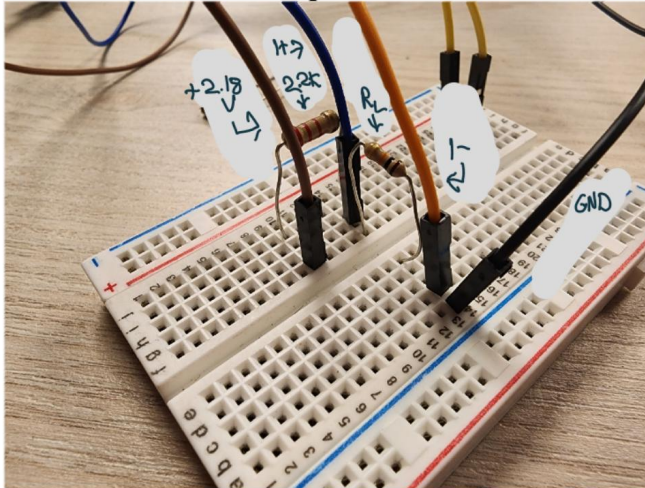


Impedance Measurement

Theoretical Resistance (Ω)	Measured Resistance (Ω)
$R_1 = 5.6k\Omega$	5601 Ω
$R_2 = 680\Omega$	67.5 Ω
$R_3 = 2.2k\Omega$	2164 Ω

Theoretical Analysis:

V_{TH} , V	I_N , mA	$R_{TH/N}$, Ω
2.18 V	0.000965A	2259.07 Ω

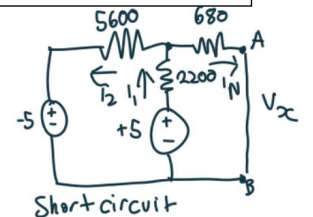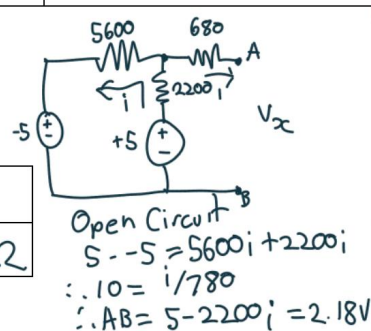

$$5 - 5 = 5600i_2 + 2200i_1$$

$$i_1 = i_2 + i_N$$

$$5 = 2200i_1 + 680i_N$$

Solving for i_N ,

$$I_N = 0.000965A$$

$$\therefore R_{eq} = \frac{V_{TH}}{I_N} = 2259.07\Omega$$


$\approx 2200\Omega$
which is what i will use

Practical Open Circuit Voltage, Equivalent Resistance in Original Circuit:

V_{OC} , V	I_{SC} , mA	R_{eq} , Ω
2.2 V	0.000983A	2238 Ω

Practical Observations in Thevenin Equivalent Circuit:

Voltage across Load Resistor	1.798V 1.789V
	E_q Original

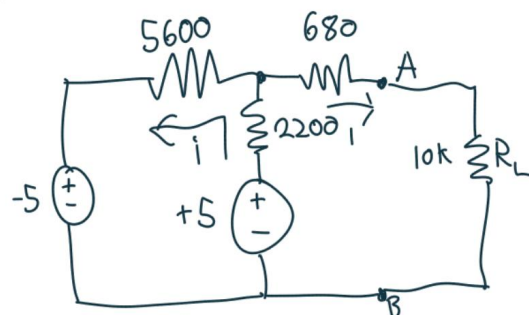

2.4 Voltage and Eq. Resistance in Original Circuit 6 / 6

✓ - **0 pts** Correct


- **1 pts** Minor Mistake

- **2 pts** Minor Mistake

- **3 pts** Major Mistake

- **6 pts** Missing

2. Thevenin/Norton Equivalent


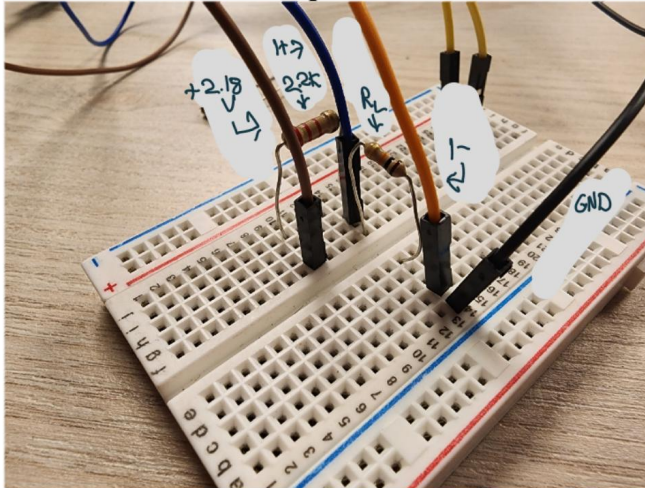


Impedance Measurement

Theoretical Resistance (Ω)	Measured Resistance (Ω)
$R_1 = 5.6k\Omega$	5601 Ω
$R_2 = 680\Omega$	67.5 Ω
$R_3 = 2.2k\Omega$	2164 Ω

Theoretical Analysis:

V_{TH} , V	I_N , mA	$R_{TH/N}$, Ω
2.18 V	0.000965A	2259.07 Ω

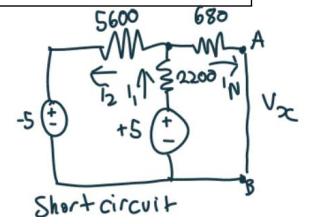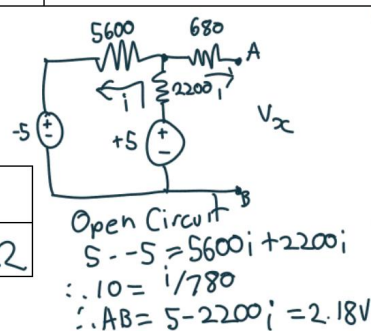

$$5 - 5 = 5600i_2 + 2200i_1$$

$$i_1 = i_2 + i_N$$

$$5 = 2200i_1 + 680i_N$$

Solving for i_N ,

$$I_N = 0.000965A$$

$$\therefore R_{eq} = \frac{V_{TH}}{I_N} = 2259.07\Omega$$


$\approx 2200\Omega$
which is what i will use

Practical Open Circuit Voltage, Equivalent Resistance in Original Circuit:

V_{OC} , V	I_{SC} , mA	R_{eq} , Ω
2.2 V	0.000983A	2238 Ω

Practical Observations in Thevenin Equivalent Circuit:

Voltage across Load Resistor	1.798V 1.789V
	E_q Original

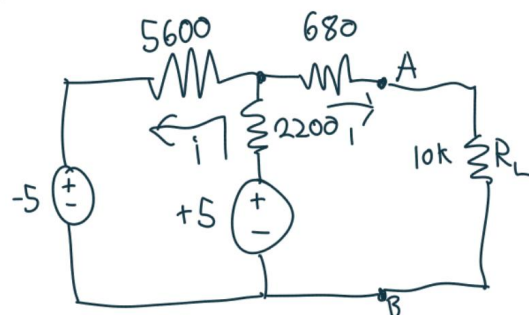

2.5 Voltage in Thevenin Equivalent Circuit 6 / 6

✓ - **0 pts** *Correct*

- **1 pts** Minor Mistake

- **2 pts** Minor Mistake

- **3 pts** Major Mistake

Discussion

- How did the voltage across the load compare between the original circuit and Thevenin equivalent circuit?

The original circuit had a V_{drop} of 1.789, vs the Thevenin Eq had a V_{drop} of 1.798V, this equates to a % Error of 0.5%, which is acceptable. Additionally, the theoretical Voltage Drop would equate to $\frac{2.18}{2200+10000} \cdot 10000 = 1.786V$

which is also within an acceptable tolerance.

- If our goal is to achieve maximum power dissipation across the load resistance, what load is the best choice? How does this value compare with the Thevenin equivalent resistance?

To achieve Power dissipation, we want to maximize $P = IV$. \therefore For a Load R_L ,

$$\text{Power} = \left(\frac{2.18}{2200 + R_L} \right) \cdot \left(\frac{2.18 R_L}{2200 + R_L} \right) = \left(\frac{2.18}{2200 + R_L} \right)^2 R_L$$

$$\therefore \text{Maximizing } R_L, R_L = 2200 = R_{eq}$$

\therefore To maximize the Power dissipation, use R_L such $R_L = R_{eq}$

2.6 Discussion 1 3 / 3

✓ - **0 pts** *Correct*

- **1 pts** Minor Mistake

- **2 pts** Wrong Interpretation.

- **3 pts** Missing

Discussion

- How did the voltage across the load compare between the original circuit and Thevenin equivalent circuit?

The original circuit had a V_{drop} of 1.789, vs the Thevenin Eq had a V_{drop} of 1.798V, this equates to a % Error of 0.5%, which is acceptable. Additionally, the theoretical Voltage Drop would equate to $\frac{2.18}{2200+10000} \cdot 10000 = 1.786V$

which is also within an acceptable tolerance.

- If our goal is to achieve maximum power dissipation across the load resistance, what load is the best choice? How does this value compare with the Thevenin equivalent resistance?

To achieve Power dissipation, we want to maximize $P = IV$. \therefore For a Load R_L ,

$$\text{Power} = \left(\frac{2.18}{2200 + R_L} \right) \cdot \left(\frac{2.18 R_L}{2200 + R_L} \right) = \left(\frac{2.18}{2200 + R_L} \right)^2 R_L$$

$$\therefore \text{Maximizing } R_L, R_L = 2200 = R_{eq}$$

\therefore To maximize the Power dissipation, use R_L such $R_L = R_{eq}$

2.7 Discussion 2 3 / 3


✓ - **0 pts** *Correct*

- **1 pts** Minor Mistake

- **2 pts** Wrong Interpretation

- **3 pts** Missing

3. Wheatstone Bridge

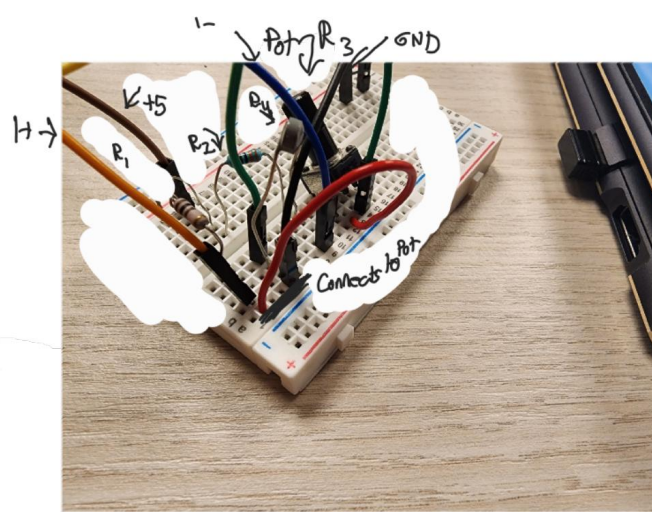

- Derive the expression for the voltage 'V' across Wheatstone bridge in terms of resistance values.

$V = C - D$

$$I_1 = \frac{V_S}{R_1 + R_3}$$

$$I_2 = \frac{V_S}{R_2 + R_4}$$

$$V_{R_1} = \frac{V_S}{R_1 + R_3} R_1 = V_S - \frac{V_S}{R_1 + R_3} R_3$$

$$V_{R_2} = \frac{V_S}{R_2 + R_4} R_2 = V_S - \frac{V_S}{R_2 + R_4} R_4$$

$$\therefore C = \frac{V_S R_3}{R_1 + R_3}$$

$$D = \frac{V_S R_4}{R_2 + R_4}$$

$$\therefore V = C - D = V_S \left(\frac{R_3}{R_1 + R_3} - \frac{R_4}{R_2 + R_4} \right)$$

$$V = 5 \left(\frac{R_3}{R_1 + R_3} - \frac{R_2}{R_2 + R_4} \right)$$

- What are the resistance values obtained for the Wheatstone bridge?

Potentiometer

$$R_1 = 5600 \, \Omega$$

$$R_2 = 3300 \, \Omega$$


$$R_3 = 1680 \, \Omega$$

3.1 Sample Setup Image 1 / 1

✓ - **0 pts** Correct

- **1 pts** Missing

3. Wheatstone Bridge

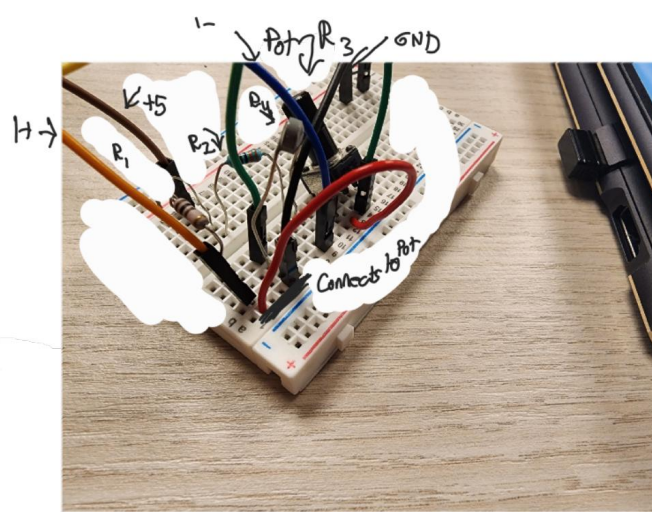

- Derive the expression for the voltage 'V' across Wheatstone bridge in terms of resistance values.

$V = C - D$

$$I_1 = \frac{V_S}{R_1 + R_3}$$

$$I_2 = \frac{V_S}{R_2 + R_4}$$

$$V_{R1} = \frac{V_S}{R_1 + R_3} R_1 = V_S - \frac{V_S}{R_1 + R_3} R_3$$

$$V_{R2} = \frac{V_S}{R_2 + R_4} R_2 = V_S - \frac{V_S}{R_2 + R_4} R_4$$

$$\therefore C = \frac{V_S R_3}{R_1 + R_3}$$

$$D = \frac{V_S R_4}{R_2 + R_4}$$

$$\therefore V = C - D = V_S \left(\frac{R_3}{R_1 + R_3} - \frac{R_4}{R_2 + R_4} \right)$$

$$V = 5 \left(\frac{R_3}{R_1 + R_3} - \frac{R_4}{R_2 + R_4} \right)$$

- What are the resistance values obtained for the Wheatstone bridge?

Potentiometer

$$R_1 = 5600 \, \Omega$$

$$R_2 = 3300 \, \Omega$$

$$R_3 = 1680 \, \Omega$$

3.2 Theoretical Derivation of Output Voltage 6 / 6

✓ - **0 pts** Correct


- **6 pts** Incorrect

- **6 pts** Missing

- **3 pts** Partially wrong

- **2 pts** Final ratio not given

3. Wheatstone Bridge

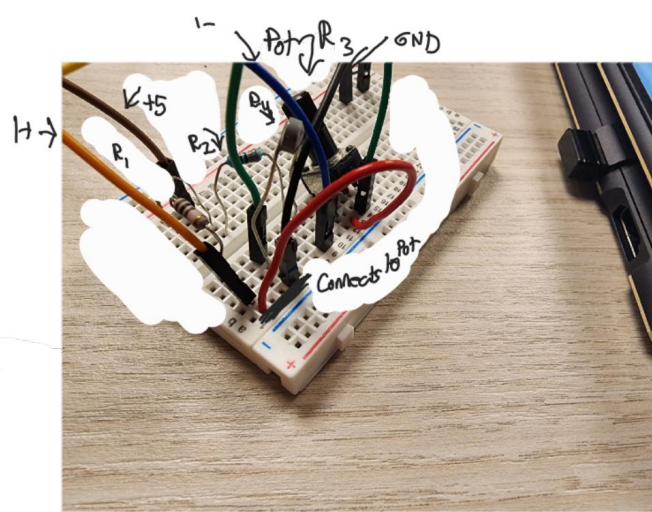

- Derive the expression for the voltage 'V' across Wheatstone bridge in terms of resistance values.

$V = C - D$

$$I_1 = \frac{V_S}{R_1 + R_3}$$

$$I_2 = \frac{V_S}{R_2 + R_4}$$

$$V_{R1} = \frac{V_S}{R_1 + R_3} R_1 = V_S - \frac{V_S}{R_1 + R_3} R_3$$

$$V_{R2} = \frac{V_S}{R_2 + R_4} R_2 = V_S - \frac{V_S}{R_2 + R_4} R_4$$

$$\therefore C = \frac{V_S R_3}{R_1 + R_3}$$

$$D = \frac{V_S R_4}{R_2 + R_4}$$

$$\therefore V = C - D = V_S \left(\frac{R_3}{R_1 + R_3} - \frac{R_4}{R_2 + R_4} \right)$$

$$V = 5 \left(\frac{R_3}{R_1 + R_3} - \frac{R_4}{R_2 + R_4} \right)$$

- What are the resistance values obtained for the Wheatstone bridge?

Potentiometer

$$R_1 = 5600 \, \Omega$$

$$R_2 = 3300 \, \Omega$$

$$R_3 = 1680 \, \Omega$$

3.3 Wheatstone Bridge Resistor Values 10 / 10

✓ - **0 pts** Correct

- **2 pts** Slightly incorrect

- **10 pts** Missing

- **5 pts** Partial answer

- **5 pts** Partially incorrect

- **7 pts** Major value mismatch

- **3 pts** Values interchanged

Discussion

- The light sensing circuit built earlier was susceptible to input voltage change, and was also biased away from zero. Both characteristics are not desirable in general. How does the temperature sensing circuit employing Wheatstone bridge compare?

For the V_{Drop} on a voltage divider to be near 0, the Ref voltage would need to be much larger than the R_{measured} . This is also bad, because if you calculate the error propagation, this will be much larger. On the other hand a Wheatstone bridge performs much better. The wheatstone bridge is not biased against 0. At its natural state it is @ 0, otherwise it increases or decreases the potential difference.

3.4 Discussion 3 / 3

✓ - **0 pts** *Correct*

- **2 pts** Partially wrong

- **3 pts** Missing

- **1 pts** Minor mistake

- **1 pts** Partial explanation

University of California, Los Angeles

School of Engineering and Applied Science

Department of Electrical and Computer Engineering

Name:

Sanjit Sarda

UID:

805964031

Experiment 2: Simple Resistive Networks

ECE11L Lab

Instructor: Sudhakar Pamarti