

23W-EC ENGR-10-LEC-1 Hw #1

SANJIT SARDA

TOTAL POINTS

48 / 50

QUESTION 1

1 Problem 1 5 / 5

✓ - 0 pts Correct

✓ - 0 pts Correct

3.5 (e) 3 / 3

✓ - 0 pts Correct

QUESTION 2

Problem 2 9 pts

3.6 (f) 4.5 / 5

✓ - 0.5 pts Partially Correct Explanation

2.1 (a) 1.5 / 3

✓ - 1.5 pts Wrong Sign

QUESTION 4

Problem 4 10 pts

2.2 (b) 3 / 3

✓ - 0 pts Correct

4.1 (a) 5 / 5

✓ - 0 pts Correct

2.3 (c) 3 / 3

✓ - 0 pts Correct

4.2 (b) 5 / 5

✓ - 0 pts Correct (based on answer in part a)

QUESTION 3

Problem 3 20 pts

QUESTION 5

5 Problem 5 6 / 6

3.1 (a) 3 / 3

✓ - 0 pts Correct

✓ - 0 pts Correct

3.2 (b) 3 / 3

✓ - 0 pts Correct

3.3 (c) 3 / 3


✓ - 0 pts Correct

3.4 (d) 3 / 3

$$1) \quad i(t) = \begin{cases} \frac{1}{2} e^{-5t}, & t \geq 6 \\ 0, & t < 6 \end{cases}$$

$$Q = \int_{-\infty}^{\infty} i(t) dt = \int_6^{\infty} \frac{1}{2} e^{-5t} dt + \int_{-\infty}^6 0 dt = -\frac{1}{10} e^{-5t} \Big|_6^{\infty} = 0 - \left(-\frac{1}{10} e^{-30}\right) = \boxed{\frac{e^{-30}}{10} \text{ C}}$$

2)

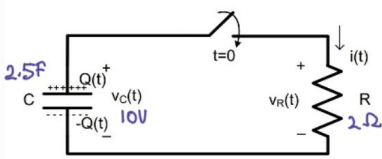

$$i(t_0) = 2 \text{ A}$$

$$i(t) = 5e^{-t/5} u(t) \longrightarrow \frac{2}{5} = e^{-t_0/5} \therefore \ln\left(\frac{2}{5}\right) = -\frac{t_0}{5} \therefore t_0 = -5 \ln\left(\frac{2}{5}\right) = 5 \ln\left(\frac{5}{2}\right)$$

$$a) \quad v_C(t) = \frac{Q(t)}{C} = \frac{1}{C} \int i dt$$

$$\therefore \frac{dv_C(t)}{dt} \Big|_{t=t_0} = \frac{i(t_0)}{C} = \frac{2}{2.5} = \boxed{\frac{4}{5} \text{ V s}^{-1}}$$



$$b) \quad v_R(t_0) = i(t_0) \cdot R = 2 \cdot 2 = \boxed{4 \text{ V}} \text{ Polarity: } AB = 4 \text{ V} \text{ \& } BA = -4 \text{ V}$$

$$c) \quad Q(t_0) = CV = 2.5 \text{ F} \cdot v_R(t_0) = 2.5 \text{ F} \cdot 4 \text{ V} = \boxed{10 \text{ C}}$$

$$\text{We also have } Q(t_0) = Q_0 - \int_{t_0}^{\infty} i dt = 25 \text{ C} - 15 \text{ C} = 10 \text{ C}$$


1 Problem 1 5 / 5

✓ - 0 pts Correct

$$1) \quad i(t) = \begin{cases} \frac{1}{2} e^{-5t}, & t \geq 6 \\ 0, & t < 6 \end{cases}$$

$$Q = \int_{-\infty}^{\infty} i(t) dt = \int_6^{\infty} \frac{1}{2} e^{-5t} dt + \int_{-\infty}^6 0 dt = -\frac{1}{10} e^{-5t} \Big|_6^{\infty} = 0 - \left(-\frac{1}{10} e^{-30}\right) = \boxed{\frac{e^{-30}}{10} \text{ C}}$$

2)

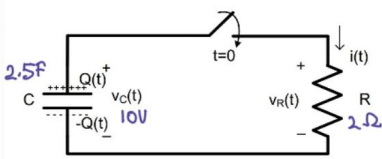

$$i(t_0) = 2 \text{ A}$$

$$i(t) = 5e^{-t/5} u(t) \longrightarrow \frac{2}{5} = e^{-t_0/5} \therefore \ln\left(\frac{2}{5}\right) = -\frac{t_0}{5} \therefore t_0 = -5 \ln\left(\frac{2}{5}\right) = 5 \ln\left(\frac{5}{2}\right)$$

$$a) \quad v_C(t) = \frac{Q(t)}{C} = \frac{1}{C} \int i dt$$

$$\therefore \frac{dv_C(t)}{dt} \Big|_{t=t_0} = \frac{i(t_0)}{C} = \frac{2}{2.5} = \boxed{\frac{4}{5} \text{ V s}^{-1}}$$



$$b) \quad v_R(t_0) = i(t_0) \cdot R = 2 \cdot 2 = \boxed{4 \text{ V}} \text{ Polarity: } AB = 4 \text{ V} \text{ \& } BA = -4 \text{ V}$$

$$c) \quad Q(t_0) = CV = 2.5 \text{ F} \cdot v_R(t_0) = 2.5 \text{ F} \cdot 4 \text{ V} = \boxed{10 \text{ C}}$$

$$\text{We also have } Q(t_0) = Q_0 - \int_{t_0}^{\infty} i dt = 25 \text{ C} - 15 \text{ C} = 10 \text{ C}$$


2.1 (a) 1.5 / 3

✓ - 1.5 pts *Wrong Sign*

$$1) \quad i(t) = \begin{cases} \frac{1}{2} e^{-5t}, & t \geq 6 \\ 0, & t < 6 \end{cases}$$

$$Q = \int_{-\infty}^{\infty} i(t) dt = \int_6^{\infty} \frac{1}{2} e^{-5t} dt + \int_{-\infty}^6 0 dt = -\frac{1}{10} e^{-5t} \Big|_6^{\infty} = 0 - \left(-\frac{1}{10} e^{-30}\right) = \boxed{\frac{e^{-30}}{10} \text{ C}}$$

2)

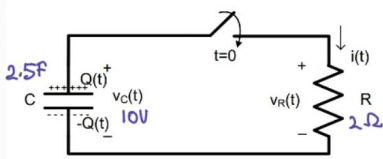

$$i(t_0) = 2 \text{ A}$$

$$i(t) = 5e^{-t/5} u(t) \longrightarrow \frac{2}{5} = e^{-t_0/5} \therefore \ln\left(\frac{2}{5}\right) = -\frac{t_0}{5} \therefore t_0 = -5 \ln\left(\frac{2}{5}\right) = 5 \ln\left(\frac{5}{2}\right)$$

$$a) \quad v_C(t) = \frac{Q(t)}{C} = \frac{1}{C} \int i dt$$

$$\therefore \frac{dv_C(t)}{dt} \Big|_{t=t_0} = \frac{i(t_0)}{C} = \frac{2}{2.5} = \boxed{\frac{4}{5} \text{ V s}^{-1}}$$



$$b) \quad v_R(t_0) = i(t_0) \cdot R = 2 \cdot 2 = \boxed{4 \text{ V}} \text{ Polarity: } AB = 4 \text{ V} \text{ \& } BA = -4 \text{ V}$$

$$c) \quad Q(t_0) = CV = 2.5 \text{ F} \cdot v_R(t_0) = 2.5 \text{ F} \cdot 4 \text{ V} = \boxed{10 \text{ C}}$$

$$\text{We also have } Q(t_0) = Q_0 - \int_{t_0}^{\infty} i dt = 25 \text{ C} - 15 \text{ C} = 10 \text{ C}$$


2.2 (b) 3 / 3

✓ - 0 pts Correct

$$1) \quad i(t) = \begin{cases} \frac{1}{2} e^{-5t}, & t \geq 6 \\ 0, & t < 6 \end{cases}$$

$$Q = \int_{-\infty}^{\infty} i(t) dt = \int_6^{\infty} \frac{1}{2} e^{-5t} dt + \int_{-\infty}^6 0 dt = -\frac{1}{10} e^{-5t} \Big|_6^{\infty} = 0 - \left(-\frac{1}{10} e^{-30}\right) = \boxed{\frac{e^{-30}}{10} \text{ C}}$$

2)

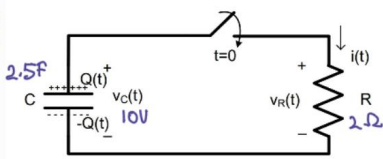

$$i(t_0) = 2 \text{ A}$$

$$i(t) = 5e^{-t/5} u(t) \longrightarrow \frac{2}{5} = e^{-t_0/5} \therefore \ln\left(\frac{2}{5}\right) = -\frac{t_0}{5} \therefore t_0 = -5 \ln\left(\frac{2}{5}\right) = 5 \ln\left(\frac{5}{2}\right)$$

$$a) \quad v_C(t) = \frac{Q(t)}{C} = \frac{1}{C} \int i dt$$

$$\therefore \frac{dv_C(t)}{dt} \Big|_{t=t_0} = \frac{i(t_0)}{C} = \frac{2}{2.5} = \boxed{\frac{4}{5} \text{ V s}^{-1}}$$



$$b) \quad v_R(t_0) = i(t_0) \cdot R = 2 \cdot 2 = \boxed{4 \text{ V}} \text{ Polarity: } AB = 4 \text{ V} \text{ \& } BA = -4 \text{ V}$$



$$c) \quad Q(t_0) = CV = 2.5 \text{ F} \cdot v_R(t_0) = 2.5 \text{ F} \cdot 4 \text{ V} = \boxed{10 \text{ C}}$$

$$\text{We also have } Q(t_0) = Q_0 - \int_{t_0}^{\infty} i dt = 25 \text{ C} - 15 \text{ C} = 10 \text{ C}$$

2.3 (c) 3 / 3

✓ - 0 pts Correct

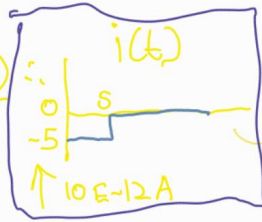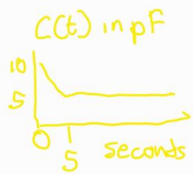3) Parallel Plate Capacitor to a 5V source



$$a) i(t) = \frac{dC(t) \cdot V(t)}{dt} = 5 \frac{dC}{dt}$$

$$b) E = \frac{1}{2} CV^2 = \frac{1}{2} \cdot 10 \text{ pF} \cdot (5V)^2 = 1.25 \times 10^{-10} \text{ joules}$$

$$c) E = \frac{1}{2} CV^2 = \frac{1}{2} \cdot 5 \text{ pF} \cdot (5V)^2 = 6.25 \times 10^{-11} \text{ joules}$$

$$d) \Delta E = E_f - E_i = (6.25 - 1.25) \times 10^{-10} \text{ joules} = -6.25 \times 10^{-11} \text{ joules}$$

Since change in Energy is negative Energy is being removed.

$$e) \Delta E_B = \int_0^5 V I dt = \int_0^5 5(+5 \times 10^{-12}) dt = 1.25 \times 10^{-10} \text{ joules}$$

\uparrow positive since work is done on the battery.

$$f) \Delta E_{\text{Battery}} = -\frac{1}{2} \Delta E_{\text{Cap}}$$


\therefore The battery is getting twice the amount of energy that is released from the capacitor.

This doesn't indicate energy is being conserved, since in this case energy seemingly is produced from thin air. However this may be a result of work done on the capacitor to bring the plates further away.

3.1 (a) 3 / 3

✓ - 0 pts Correct

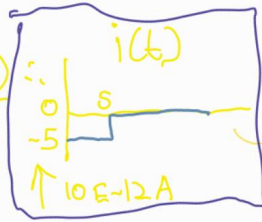3) Parallel Plate Capacitor to a 5V source



$$a) i(t) = \frac{dC(t) \cdot V(t)}{dt} = 5 \frac{dC}{dt}$$

$$b) E = \frac{1}{2} CV^2 = \frac{1}{2} \cdot 10 \text{ pF} \cdot (5V)^2 = 1.25 \times 10^{-10} \text{ joules}$$

$$c) E = \frac{1}{2} CV^2 = \frac{1}{2} \cdot 5 \text{ pF} \cdot (5V)^2 = 6.25 \times 10^{-11} \text{ joules}$$

$$d) \Delta E = E_f - E_i = (6.25 - 1.25) \times 10^{-10} \text{ joules} = -6.25 \times 10^{-11} \text{ joules}$$

Since change in Energy is negative Energy is being removed.

$$e) \Delta E_B = \int_0^5 V I dt = \int_0^5 5(+5 \times 10^{-12}) dt = 1.25 \times 10^{-10} \text{ joules}$$

\uparrow positive since work is done on the battery.

$$f) \Delta E_{\text{Battery}} = -\frac{1}{2} \Delta E_{\text{Cap}}$$



\therefore The battery is getting twice the amount of energy that is released from the capacitor.

This doesn't indicate energy is being conserved, since in this case energy seemingly is produced from thin air. However this may be a result of work done on the capacitor to bring the plates further away.

3.2 (b) 3 / 3

✓ - 0 pts Correct

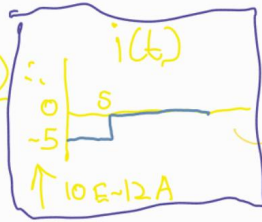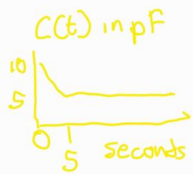3) Parallel Plate Capacitor to a 5V source



$$a) i(t) = \frac{dC(t) \cdot V(t)}{dt} = 5 \frac{dC}{dt}$$

$$b) E = \frac{1}{2} CV^2 = \frac{1}{2} \cdot 10 \text{ pF} \cdot (5V)^2 = 1.25 \times 10^{-10} \text{ joules}$$

$$c) E = \frac{1}{2} CV^2 = \frac{1}{2} \cdot 5 \text{ pF} \cdot (5V)^2 = 6.25 \times 10^{-11} \text{ joules}$$

$$d) \Delta E = E_f - E_i = (6.25 - 1.25) \times 10^{-10} \text{ joules} = -6.25 \times 10^{-11} \text{ joules}$$

Since change in Energy is negative Energy is being removed.

$$e) \Delta E_B = \int_0^5 V I dt = \int_0^5 5(+5 \times 10^{-12}) dt = 1.25 \times 10^{-10} \text{ joules}$$

\uparrow positive since work is done on the battery.

$$f) \Delta E_{\text{Battery}} = -\frac{1}{2} \Delta E_{\text{Cap}}$$


\therefore The battery is getting twice the amount of energy that is released from the capacitor.

This doesn't indicate energy is being conserved, since in this case energy seemingly is produced from thin air. However this may be a result of work done on the capacitor to bring the plates further away.

3.3 (c) 3 / 3

✓ - 0 pts Correct

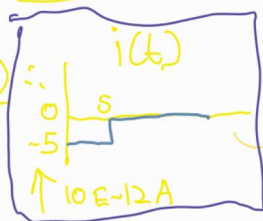3) Parallel Plate Capacitor to a 5V source



$$a) i(t) = \frac{dC(t) \cdot V(t)}{dt}$$

$$= 5 \frac{dC}{dt}$$

$$b) E = \frac{1}{2} CV^2 = \frac{1}{2} \cdot 10 \text{ pF} \cdot (5V)^2 = 1.25 \text{ E-10 joules.}$$

$$c) E = \frac{1}{2} CV^2 = \frac{1}{2} \cdot 5 \text{ pF} \cdot (5V)^2 = 6.25 \text{ E-11 joules.}$$

$$d) \Delta E = E_f - E_i = (6.25 - 1.25) \text{ E-10 joules} = -6.25 \text{ E-11 joules}$$

Since change in Energy is negative Energy is being removed.

$$e) \Delta E_B = \int_0^5 V I dt = \int_0^5 5(+5E-12) dt = 1.25 \text{ E-10 joules}$$

positive since work is done on the battery.

$$f) \Delta E_{\text{Battery}} = -\frac{1}{2} \Delta E_{\text{Cap}}$$



∴ The battery is getting twice the amount of energy that is released from the capacitor.

This doesn't indicate energy is being conserved, since in this case energy seemingly is produced from thin air. However this may be a result of work done on the capacitor to bring the plates further away.

3.4(d) 3 / 3

✓ - 0 pts Correct

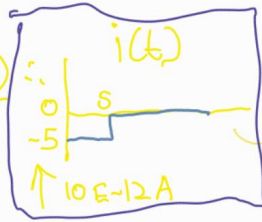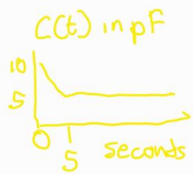3) Parallel Plate Capacitor to a 5V source



$$\begin{aligned} a) i(t) &= \frac{dC(t) \cdot V(t)}{dt} \\ &= 5 \frac{dC}{dt} \end{aligned}$$

$$b) E = \frac{1}{2} CV^2 = \frac{1}{2} \cdot 10 \text{ pF} \cdot (5V)^2 = 1.25 \text{ E-10 joules.}$$

$$c) E = \frac{1}{2} CV^2 = \frac{1}{2} \cdot 5 \text{ pF} \cdot (5V)^2 = 6.25 \text{ E-11 joules.}$$

$$d) \Delta E = E_f - E_i = (6.25 - 1.25) \text{ E-10 joules} = -6.25 \text{ E-11 joules}$$

Since change in Energy is negative Energy is being removed.

$$e) \Delta E_B = \int_0^5 V I dt = \int_0^5 5(+5 \text{ E-12}) dt = 1.25 \text{ E-10 joules}$$

positive since work is done on the battery.

$$f) \Delta E_{\text{Battery}} = -\frac{1}{2} \Delta E_{\text{Cap}}$$


∴ The battery is getting twice the amount of energy that is released from the capacitor.

This doesn't indicate energy is being conserved, since in this case energy seemingly is produced from thin air. However this may be a result of work done on the capacitor to bring the plates further away.

3.5 (e) 3 / 3

✓ - 0 pts Correct

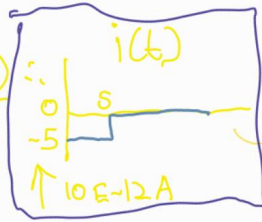3) Parallel Plate Capacitor to a 5V source



$$a) i(t) = \frac{dC(t) \cdot V(t)}{dt} = 5 \frac{dC}{dt}$$

$$b) E = \frac{1}{2} CV^2 = \frac{1}{2} \cdot 10 \text{ pF} \cdot (5V)^2 = 1.25 \text{ E-10 joules.}$$

$$c) E = \frac{1}{2} CV^2 = \frac{1}{2} \cdot 5 \text{ pF} \cdot (5V)^2 = 6.25 \text{ E-11 joules.}$$

$$d) \Delta E = E_f - E_i = (6.25 - 1.25) \text{ E-10 joules} = 5 \text{ E-10 joules}$$

Since change in Energy is negative Energy is being removed.

$$e) \Delta E_B = \int_0^5 V I dt = \int_0^5 5(+5 \text{ E-12}) dt = 1.25 \text{ E-10 joules}$$

positive since work is done on the battery.

$$f) \Delta E_{\text{Battery}} = -\frac{1}{2} \Delta E_{\text{Cap}}$$


∴ The battery is getting twice the amount of energy that is released from the capacitor.

This doesn't indicate energy is being conserved, since in this case energy seemingly is produced from thin air. However this may be a result of work done on the capacitor to bring the plates further away.

3.6 (f) 4.5 / 5

✓ - 0.5 pts Partially Correct Explanation

9)

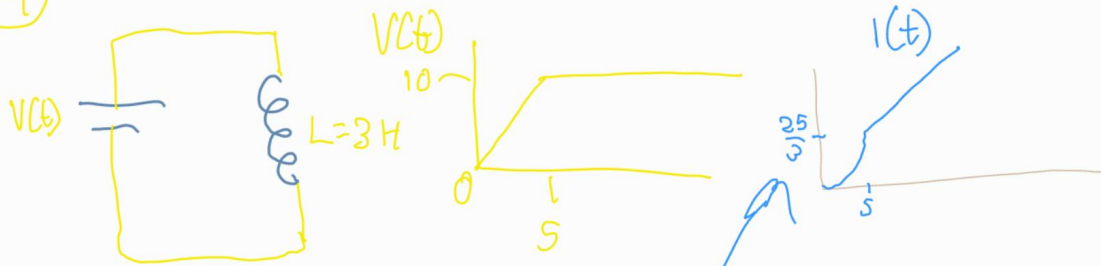


$$a) v(t) = L \frac{di}{dt} \quad \therefore \frac{1}{L} v(t) dt = di \therefore i(t) = \frac{1}{3} \int v(t) dt = \begin{cases} \frac{t^2}{3}, & 0 \leq t < 5 \\ \frac{10t-25}{3}, & 5 \leq t \end{cases}$$

$$b) E = \frac{1}{2} L I^2 = \begin{cases} \frac{t^4}{6}, & 0 \leq t < 5 \\ \frac{100t^2 - 500t + 625}{6}, & 5 \leq t \end{cases}$$

4.1 (a) 5 / 5

✓ - 0 pts Correct

9)

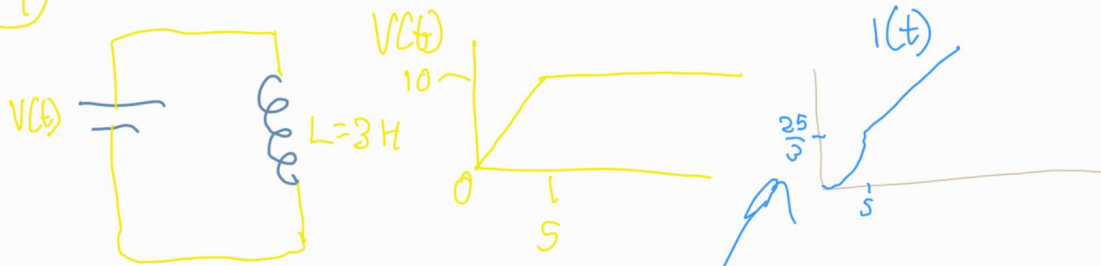


$$a) v(t) = L \frac{di}{dt} \quad \therefore \frac{1}{L} v(t) dt = di \therefore i(t) = \frac{1}{3} \int v(t) dt = \begin{cases} \frac{t^2}{3}, & 0 \leq t < 5 \\ \frac{10t-25}{3}, & 5 \leq t \end{cases}$$

$$b) E = \frac{1}{2} L I^2 = \begin{cases} \frac{t^4}{6}, & 0 \leq t < 5 \\ \frac{100t^2 - 500t + 625}{6}, & 5 \leq t \end{cases}$$

4.2 (b) 5 / 5

✓ - 0 pts Correct (based on answer in part a)

5)

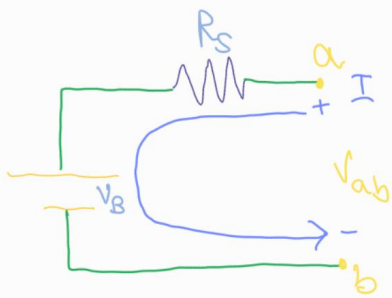

$$V = IR$$

$$V_{RS} = -I \cdot R_S$$

$$V_B = V_{ab} + V_{RS} \quad \therefore V_{ab} = V_B + IR_S$$

Since current is going against V_{ab}

$$Q = CV$$

$$I = C \frac{dV}{dt}$$

$$Q = \int I dt$$

$$= C \frac{dV}{dt}$$

$$I = C \frac{dV}{dt}$$

$$\int I dt = C \int dV$$

5 Problem 5 6 / 6

✓ - 0 pts Correct

