

ECE 10, Winter 2023, Midterm #2 – March 2, 2022

Instructions: This exam booklet consists of four problems, blank sheets for the solutions, reference sheets with mathematical identities, and additional blank sheets. Please follow these instructions while answering your exam:

1. Write your name and student identification number below.
2. Write the names of students to your left and right as well.
3. You have 1 hour 45 minutes to finish your exam.
4. Write your solutions in the provided blank sheets after each problem.
5. The sheets marked "Scratch..." will NOT be graded. These sheets are provided for your rough calculations only.
6. Write your solutions clearly. Put a box around your final answer. Illegible solutions will not be graded.
7. Be brief.
8. Open book & open notes only. NO homework solutions allowed!
9. Regular, scientific, and graphing calculators are allowed.

NAME: Sanjit Sarda

STUDENT ID: 805964031

NAMES OF ADJACENT STUDENTS:

LEFT: Inesh Chakrabarti

RIGHT: 

Problem	Score
#1	7 / 8
#2	16 / 12
#3	5 / 10
#4	10 / 20
Total	32 / 50

Problem 1: Assume that the circuit shown in Figure 1 has reached steady state i.e. it has existed in this form for a very long time. Given $R_1 = 1 \text{ k}\Omega$, $R_2 = 4 \text{ k}\Omega$, $L = 1 \text{ nH}$, $C_1 = 1 \text{ nF}$, $C_2 = 1 \text{ nF}$, and $V_B = 3 \text{ V}$, calculate the steady state values of $v_{C1}(t)$ and $i_L(t)$.


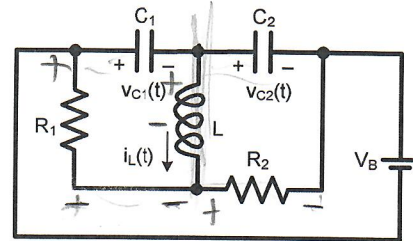
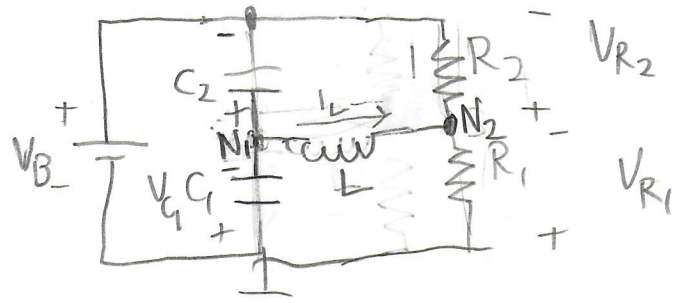


Figure 1.

(4 + 4 = 8 points)

Solution:

Redrawn

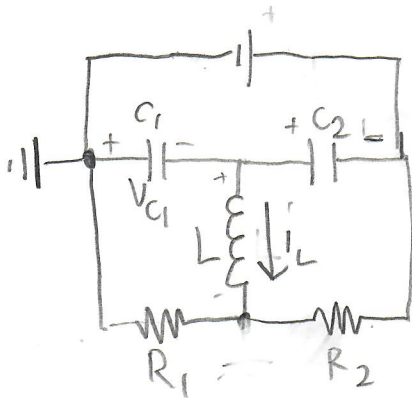

$$V_{R2} = I_{R2} R_2$$

$$V_{R1} = I_{R1} R_1$$

$$I_L + I_{R2} = I_{R1}$$

$$V_{C2} - V_{R2} - L \frac{di_L}{dt} = 0$$

$$V_{C1} + L \frac{di_L}{dt} - V_{R1} = 0$$

$$V_{C1} + V_{C2} - I_{R2} R_2 - I_{R1} R_1 = 0$$

@ Steady State, $\frac{di_L}{dt} = 0$

$$\therefore V_{C1} = V_{R1}$$

@ Steady State

@ Steady State

$$V_{C1} = V_{R1} \quad V_B = -V_{R2} - V_{R1}$$

$$V_{C2} = V_{R2} \quad V_B = -V_{C2} - V_{C1}$$

$$I_L + \frac{V_{C1}}{R_1} = \frac{V_{C2}}{R_2}$$

$$V_B = -V_{C1} - V_{C2}$$

$$V_{C1}(t) = \frac{V_B \cdot R_1}{R_1 + R_2} = -\frac{3}{5} \text{ V}$$

$$I_L(t) = 0$$

Problem 2: Consider the circuit shown in Figure 2. Assume that the inductors have no stored energy prior to $t = 0$. Assume also that $I_B = 4\text{mA}$, $R_1 = 2\text{k}\Omega$, $R_2 = 6\text{k}\Omega$, $L_1 = 4\text{mH}$, and $L_2 = 2\text{mH}$.

- Show that this is a 1st order circuit.
- What is the time constant of this circuit?
- Derive an expression for $i_1(t)$ valid for $t \geq 0$.

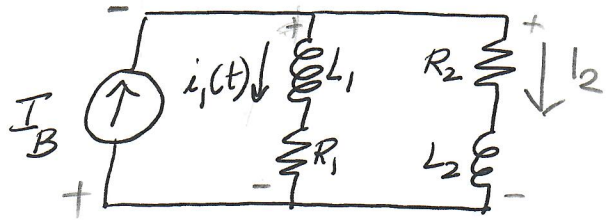


Figure 2.

(4 + 3 + 5 = 12 points)

Solution:

$$I_B = i_1 + i_2 \quad \therefore i_2 = I_B - i_1$$

$$\textcircled{a} L_1 i_1' + R_1 i_1 = L_2 i_2' + R_2 i_2$$

$$\therefore L_1 i_1' + R_1 i_1 = L_2 (I_B - i_1)' + R_2 (I_B - i_1)$$

$$\therefore L_1 i_1' + R_1 i_1 = -L_2 i_1' + R_2 I_B - I_1 R_2$$

$$\textcircled{a} \therefore (L_1 + L_2) i_1' + (R_1 + R_2) i_1 = R_2 I_B \quad \therefore \text{this is a 1st order circuit}$$

$$\therefore i_1' + \frac{(R_1 + R_2)}{(L_1 + L_2)} i_1 = \frac{R_2}{L_1 + L_2} I_B \quad \left| \quad i_1' + \frac{(7.5 \text{E-} 7)}{7.5 \text{E-} 7} i_1 = 40009 \right.$$

$$\text{Homogenized: } i_1' + \frac{R_1 + R_2}{L_1 + L_2} i_1 = 0$$

$$\textcircled{b} \therefore \tau = \frac{L_1 + L_2}{R_1 + R_2} = \frac{4\text{mH} + 2\text{mH}}{2\text{k}\Omega + 6\text{k}\Omega} = \frac{3\text{mH}}{4\text{k}\Omega} = \frac{3}{4} \text{E-} 6 \text{ s} = 7.5 \text{E-} 7 \text{ s}$$

$$\therefore i(t) = C_1 e^{-t/(7.5 \text{E-} 7)} + \frac{3}{1000}$$

$$i(0^+) = i(0^-) = 0 \quad \therefore 0 = C_1 + \frac{3}{1000} \quad \therefore C_1 = -\frac{3}{1000}$$

$$\textcircled{c} \therefore i_1(t) = \frac{3}{1000} (1 - e^{-t/(7.5 \text{E-} 7)})$$

Problem 3: Refer to the circuit in Figure 3. Assume that $V_B = 3V$, $I_B = 4mA$, $R = 1k\Omega$, $L_1 = 1mH$, and $L_2 = 2mH$.

- (a) Calculate the value of $i_1(t)$ at $t = 0^-$.
 (b) Calculate the value of $i_1(t)$ at $t = 0^+$.

(3 + 7 = 10 points)

Solution:

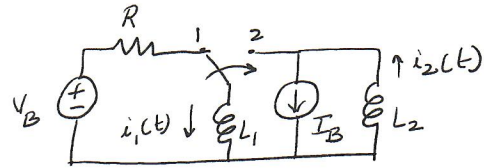


Figure 3.

(a) $@ t < 0^-$

$@ \text{ steady state: } i_1(0^-) = \frac{V_B}{R} = \frac{3}{1000} \text{ A}$

$V_{L_1} = L_1 i_1'$

$i_1' = 0 \therefore V_{L_1} = 0 \therefore V_B - i_1 R - V_{L_1} = 0$

$\therefore V_B = i_1 R \therefore i_1 = \frac{V_B}{R}$

(b) $i_1(0^-) = \frac{V_B}{R} = \frac{3}{1000} \text{ A}$ & $i_2(0^-) = I_B$

$i_2(0^+) = I_B$

$@ t > 0$

$i_2 = I_B + i_1$

$L_1 i_1' = -L_2 i_2'$

$i_1(0^+) = -\frac{L_2}{L_1} i_2(0^+) + i_1(0^-) = 1.4 \text{ mA} + \frac{3}{1000} \text{ A}$

$\times \uparrow = 7 \text{ mA}$

$i_1' = -\frac{L_2}{L_1} i_2' \therefore i_1(t) = -\frac{L_2}{L_1} \int_0^t i_2'(\tau) d\tau + i_1(0^+) = i_1(0^+) - \frac{L_2}{L_1} \int_0^t i_2(\tau) d\tau = i_1(0^+) - \frac{L_2}{L_1} i_2(t)$

$$C V_C' + \frac{V_C}{R} = I_L \quad \hookrightarrow \quad \frac{I_L - \frac{V_C}{R}}{C} = V_C'$$

$$\therefore V_C'(0) = \frac{4 \text{ mA}}{1 \text{ nF}} - \frac{5 \text{ V}}{(2500)(2 \text{ nF})}$$

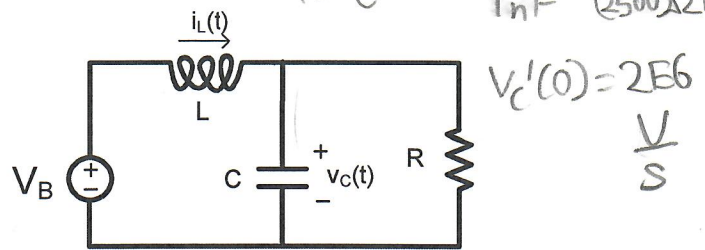


Figure 4.

Problem 3: Refer to the circuit in Figure 4. Assume that $V_B = 2\text{V}$, $L = 16\text{mH}$, $C = 1\text{nF}$, $R = 2500\text{ Ohms}$, $v_C(0+) = 5\text{V}$, and $i_L(0+) = 4\text{mA}$.

- Derive a differential equation in terms of $V_C(t)$ to show that this is a 2nd order circuit.
- Is this circuit overdamped or underdamped? Give numerical reasons.
- Derive an expression for the total solution of $V_C(t)$.
- Should you increase or decrease the value of R to make the circuit critically damped? Explain.

(4 + 3 + 10 + 3 = 20 points)

Solution:

$$I_L = C V_C' + \frac{V_C}{R} \quad \therefore I_L' = C V_C'' + \frac{V_C'}{R}$$

$$V_B - V_C = L I_L'$$

$$\therefore V_B - V_C = L C V_C'' + \frac{L}{R} V_C'$$

$$\textcircled{a} \therefore V_C'' + \frac{V_C'}{RC} + \frac{V_C}{LC} = \frac{V_B}{L} \quad \checkmark \quad \text{Second order}$$

$$\therefore V_C'' + 400000 V_C' + (6.25 \times 10^{10}) V_C = 2, \quad V_C(0+) = 5\text{V}, \quad V_C'(0+) = 2 \times 10^6 \frac{\text{V}}{\text{s}}$$

$$\omega_0 = \sqrt{1/LC}$$

$$= \sqrt{1.6 \times 10^{11}}$$

$$= \sqrt{16 \times 10^{12}}$$

$$= 4 \times 10^6$$

$$= 2 \times 10^6 \quad \times!$$

$$2\beta\omega_0 = 400000$$

$$\therefore \beta = 400000 \times \frac{1}{2} = \frac{1}{2 \times 10^6}$$

$$\beta = 0.125$$

$$\textcircled{b} \quad \beta < 1 \quad \therefore \text{Underdamped}$$

$$\textcircled{c} \quad V_C(t) = C_1 e^{-200000t} \cos(1500000t) + C_2 e^{-200000t} \sin(1500000t) + 3.2 \times 10^{-11}$$

$$C_1 = 5 - 3.2 \times 10^{-11} \approx 5$$

$$C_2 = 20 - 3.2 \times 10^{-11} \approx 20$$

$$\therefore V_C(t) = 5 e^{-200000t} \cos(1500000t) + 20 e^{-200000t} \sin(1500000t) + 3.2 \times 10^{-11}$$

$$\textcircled{d} \quad \text{For Crit damped, } \beta = 1 \quad \therefore \frac{1}{RC} = 2\beta \cdot (2 \times 10^6) \quad \therefore R = \frac{1}{C \cdot 2 \cdot (2 \times 10^6)}$$

$$\therefore R = 250 \quad \leftarrow \text{Since } 250 < 2500$$

$$\therefore \text{We need to decrease}$$

Reference Sheet #1

Trigonometric Identities:

$$\sin A = \cos(A - 90^\circ) = \cos(A - \pi/2)$$

$$\cos A = \sin(A + 90^\circ) = \sin(A + \pi/2)$$

$$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$$

$$\sin(A \pm B) = \cos A \cos B \pm \sin A \sin B$$

$$\cos A + \cos B = 2 \cos((A+B)/2) \cos((A-B)/2)$$

$$\cos A - \cos B = -2 \sin((A+B)/2) \sin((A-B)/2)$$

$$\sin A + \sin B = 2 \sin((A+B)/2) \cos((A-B)/2)$$

$$\sin A - \sin B = 2 \cos((A+B)/2) \sin((A-B)/2)$$

$$\cos 2A = 2 \cos^2 A - 1 = \cos^2 A - \sin^2 A = 1 - 2 \sin^2 A$$

$$\sin 2A = 2 \sin A \cos A$$

$$\cos 3A = 4 \cos^3 A - 3 \cos A$$

$$\sin 3A = 3 \sin A - 4 \sin^3 A$$

$$a \cos A + b \sin A = \sqrt{a^2 + b^2} \cos(A - \tan^{-1}(b/a))$$

Complex Arithmetic:

$$\operatorname{Re}\{z_1 \pm z_2\} = \operatorname{Re}\{z_1\} \pm \operatorname{Re}\{z_2\}$$

$$\operatorname{Im}\{z_1 \pm z_2\} = \operatorname{Im}\{z_1\} \pm \operatorname{Im}\{z_2\}$$

$$\operatorname{Re}\{z_1 z_2\} = \operatorname{Re}\{z_1\} \operatorname{Re}\{z_2\} - \operatorname{Im}\{z_1\} \operatorname{Im}\{z_2\}$$

$$\operatorname{Im}\{z_1 z_2\} = \operatorname{Re}\{z_1\} \operatorname{Im}\{z_2\} + \operatorname{Im}\{z_1\} \operatorname{Re}\{z_2\}$$

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$x + jy = re^{j\theta} \text{ where } r = \sqrt{x^2 + y^2}, \theta = \tan^{-1}(y/x)$$

$$re^{j\theta} = x + jy \text{ where } x = r \cos \theta, y = r \sin \theta$$

$$|z_1 z_2| = |z_1| |z_2|, \text{ angle}(z_1 z_2) = \text{angle}(z_1) + \text{angle}(z_2)$$

$$|1/z| = 1/|z|, \text{ angle}(1/z) = -\text{angle}(z)$$

$$(x + jy)^* = x - jy, \text{ angle}(z^*) = -\text{angle}(z)$$

Quadratic Equations:

$$\text{The roots of } ax^2 + bx + c = 0 \text{ are } x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

SCRATCH (Will NOT Be Graded)

SCRATCH (Will NOT Be Graded)