

23S-EC ENGR-3-LEC-1 Homework 1

SANJIT SARDA

TOTAL POINTS

97 / 100

QUESTION 1

Q1 70 pts

1.1 a 10 / 10

✓ - 0 pts Correct

- 3 pts Minor mistake

- 6 pts Major mistake

- 10 pts Incorrect

1.2 b 10 / 10

✓ - 0 pts Correct

- 1 pts Same mistake

- 3 pts Minor mistake

- 10 pts Incorrect

1.3 c 10 / 10

✓ - 0 pts Correct

- 1 pts Same mistake

- 3 pts Minor mistake

- 10 pts Incorrect

1.4 d 10 / 10

✓ - 0 pts Correct

- 1 pts Same mistake

- 3 pts Minor mistake

- 10 pts Incorrect

1.5 e 17 / 20

- 0 pts Correct

- 1 pts Same mistake

✓ - 3 pts Minor mistake

- 10 pts Multiple mistakes

- 20 pts Incorrect

1.6 f 10 / 10

✓ - 0 pts Correct

- 1 pts Same mistake

- 3 pts Minor mistake

- 10 pts Incorrect

QUESTION 2

2 Q2 15 / 15

✓ - 0 pts Correct

- 3 pts Minor mistake

- 10 pts Multiple mistakes

- 15 pts Incorrect

💬 Please leave answers in decimal form

QUESTION 3

3 Q3 15 / 15

✓ - 0 pts Correct


- 3 pts Minor mistake

- 10 pts Multiple mistakes

- 15 pts Incorrect

EE3 Fall 2022

Homework Problem 1

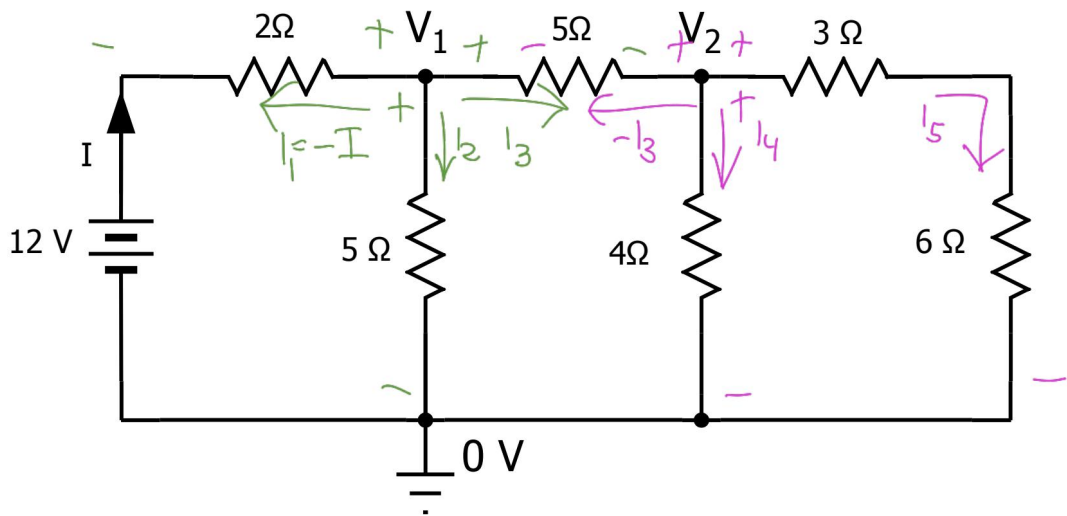

- Watch and study the KVL-KCL video as posted under Week 1. Look up and study the Passive Sign Convention.
 - Assuming that all of the currents at Node 1 (where V_1 is) are *leaving* the node, write an Ohm's Law expression for the current going through the 2Ω resistor.
 - Under the same assumption, write an Ohm's Law expression for the current through the vertical 5Ω resistor.
 - Continuing, write an expression for the current through the horizontal 5Ω resistor.
 - Now, combine the answers to 1a,b,c into a KCL equation.
 - Now, following the procedures in a, b, and c, write Ohm's Law expressions for the three currents leaving Node 2.
 - Combine the three answers to 1e into a second KCL equation.
- You now have 2 equations in 2 unknowns. Solve them for V_1 and V_2 .
- Now that you know V_1 , you can compute I .

$$\begin{array}{llll}
 \textcircled{1} \textcircled{a} \quad I_1 = -I = \frac{V_1 - 12}{2} & \textcircled{b} \quad I_2 = \frac{V_1}{5} & \textcircled{c} \quad I_3 = \frac{V_1 - V_2}{5} & \textcircled{d} \quad \frac{V_1 - 12}{2} + \frac{V_1}{5} + \frac{V_1 - V_2}{5} = 0 \\
 \textcircled{e} \quad -I_3 = \frac{V_2 - V_1}{5} & I_4 = \frac{V_2}{4} & I_5 = \frac{V_2}{3+6} & \textcircled{f} \quad \frac{V_2 - V_1}{5} + \frac{V_2}{4} + \frac{V_2}{9} = 0
 \end{array}
 \quad \left| \begin{array}{l} 5V_1 - 60 + 2V_1 + 2V_1 - 2V_2 = 0 \\ 9V_1 - 2V_2 = 60 \\ 36V_2 - 36V_1 + 45V_2 + 20V_2 = 0 \\ 101V_2 - 36V_1 = 0 \end{array} \right.$$

$$\begin{aligned}
 \textcircled{2} \quad 9V_1 - 2V_2 = 60 &\rightarrow V_1 = \frac{60 + 2V_2}{9} \\
 101V_2 - 36V_1 = 0 &\rightarrow V_2 = \frac{36V_1}{101} \\
 \therefore V_1 &= \frac{90 \cdot 20}{279} \\
 V_2 &= \frac{80}{31}
 \end{aligned}$$

$$I = -I_1 = 6 - \frac{V_1}{2} = 6 - \frac{1010}{279} = 2.38 \text{ A}$$

1.1 a 10 / 10

✓ - 0 pts Correct


- 3 pts Minor mistake

- 6 pts Major mistake

- 10 pts Incorrect

EE3 Fall 2022

Homework Problem 1

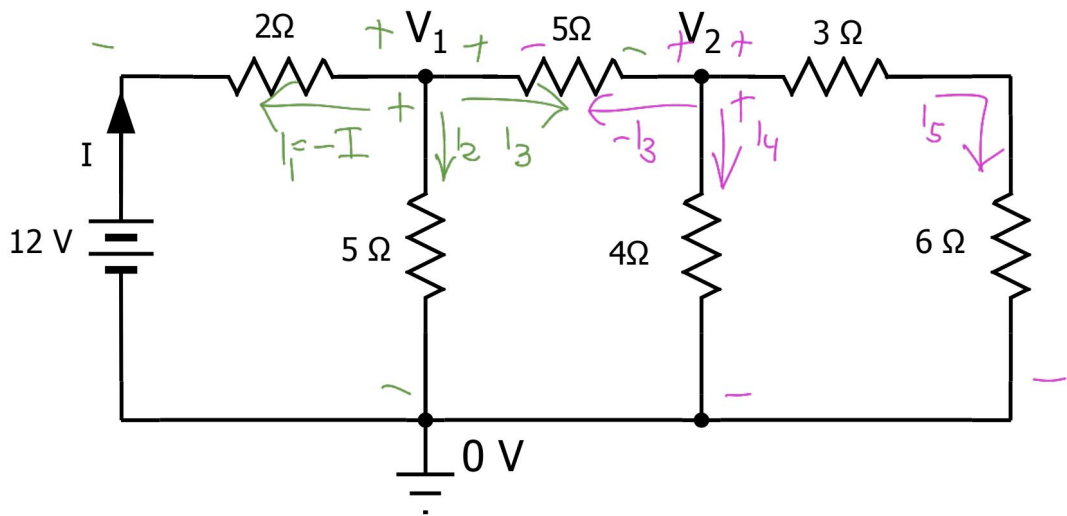

- Watch and study the KVL-KCL video as posted under Week 1. Look up and study the Passive Sign Convention.
 - Assuming that all of the currents at Node 1 (where V_1 is) are *leaving* the node, write an Ohm's Law expression for the current going through the 2Ω resistor.
 - Under the same assumption, write an Ohm's Law expression for the current through the vertical 5Ω resistor.
 - Continuing, write an expression for the current through the horizontal 5Ω resistor.
 - Now, combine the answers to 1a,b,c into a KCL equation.
 - Now, following the procedures in a, b, and c, write Ohm's Law expressions for the three currents leaving Node 2.
 - Combine the three answers to 1e into a second KCL equation.
- You now have 2 equations in 2 unknowns. Solve them for V_1 and V_2 .
- Now that you know V_1 , you can compute I .

$$\begin{array}{llll}
 \textcircled{1} \textcircled{a} \quad I_1 = -I = \frac{V_1 - 12}{2} & \textcircled{b} \quad I_2 = \frac{V_1}{5} & \textcircled{c} \quad I_3 = \frac{V_1 - V_2}{5} & \textcircled{d} \quad \frac{V_1 - 12}{2} + \frac{V_1}{5} + \frac{V_1 - V_2}{5} = 0 \\
 \textcircled{e} \quad -I_3 = \frac{V_2 - V_1}{5} & I_4 = \frac{V_2}{4} & I_5 = \frac{V_2}{3+6} & \textcircled{f} \quad \frac{V_2 - V_1}{5} + \frac{V_2}{4} + \frac{V_2}{9} = 0
 \end{array}
 \quad \left| \begin{array}{l} 5V_1 - 60 + 2V_1 + 2V_1 - 2V_2 = 0 \\ 9V_1 - 2V_2 = 60 \\ 36V_2 - 36V_1 + 45V_2 + 20V_2 = 0 \\ 101V_2 - 36V_1 = 0 \end{array} \right.$$

$$\begin{aligned}
 \textcircled{2} \quad 9V_1 - 2V_2 = 60 &\rightarrow V_1 = \frac{60 + 2V_2}{9} \\
 101V_2 - 36V_1 = 0 &\rightarrow V_2 = \frac{36V_1}{101} \\
 \therefore V_1 &= \frac{90 \cdot 20}{279} \\
 V_2 &= \frac{80}{31}
 \end{aligned}$$

$$I = -I_1 = 6 - \frac{V_1}{2} = 6 - \frac{1010}{279} = 2.38 \text{ A}$$

1.2 b 10 / 10

✓ - 0 pts Correct


- 1 pts Same mistake

- 3 pts Minor mistake

- 10 pts Incorrect

EE3 Fall 2022

Homework Problem 1

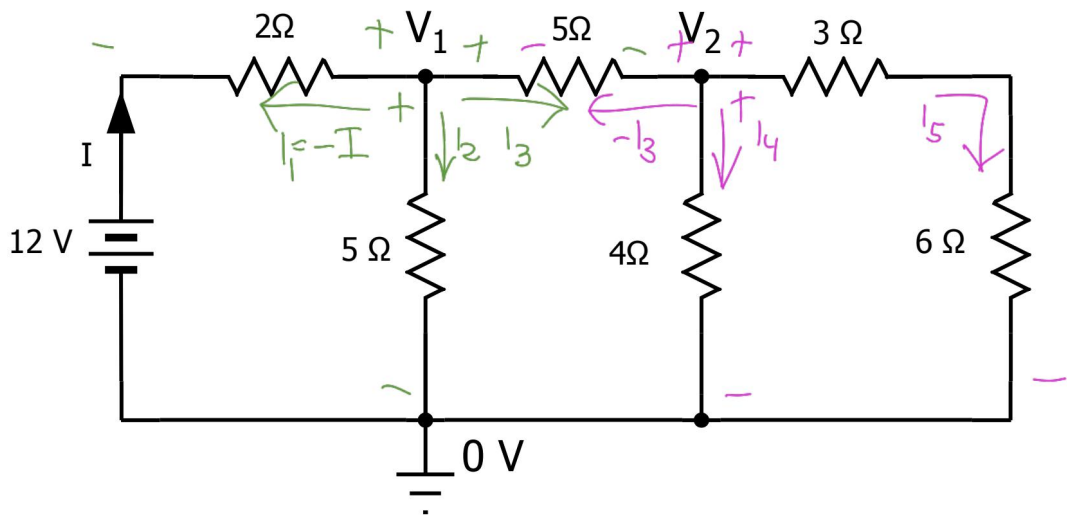

- Watch and study the KVL-KCL video as posted under Week 1. Look up and study the Passive Sign Convention.
 - Assuming that all of the currents at Node 1 (where V_1 is) are *leaving* the node, write an Ohm's Law expression for the current going through the 2Ω resistor.
 - Under the same assumption, write an Ohm's Law expression for the current through the vertical 5Ω resistor.
 - Continuing, write an expression for the current through the horizontal 5Ω resistor.
 - Now, combine the answers to 1a,b,c into a KCL equation.
 - Now, following the procedures in a, b, and c, write Ohm's Law expressions for the three currents leaving Node 2.
 - Combine the three answers to 1e into a second KCL equation.
- You now have 2 equations in 2 unknowns. Solve them for V_1 and V_2 .
- Now that you know V_1 , you can compute I .

$$\begin{array}{llll}
 \textcircled{1} \textcircled{a} \quad I_1 = -I = \frac{V_1 - 12}{2} & \textcircled{b} \quad I_2 = \frac{V_1}{5} & \textcircled{c} \quad I_3 = \frac{V_1 - V_2}{5} & \textcircled{d} \quad \frac{V_1 - 12}{2} + \frac{V_1}{5} + \frac{V_1 - V_2}{5} = 0 \\
 \textcircled{e} \quad -I_3 = \frac{V_2 - V_1}{5} & I_4 = \frac{V_2}{4} & I_5 = \frac{V_2}{3+6} & \textcircled{f} \quad \frac{V_2 - V_1}{5} + \frac{V_2}{4} + \frac{V_2}{9} = 0
 \end{array}
 \quad \left| \begin{array}{l} 5V_1 - 60 + 2V_1 + 2V_1 - 2V_2 = 0 \\ 9V_1 - 2V_2 = 60 \\ 36V_2 - 36V_1 + 45V_2 + 20V_2 = 0 \\ 101V_2 - 36V_1 = 0 \end{array} \right.$$

$$\begin{aligned}
 \textcircled{2} \quad 9V_1 - 2V_2 = 60 &\rightarrow V_1 = \frac{60 + 2V_2}{9} \\
 101V_2 - 36V_1 = 0 &\rightarrow V_2 = \frac{36V_1}{101} \\
 \therefore V_1 &= \frac{90 \cdot 20}{279} \\
 V_2 &= \frac{80}{31}
 \end{aligned}$$

$$I = -I_1 = 6 - \frac{V_1}{2} = 6 - \frac{1010}{279} = 2.38 \text{ A}$$

1.3 C 10 / 10

✓ - 0 pts Correct


- 1 pts Same mistake

- 3 pts Minor mistake

- 10 pts Incorrect

EE3 Fall 2022

Homework Problem 1

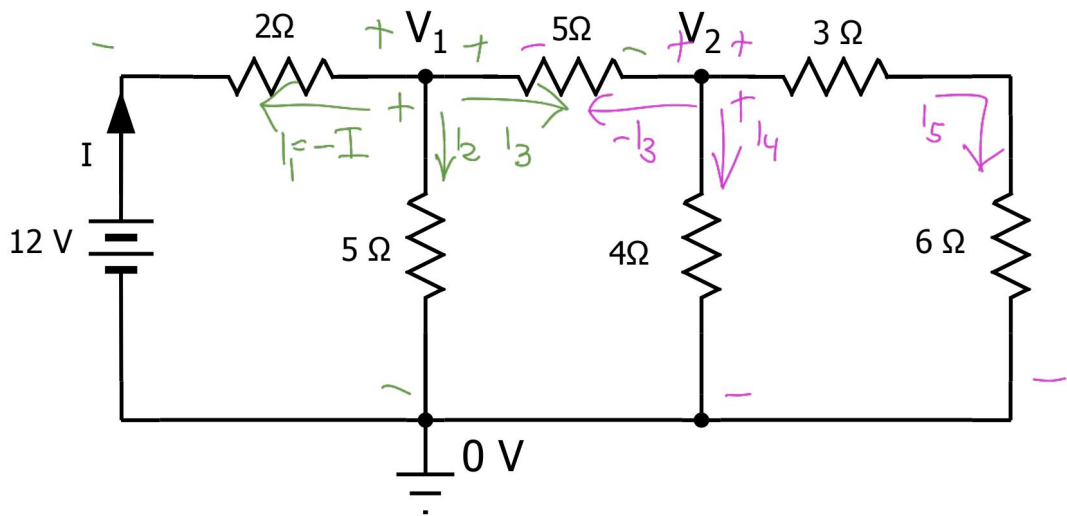

- Watch and study the KVL-KCL video as posted under Week 1. Look up and study the Passive Sign Convention.
 - Assuming that all of the currents at Node 1 (where V_1 is) are *leaving* the node, write an Ohm's Law expression for the current going through the 2Ω resistor.
 - Under the same assumption, write an Ohm's Law expression for the current through the vertical 5Ω resistor.
 - Continuing, write an expression for the current through the horizontal 5Ω resistor.
 - Now, combine the answers to 1a,b,c into a KCL equation.
 - Now, following the procedures in a, b, and c, write Ohm's Law expressions for the three currents leaving Node 2.
 - Combine the three answers to 1e into a second KCL equation.
- You now have 2 equations in 2 unknowns. Solve them for V_1 and V_2 .
- Now that you know V_1 , you can compute I .

$$\begin{array}{llll}
 \textcircled{1} \textcircled{a} \quad I_1 = -I = \frac{V_1 - 12}{2} & \textcircled{b} \quad I_2 = \frac{V_1}{5} & \textcircled{c} \quad I_3 = \frac{V_1 - V_2}{5} & \textcircled{d} \quad \frac{V_1 - 12}{2} + \frac{V_1}{5} + \frac{V_1 - V_2}{5} = 0 \\
 \textcircled{e} \quad -I_3 = \frac{V_2 - V_1}{5} & I_4 = \frac{V_2}{4} & I_5 = \frac{V_2}{3+6} & \textcircled{f} \quad \frac{V_2 - V_1}{5} + \frac{V_2}{4} + \frac{V_2}{9} = 0
 \end{array}
 \quad \left| \begin{array}{l} 5V_1 - 60 + 2V_1 + 2V_1 - 2V_2 = 0 \\ 9V_1 - 2V_2 = 60 \\ 36V_2 - 36V_1 + 45V_2 + 20V_2 = 0 \\ 101V_2 - 36V_1 = 0 \end{array} \right.$$

$$\begin{aligned}
 \textcircled{2} \quad 9V_1 - 2V_2 = 60 &\rightarrow V_1 = \frac{60 + 2V_2}{9} \\
 101V_2 - 36V_1 = 0 &\rightarrow V_2 = \frac{36V_1}{101} \\
 \therefore V_1 &= \frac{90 \cdot 20}{279} \\
 V_2 &= \frac{80}{31}
 \end{aligned}$$

$$I = -I_1 = 6 - \frac{V_1}{2} = 6 - \frac{1010}{279} = 2.38 \text{ A}$$

1.4 d 10 / 10

✓ - 0 pts Correct


- 1 pts Same mistake

- 3 pts Minor mistake

- 10 pts Incorrect

EE3 Fall 2022

Homework Problem 1

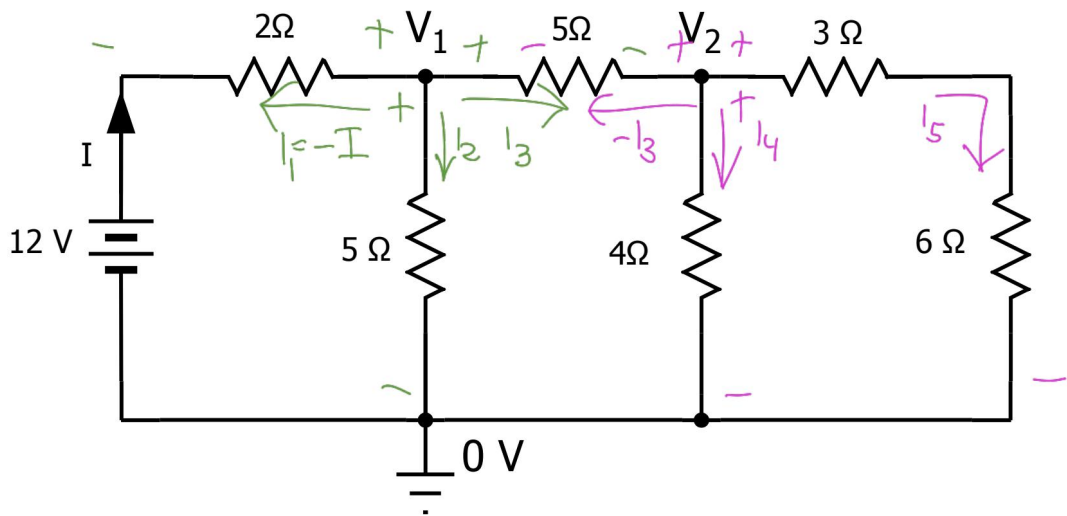

- Watch and study the KVL-KCL video as posted under Week 1. Look up and study the Passive Sign Convention.
 - Assuming that all of the currents at Node 1 (where V_1 is) are *leaving* the node, write an Ohm's Law expression for the current going through the 2Ω resistor.
 - Under the same assumption, write an Ohm's Law expression for the current through the vertical 5Ω resistor.
 - Continuing, write an expression for the current through the horizontal 5Ω resistor.
 - Now, combine the answers to 1a,b,c into a KCL equation.
 - Now, following the procedures in a, b, and c, write Ohm's Law expressions for the three currents leaving Node 2.
 - Combine the three answers to 1e into a second KCL equation.
- You now have 2 equations in 2 unknowns. Solve them for V_1 and V_2 .
- Now that you know V_1 , you can compute I .

$$\begin{array}{llll}
 \textcircled{1} \textcircled{a} \quad I_1 = -I = \frac{V_1 - 12}{2} & \textcircled{b} \quad I_2 = \frac{V_1}{5} & \textcircled{c} \quad I_3 = \frac{V_1 - V_2}{5} & \textcircled{d} \quad \frac{V_1 - 12}{2} + \frac{V_1}{5} + \frac{V_1 - V_2}{5} = 0 \\
 \textcircled{e} \quad -I_3 = \frac{V_2 - V_1}{5} & I_4 = \frac{V_2}{4} & I_5 = \frac{V_2}{3+6} & \textcircled{f} \quad \frac{V_2 - V_1}{5} + \frac{V_2}{4} + \frac{V_2}{9} = 0
 \end{array}
 \quad \left| \begin{array}{l} 5V_1 - 60 + 2V_1 + 2V_1 - 2V_2 = 0 \\ 9V_1 - 2V_2 = 60 \\ 36V_2 - 36V_1 + 45V_2 + 20V_2 = 0 \\ 101V_2 - 36V_1 = 0 \end{array} \right.$$

$$\begin{aligned}
 \textcircled{2} \quad 9V_1 - 2V_2 = 60 &\rightarrow V_1 = \frac{60 + 2V_2}{9} \\
 101V_2 - 36V_1 = 0 &\rightarrow V_2 = \frac{36V_1}{101} \\
 \therefore V_1 &= \frac{90 \cdot 20}{279} \\
 V_2 &= \frac{80}{31}
 \end{aligned}$$


$$I = -I_1 = 6 - \frac{V_1}{2} = 6 - \frac{1010}{279} = 2.38 \text{ A}$$

1.5 e 17 / 20

- 0 pts Correct
- 1 pts Same mistake
- ✓ - 3 pts *Minor mistake*
- 10 pts Multiple mistakes
- 20 pts Incorrect

EE3 Fall 2022

Homework Problem 1

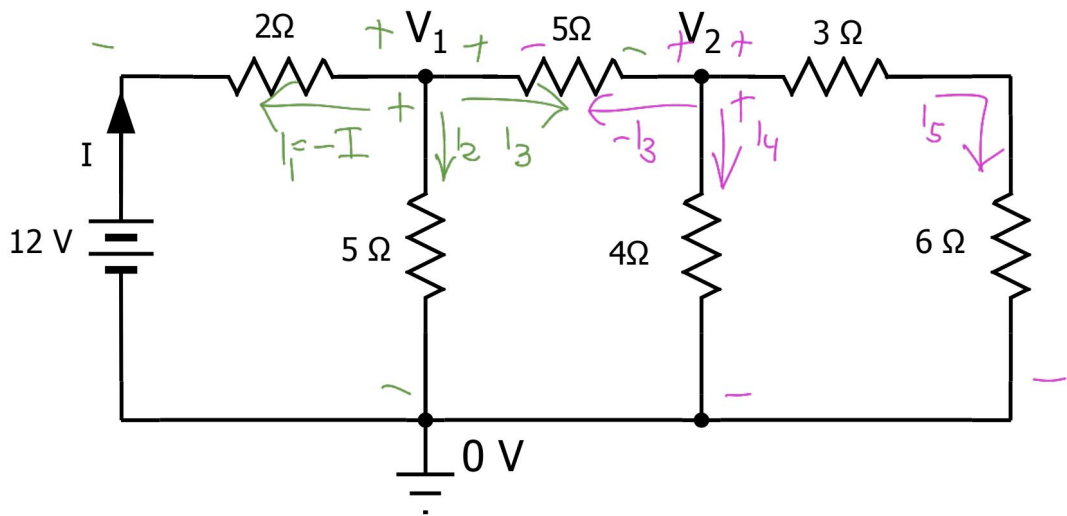

- Watch and study the KVL-KCL video as posted under Week 1. Look up and study the Passive Sign Convention.
 - Assuming that all of the currents at Node 1 (where V_1 is) are *leaving* the node, write an Ohm's Law expression for the current going through the 2Ω resistor.
 - Under the same assumption, write an Ohm's Law expression for the current through the vertical 5Ω resistor.
 - Continuing, write an expression for the current through the horizontal 5Ω resistor.
 - Now, combine the answers to 1a,b,c into a KCL equation.
 - Now, following the procedures in a, b, and c, write Ohm's Law expressions for the three currents leaving Node 2.
 - Combine the three answers to 1e into a second KCL equation.
- You now have 2 equations in 2 unknowns. Solve them for V_1 and V_2 .
- Now that you know V_1 , you can compute I .

$$\begin{array}{llll}
 \textcircled{1} \textcircled{a} \quad I_1 = -I = \frac{V_1 - 12}{2} & \textcircled{b} \quad I_2 = \frac{V_1}{5} & \textcircled{c} \quad I_3 = \frac{V_1 - V_2}{5} & \textcircled{d} \quad \frac{V_1 - 12}{2} + \frac{V_1}{5} + \frac{V_1 - V_2}{5} = 0 \\
 \textcircled{e} \quad -I_3 = \frac{V_2 - V_1}{5} & I_4 = \frac{V_2}{4} & I_5 = \frac{V_2}{3+6} & \textcircled{f} \quad \frac{V_2 - V_1}{5} + \frac{V_2}{4} + \frac{V_2}{9} = 0
 \end{array}
 \quad \left| \begin{array}{l} 5V_1 - 60 + 2V_1 + 2V_1 - 2V_2 = 0 \\ 9V_1 - 2V_2 = 60 \\ 36V_2 - 36V_1 + 45V_2 + 20V_2 = 0 \\ 101V_2 - 36V_1 = 0 \end{array} \right.$$

$$\begin{aligned}
 \textcircled{2} \quad 9V_1 - 2V_2 = 60 &\rightarrow V_1 = \frac{60 + 2V_2}{9} \\
 101V_2 - 36V_1 = 0 &\rightarrow V_2 = \frac{36V_1}{101} \\
 \therefore V_1 &= \frac{90 \cdot 20}{279} \\
 V_2 &= \frac{80}{31}
 \end{aligned}$$

$$I = -I_1 = 6 - \frac{V_1}{2} = 6 - \frac{1010}{279} = 2.38A$$

1.6 f 10 / 10

✓ - 0 pts Correct

- 1 pts Same mistake

- 3 pts Minor mistake

- 10 pts Incorrect

2 Q2 15 / 15

✓ - **0 pts** Correct

- **3 pts** Minor mistake

- **10 pts** Multiple mistakes

- **15 pts** Incorrect

💬 Please leave answers in decimal form

3 Q3 15 / 15

✓ - **0 pts** *Correct*

- **3 pts** Minor mistake

- **10 pts** Multiple mistakes

- **15 pts** Incorrect