

23S-EC ENGR-3-LEC-1 FINAL EXAM NEW

SANJIT SARDA

TOTAL POINTS

95 / 100

QUESTION 1

Q1 15 pts

1.1 A 10 / 10

- ✓ - **0 pts** Correct
- **5 pts** Wrong with partial correct steps
- **10 pts** Wrong

1.2 B 5 / 5

- ✓ - **0 pts** Correct
- **5 pts** Wrong

QUESTION 2

2 Q2 15 / 15

- ✓ - **0 pts** Correct Answer (B)
- **5 pts** Missing/Incorrect explanation for R_1
- **5 pts** Missing/Incorrect explanation for R_3
- **5 pts** Minor conceptual mistake
- **10 pts** Major conceptual mistake
- **15 pts** Not attempted/Missing

QUESTION 3

3 Q3 25 / 25

- ✓ - **0 pts** Correct
- **2 pts** Calculation error
- **15 pts** Minor error

- **20 pts** Major error
- **25 pts** Wrong

QUESTION 4

4 Q4 25 / 25

- ✓ - **0 pts** Correct
- **20 pts** Wrong with partial correct calculation
- **15 pts** Wrong with partial correct formula
- **2 pts** Calculation error
- **25 pts** Wrong

QUESTION 5

5 Q5 5 / 10

- **0 pts** Correct
- ✓ - **5 pts** Wrong with partial reasonable justification
- **10 pts** Wrong

QUESTION 6

6 Q6 10 / 10

- ✓ - **0 pts** Correct
- **10 pts** Wrong

ECE3 Spring 2023 Name Sarda | Sanyit
Family (Last) Name Given (First) Name

Final Exam UID 805964031

**DO NOT OPEN UNTIL
INSTRUCTED TO DO SO.**


- We will grade your test using Gradescope.
- Be sure to check the front and back of each sheet!
- Confine your work to the problem's page and back side.
- Put your name in the blank on every page front side.
- Show your setup.
- Circle your answers.
- ADD NOTES to help the graders determine your intentions.

(BACK OF COVER SHEET)

ECE3 Spring 2023 Name Sarda | Sanjit
 Family (Last) Name Given (First) Name

Final Exam UID 805964031

1 (front) (15 points)

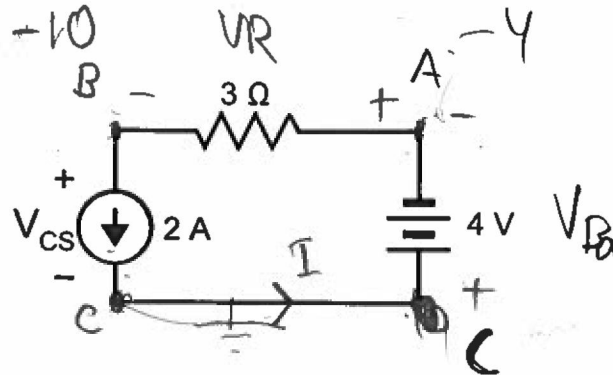

a. What is V_{CS} , if V_{CS} is defined as + at the top?

$$I = 2A$$

$$V_R = IR = 6V$$

$$V_{BA} = 4V$$

$$\therefore A = V_R + B$$

$$\textcircled{1} A = C - 4$$

$$\therefore \overset{6}{V_R} + B = C - 4$$

$$\therefore B = C - 10$$


$$\therefore B - C = -10$$

$$\therefore V_{CS} = B - C = \boxed{-10V}$$

$$V_{CS} = -10V$$

1 (back)

(Circuit from front repeated)

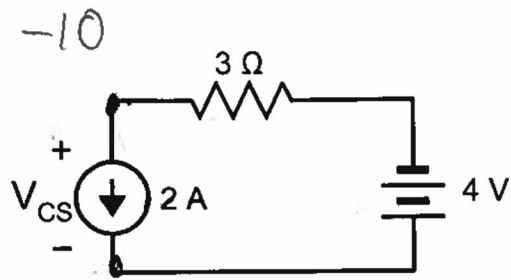

b. Is the current source providing or absorbing power? (circle one)

PROVIDING

ABSORBING

ECE3 Spring 2023 Name Sarda | Sanjit
Family (Last) Name Given (First) Name

Final Exam


UID 805964031

2 (front)

(15 points)

$$I_1 = I_3 + I_2$$

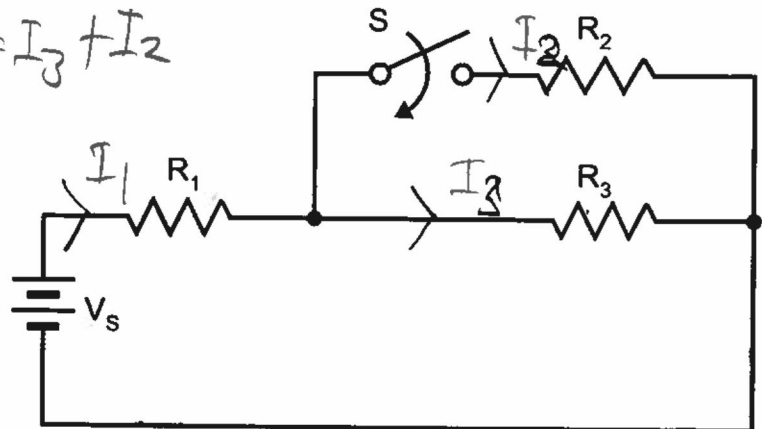NOTE: if you really understand series and parallel circuits, you will get the answer through intuition and logic; no analysis needed.



Assume all resistors are not zero and not infinite. What happens to the currents through R_1 and R_3 when switch S is closed?

- a. R_1 current stays the same, R_3 current decreases
- b. R_1 current increases, R_3 current decreases
- c. Both R_1 current and R_3 current increase
- d. Both R_1 current and R_3 current decrease
- e. Both R_1 current and R_3 current stay the same

$R_1 \uparrow$

If S_1 , then $R_{eq} < \text{Before}$

$\therefore I \uparrow$ before, since $V = I \uparrow R \downarrow$


$\therefore R_1 \text{ cur} \uparrow$

I is increasing when R decreases

Since current has more space, place $R_3 \downarrow$

2 (back)

(Circuit from front repeated)

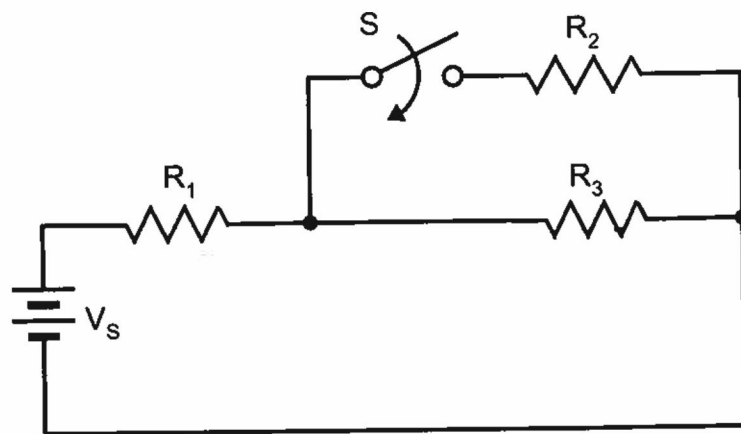

ECE3 Spring 2023 Name Sarfa

Family (Last) Name

Sanjit

Given (First) Name



Final Exam

UID 805964031

3 (front) (25 points)

The switch has been in position a for a long time. At $t=0$, the switch moves instantaneously to position b. The capacitor now discharges through the right half of the circuit according to the equation $v_c(t) = -60 + Ke^{-100t}$. Find K.

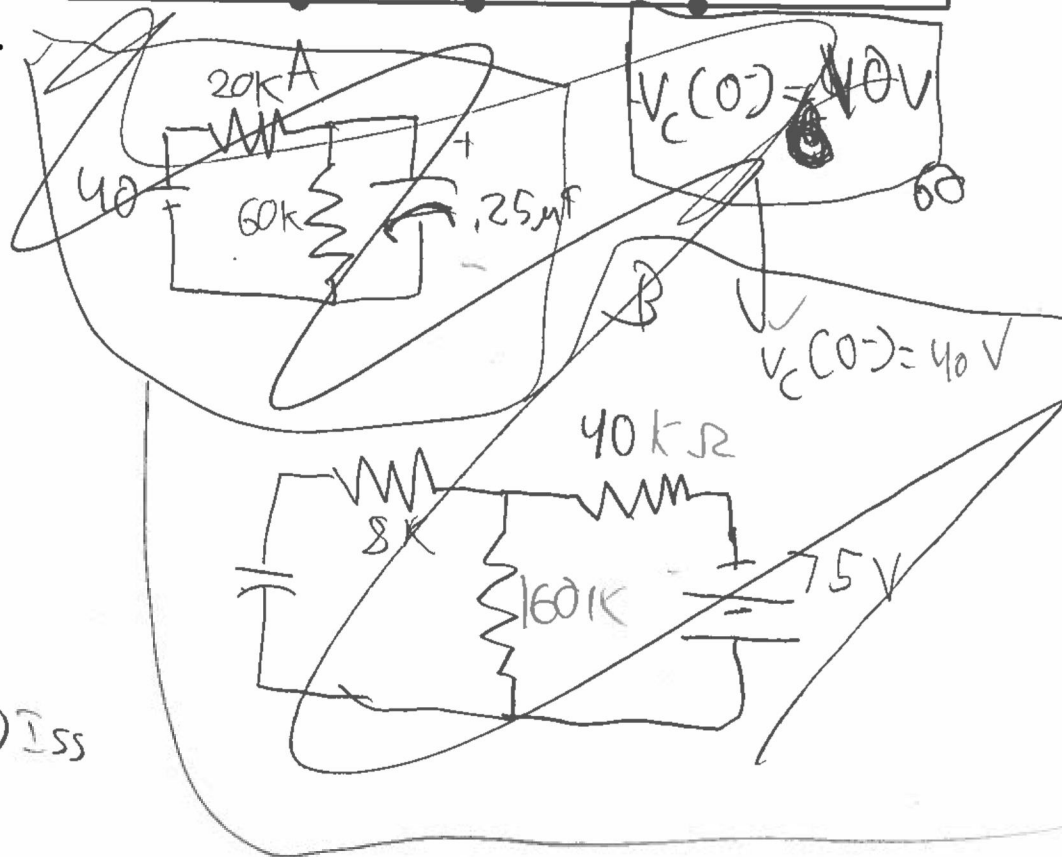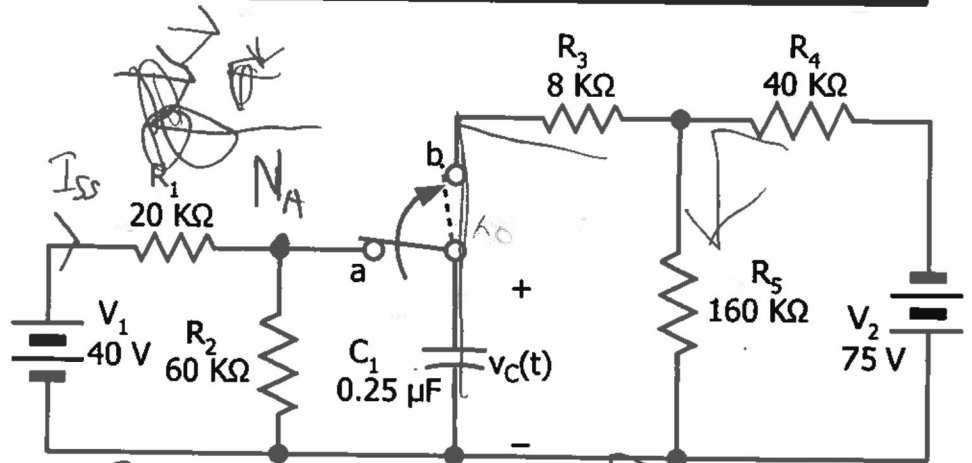HINT: the final capacitor voltage in position a is the initial capacitor voltage in position b. IOW, $v_c(0^-) = v_c(\text{long time})$.



$$I_{SS} = \frac{40}{20000}$$

$$= 5 \text{ mA}$$

$$I_{SS} = \frac{40}{20k + 60k} = \frac{1}{2k} \text{ A}$$

$$\therefore V_{NA} = V_1 + (-20k) I_{SS}$$

$$= 30 \text{ V}$$


$$\therefore V_c(0^-) = 30 \text{ V} = -60 + Ke^{-100t}$$

$$\therefore V_c(0) = 30 = -60 + Ke^{-100 \cdot 0}$$

$$\therefore 90 = Ke^0 \quad \therefore K = 90$$

3 (back)

(Circuit from front repeated)

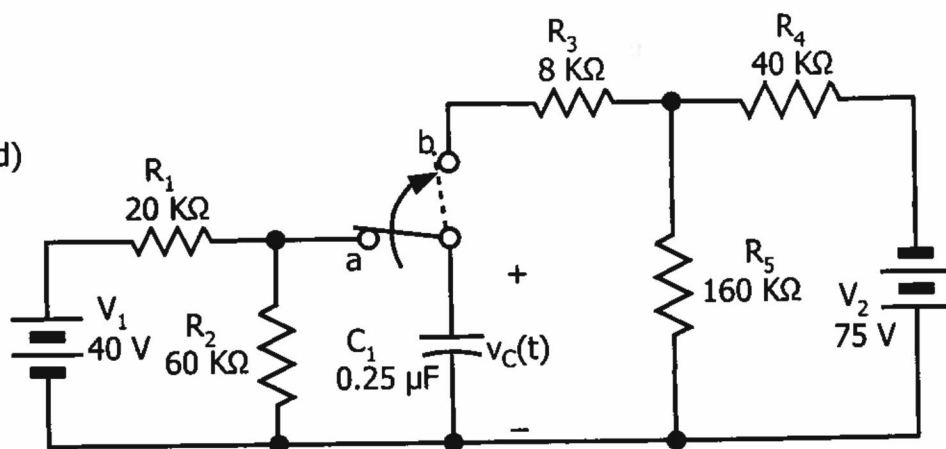

ECE3 Spring 2023 Name Sarda | Sanjit
 Family (Last) Name Given (First) Name

Final Exam

UID 805969031


4 (front) (25 points)

Find the current I_1 .

$$I_s = e^{-j\frac{\pi}{4}}$$

$$I_s = 1e^{-j\frac{\pi}{4}} \text{ A}$$

$$\omega = 5000 \text{ rad/s}$$

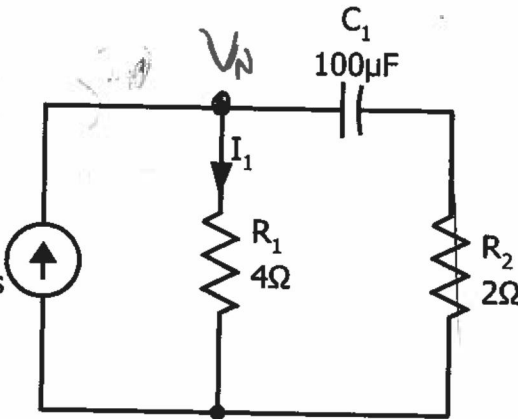

$$Z_{eq} = \left(2 + \frac{1}{j\omega C} \right) \parallel 4 = 1.788e^{-0.46j}$$

$$Z_{eq} = 1.788e^{-0.46j}$$

$$\therefore V_N = I_s Z_{eq} = (e^{-j\frac{\pi}{4}})(1.788e^{-0.46j})$$


$$I_1 = \frac{V_N}{R_1} = \frac{V_N}{4}$$

$$\therefore I_1 = \frac{(e^{-j\frac{\pi}{4}})(1.788e^{-0.46j})}{4}$$

$$= 0.1429 - 0.4235j$$

4 (back)

(Circuit from front repeated)

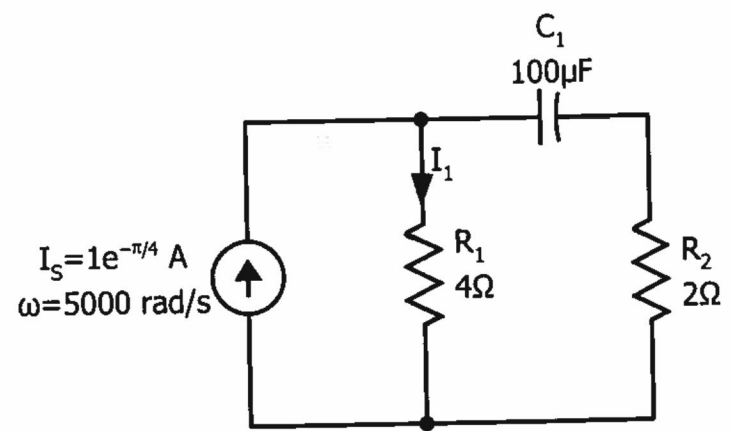

ECE3 Spring 2023 Name Sarda | Sanjay
Family (Last) Name Given (First) Name


Final Exam UID 805964031

5 (front) (10 points)

In the world of EE3, is this a legal circuit?

Yes


No

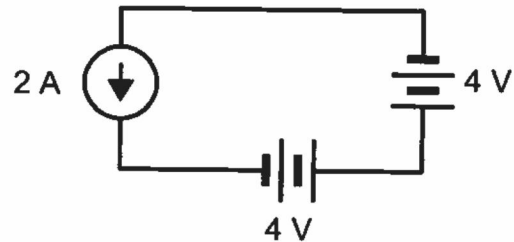

Basically shorted current source

5 (back)

(Circuit from front repeated)

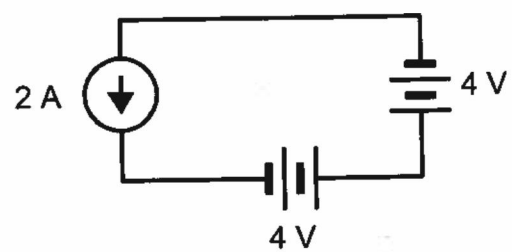


ECE3 Spring 2023 Name Sarden | Sanyit
Family (Last) Name Given (First) Name

Final Exam UID 805964031

6 (front) (10 points)

In this circuit, $R_1 < R_2$. Which resistor dissipates the least power?

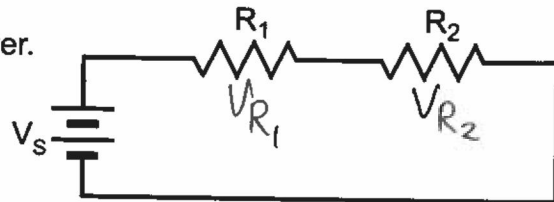- a. Neither; they dissipate the same power.
☒ b. R_1
c. R_2



$$P = VI = I^2 R$$

$$\therefore P_1 = \cancel{V_{R_1} I} = I^2 \cdot R_1$$

$$P_2 = I^2 \cdot R_2$$

$$\therefore R_1 < R_2 \rightarrow P_1 < P_2$$

6 (back)

(Circuit from front repeated)

