

23S-EC ENGR-3-LEC-1 Homework 2

SANJIT SARDA

TOTAL POINTS

100 / 100

QUESTION 1

Q1 100 pts

1.1 **a** 25 / 25

- ✓ - **0 pts** *Correct*
- **10 pts** Partially incorrect
- **20 pts** Mostly incorrect
- **25 pts** Incorrect

1.2 **b** 25 / 25

- ✓ - **0 pts** *Correct*
- **10 pts** partially incorrect
- **25 pts** Incorrect


1.3 **C** 25 / 25

- ✓ - **0 pts** *Correct*
- **10 pts** Partially Incorrect
- **20 pts** Mostly Incorrect
- **25 pts** Incorrect


1.4 **d** 25 / 25

- ✓ - **0 pts** *Correct*
- **10 pts** Partially Incorrect
- **25 pts** Incorrect


EE3 Spring 2023 Homework Problem 2

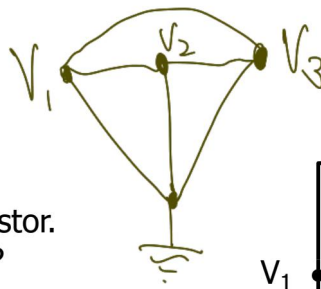

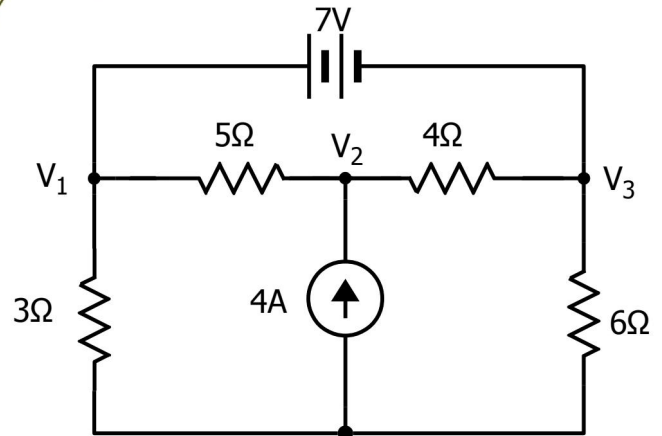- Find the current through the 6Ω resistor.
- Is the 6Ω current moving toward V_3 ?
- Find the current through the battery.
- Is the battery providing or absorbing power?



Analysis


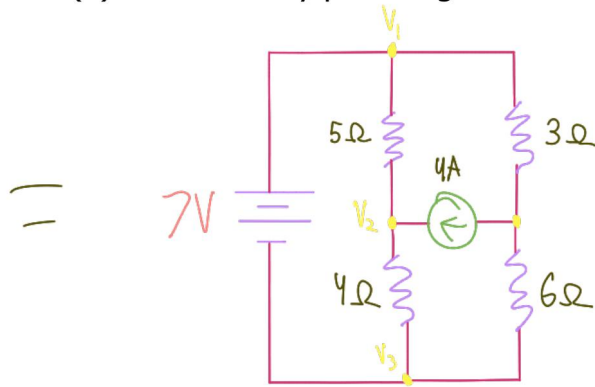


Solving for V_1, V_2, V_3 :

$$\begin{aligned} \text{KVL at } V_2: 4 + \frac{V_1 - V_2}{5} + \frac{V_3 - V_2}{4} &= 0 \\ V_1 &= V_3 + 7 \\ \frac{V_1}{3} + \frac{V_3}{6} &= 4 \end{aligned}$$

$$\begin{aligned} 80 + 4V_1 + 5V_3 - 9V_2 &= 0 \\ V_1 &= V_3 + 7 \\ 2V_1 + V_3 - 24 &= 0 \end{aligned}$$

$V_1 = \frac{31}{3} \text{ V}$	10.33
$V_2 = \frac{46}{3} \text{ V}$	15.33
$V_3 = \frac{10}{3} \text{ V}$	3.33

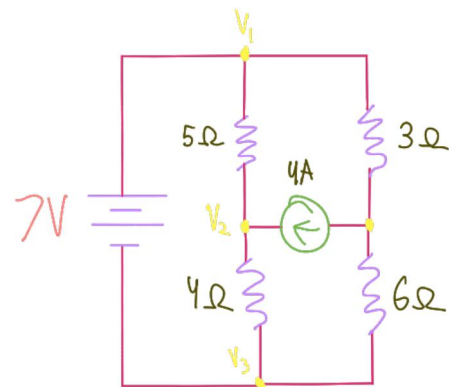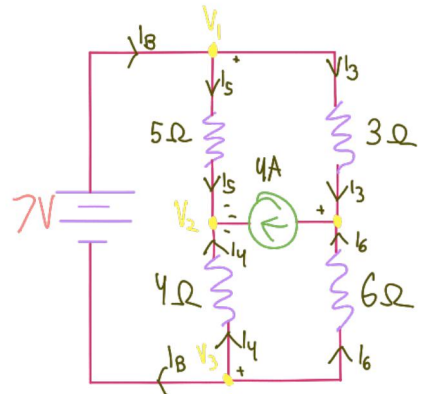

a) $I_6 = \frac{V_3}{6} = \frac{5}{9} = 0.556 \text{ A}$

b) I_+ is moving against V_3 .

c) $I_B = I_5 + I_3 = \frac{V_1 - V_2}{5} + \frac{V_1}{3} = \frac{31 - 46}{15} + \frac{31}{9} = \frac{22}{9} = 2.44 \text{ A}$

d) The current is flowing from the positive terminal, which means that the battery is delivering power.

1.1 a 25 / 25


✓ - **0 pts** Correct

- **10 pts** Partially incorrect



- **20 pts** Mostly incorrect

- **25 pts** Incorrect

EE3 Spring 2023 Homework Problem 2

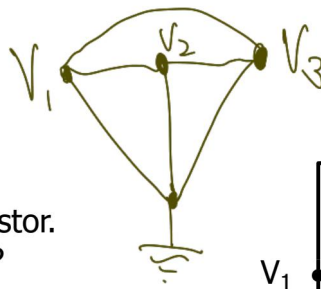

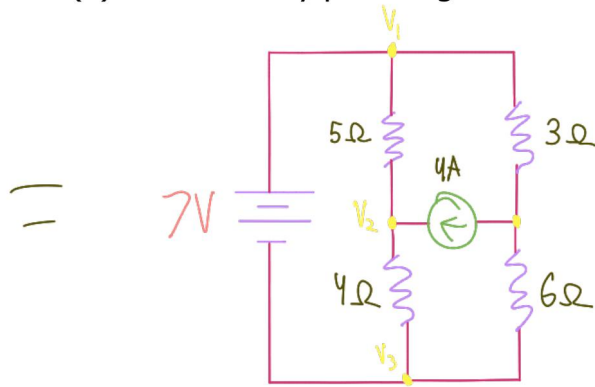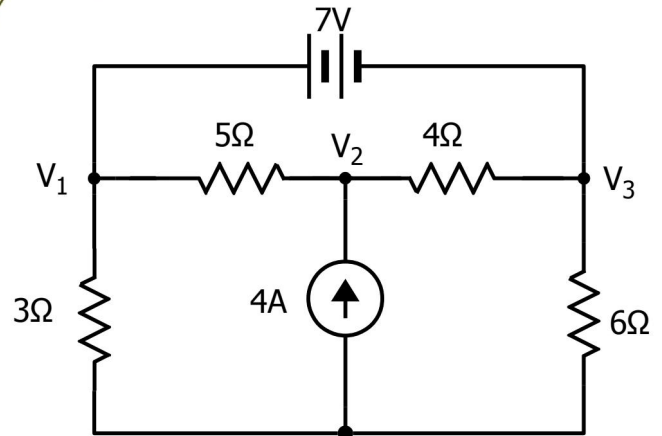- Find the current through the 6Ω resistor.
- Is the 6Ω current moving toward V_3 ?
- Find the current through the battery.
- Is the battery providing or absorbing power?





Analysis

Solving for V_1, V_2, V_3 :

$$\begin{aligned} \text{KCL at } V_2: 4 + \frac{V_1 - V_2}{5} + \frac{V_3 - V_2}{4} &= 0 \\ V_1 &= V_3 + 7 \\ \frac{V_1}{3} + \frac{V_3}{6} &= 4 \end{aligned}$$

$$\begin{aligned} 80 + 4V_1 + 5V_3 - 9V_2 &= 0 \\ V_1 &= V_3 + 7 \\ 2V_1 + V_3 - 24 &= 0 \end{aligned}$$

$V_1 = \frac{31}{3} \text{ V}$	10.33
$V_2 = \frac{46}{3} \text{ V}$	15.33
$V_3 = \frac{10}{3} \text{ V}$	3.33

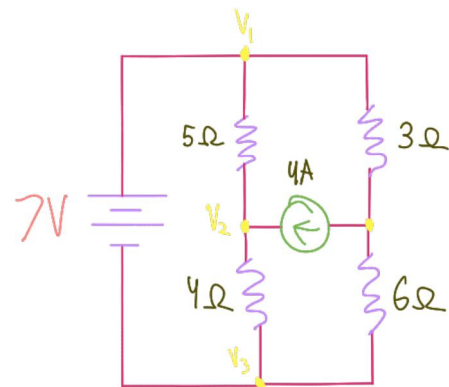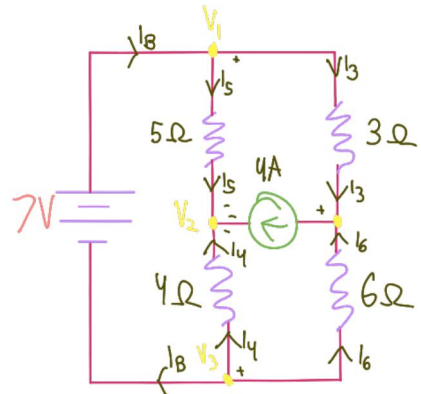

a) $I_6 = \frac{V_3}{6} = \frac{5}{9} = 0.556 \text{ A}$

b) I_+ is moving against V_3 .

c) $I_B = I_5 + I_3 = \frac{V_1 - V_2}{5} + \frac{V_1}{3} = \frac{31 - 46}{15} + \frac{31}{9} = \frac{22}{9} = 2.44 \text{ A}$

d) The current is flowing from the positive terminal, which means that the battery is delivering power.


1.2 b 25 / 25

✓ - 0 pts Correct



- 10 pts partially incorrect

- 25 pts Incorrect

EE3 Spring 2023 Homework Problem 2

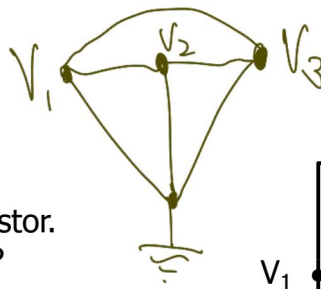

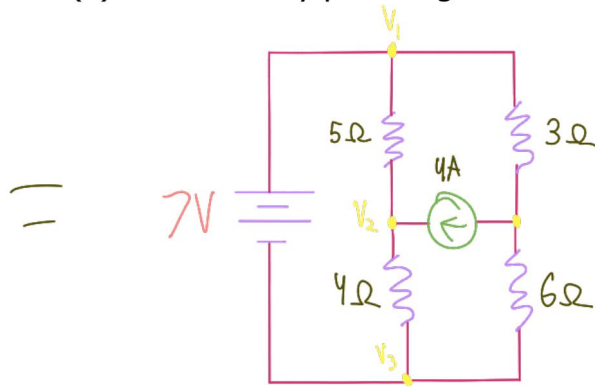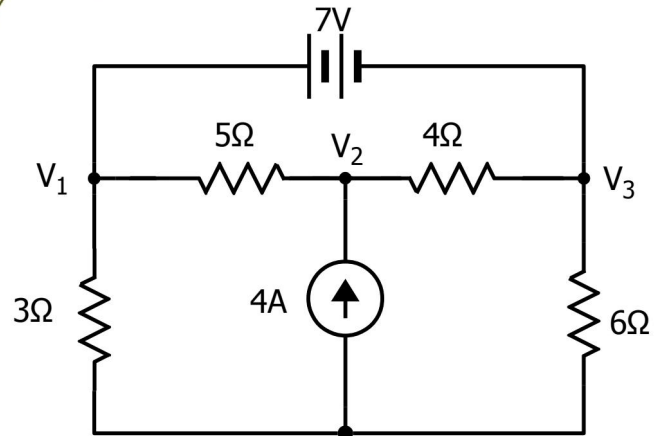- Find the current through the 6Ω resistor.
- Is the 6Ω current moving toward V_3 ?
- Find the current through the battery.
- Is the battery providing or absorbing power?





Analysis

Solving for V_1, V_2, V_3 :

$$\begin{aligned} \text{KCL at } V_2: 4 + \frac{V_1 - V_2}{5} + \frac{V_3 - V_2}{4} &= 0 \\ V_1 &= V_3 + 7 \\ \frac{V_1}{3} + \frac{V_3}{6} &= 4 \end{aligned}$$

$$\begin{aligned} 80 + 4V_1 + 5V_3 - 9V_2 &= 0 \\ V_1 &= V_3 + 7 \\ 2V_1 + V_3 - 24 &= 0 \end{aligned}$$

$V_1 = \frac{31}{3} \text{ V}$	10.33
$V_2 = \frac{46}{3} \text{ V}$	15.33
$V_3 = \frac{10}{3} \text{ V}$	3.33

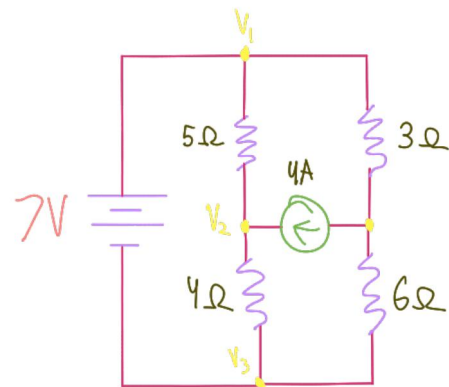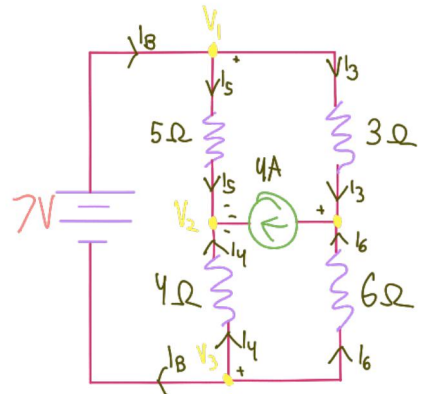

a) $I_6 = \frac{V_3}{6} = \frac{5}{9} = 0.556 \text{ A}$

b) I_+ is moving against V_3 .

c) $I_B = I_5 + I_3 = \frac{V_1 - V_2}{5} + \frac{V_1}{3} = \frac{31 - 46}{15} + \frac{31}{9} = \frac{22}{9} = 2.44 \text{ A}$

d) The current is flowing from the positive terminal, which means that the battery is delivering power.

1.3 C 25 / 25


✓ - **0 pts** Correct

- **10 pts** Partially Incorrect



- **20 pts** Mostly Incorrect

- **25 pts** Incorrect

EE3 Spring 2023 Homework Problem 2

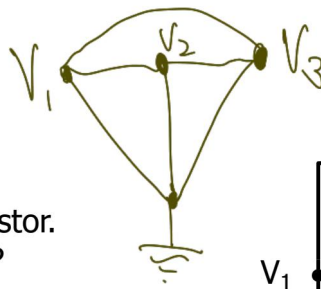

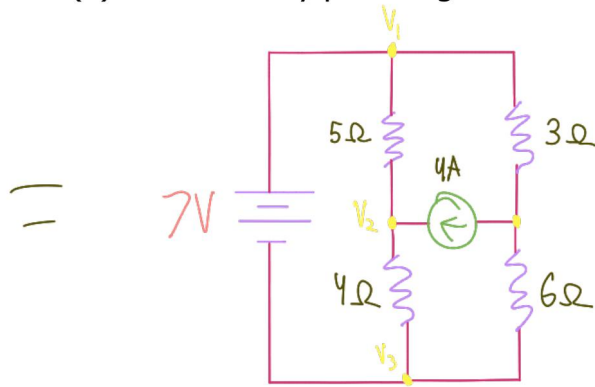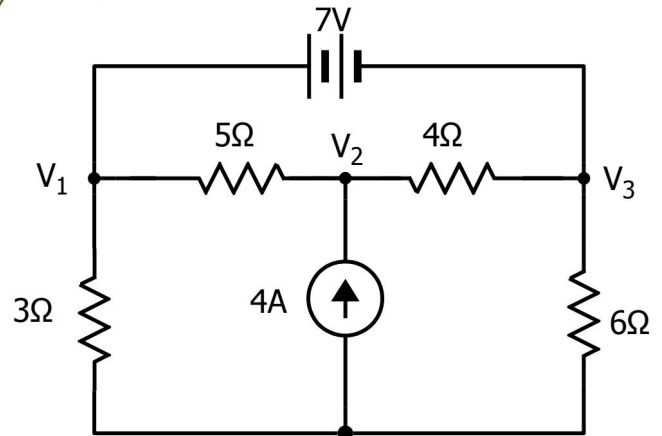- Find the current through the 6Ω resistor.
- Is the 6Ω current moving toward V_3 ?
- Find the current through the battery.
- Is the battery providing or absorbing power?





Analysis

Solving for V_1, V_2, V_3 :

$$\begin{aligned} \text{KCL at } V_2: 4 + \frac{V_1 - V_2}{5} + \frac{V_3 - V_2}{4} &= 0 \\ V_1 &= V_3 + 7 \\ \frac{V_1}{3} + \frac{V_3}{6} &= 4 \end{aligned}$$

$$\begin{aligned} 80 + 4V_1 + 5V_3 - 9V_2 &= 0 \\ V_1 &= V_3 + 7 \\ 2V_1 + V_3 - 24 &= 0 \end{aligned}$$

$V_1 = \frac{31}{3} \text{ V}$	10.33
$V_2 = \frac{46}{3} \text{ V}$	15.33
$V_3 = \frac{10}{3} \text{ V}$	3.33

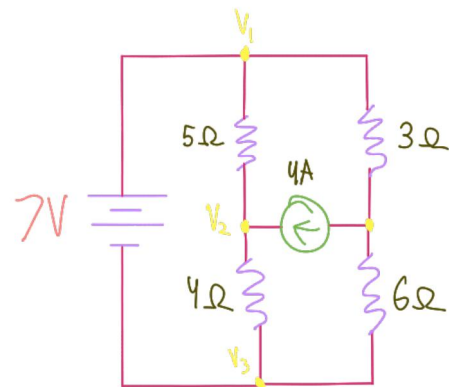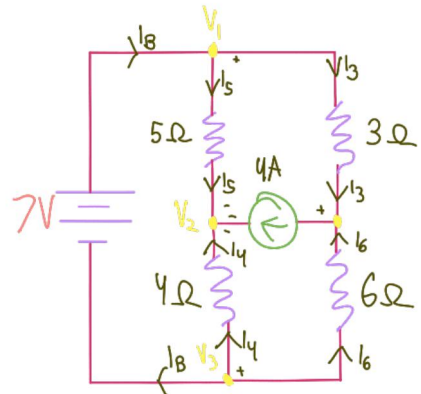

a) $I_6 = \frac{V_3}{6} = \frac{5}{9} = 0.556 \text{ A}$

b) I_+ is moving against V_3 .

c) $I_B = I_5 + I_3 = \frac{V_1 - V_2}{5} + \frac{V_1}{3} = \frac{31 - 46}{15} + \frac{31}{9} = \frac{22}{9} = 2.44 \text{ A}$

d) The current is flowing from the positive terminal, which means that the battery is delivering power.

1.4 d 25 / 25

✓ - 0 pts Correct

- 10 pts Partially Incorrect

- 25 pts Incorrect