

# 23W-EC ENGR-11L-LEC-1 Module 4: Transient Response of the 2nd -Order Circuits

SANJIT SARDA

TOTAL POINTS

**65 / 65**

## QUESTION 1

### Series RLC Circuit Analysis 20 pts

#### 1.1 Waveforms Image 6 / 6

- ✓ **+ 6 pts** Correct
- + 3 pts Click here to replace this description.
- + 0 pts Missing

#### 1.2 Inductor Resistance 3 / 3

- ✓ **+ 3 pts** Correct
- + 2 pts Slightly Incorrect
- + 0 pts Missing

#### 1.3 Derivation of Output Voltage 8 / 8

- ✓ **+ 8 pts** Correct
- + 7 pts Slightly Incorrect
- + 6 pts Slightly incorrect
- + 4 pts Incorrect
- + 2 pts Incorrect
- + 0 pts Missing

#### 1.4 Discussion 1 3 / 3

- ✓ **+ 3 pts** Correct
- + 2 pts Incomplete
- + 1 pts Incomplete
- + 0 pts Missing

## QUESTION 2

### Underdamped RLC Circuit Design 26 pts

#### 2.1 Waveforms Image 6 / 6

- ✓ **- 0 pts** Correct
- 1 pts Slightly higher Overshoot
- 3 pts Lower Overshoot
- 1 pts Slightly lower Overshoot
- 3 pts Higher Overshoot
- 6 pts Incorrect

#### 2.2 Overshoot measurement 3 / 3

- ✓ **- 0 pts** Correct
- 2 pts Too high Overshoot
- 3 pts Incorrect
- 1 pts Higher Overshoot
- 1 pts Lower Overshoot
- 3 pts Too Low Overshoot

#### 2.3 Damped Frequency measurement 3 / 3

- ✓ **- 0 pts** Correct
- 3 pts Incorrect
- 2 pts Slightly incorrect
- 2 pts Partially incorrect

#### 2.4 Derivation of Output Voltage 8 / 8

- ✓ - 0 pts Correct
- 4 pts Mistake
- 2 pts Small mistake
- 4 pts Partial
- 8 pts Missing
- 4 pts Derivation Missing

#### 2.5 Discussion 1 3 / 3

- ✓ - 0 pts Correct
- 3 pts Incorrect
- 1 pts Partially correct

#### 2.6 Discussion 2 3 / 3

- ✓ - 0 pts Correct
- 3 pts Incorrect
- 1 pts Partial explanation

#### Resistance 4 / 4

- ✓ + 4 pts Correct
- + 3 pts Slightly Incorrect
- + 2 pts Incorrect
- + 0 pts Missing

#### 3.4 Discussion 1 3 / 3

- ✓ + 3 pts Correct
- + 2 pts Slightly incorrect
- + 0 pts Missing

#### 3.5 Discussion 2 3 / 3

- ✓ + 3 pts Correct
- + 2 pts Slightly Incorrect/Incomplete.
- + 0 pts Missing

#### QUESTION 3

### Critically Damped RLC Circuit 19 pts

#### 3.1 Waveforms Image 6 / 6


- ✓ + 6 pts Correct
- + 5 pts Slightly Incorrect.
- + 4 pts Slightly Incorrect
- + 3 pts Incorrect
- + 0 pts Missing

#### 3.2 Potentiometer resistance 3 / 3

- ✓ + 3 pts Correct
- + 1 pts Incorrect
- + 0 pts Missing
- + 2 pts Slightly incorrect

#### 3.3 Derivation of Critical Damping

## 1. Series RLC Circuit Analysis

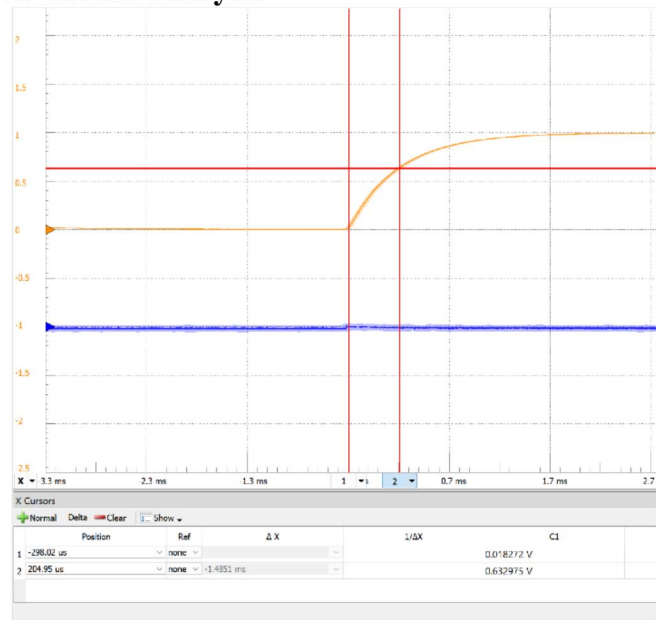

cross the capacitor.>  
transient response.>

- What is the inductor resistance?

$$R_{\text{inductor}} = 165 \, \Omega$$


## 1.1 Waveforms Image 6 / 6

✓ + 6 pts Correct

+ 3 pts [Click here to replace this description.](#)

+ 0 pts Missing

## 1. Series RLC Circuit Analysis

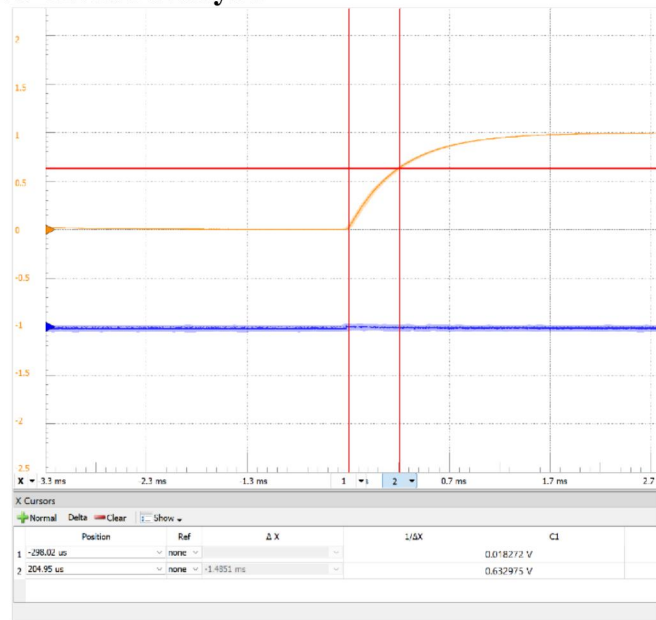

cross the capacitor.>  
transient response.>

- What is the inductor resistance?

$$R_{\text{inductor}} = 165 \, \Omega$$


## 1.2 Inductor Resistance 3 / 3

✓ + 3 pts Correct

+ 2 pts Slightly Incorrect

+ 0 pts Missing

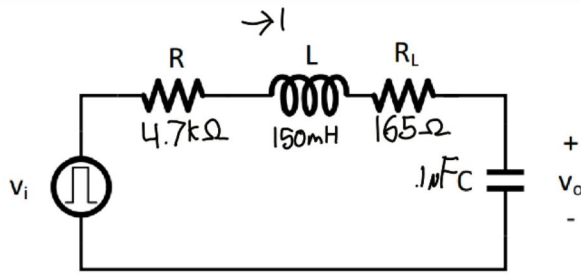- Derive theoretical equation for output voltage  $v_o(t)$  (including  $R_L$ ) across capacitor for your design.



$$V_o = \frac{1}{C} \int i$$

$$i = C v_o'$$

$$V_i - R i' - L i'' - R_L i = \frac{1}{C} \int i$$

$$\therefore V_i - R C v_o' - L C v_o'' - R_L C v_o' = V_o$$

$$L C v_o'' + (R + R_L) C v_o' + V_o = V_i$$

$$\therefore v_o'' + \frac{R + R_L}{L} v_o' + \frac{V_o}{L C} = \frac{V_i}{L C}$$

$$\therefore v_o'' + \frac{4865}{0.15} v_o' + \frac{V_o}{1.5 \times 10^{-8}} = \frac{V_i}{1.5 \times 10^{-8}}$$

$$\therefore v_o'' + 32433 v_o' + (6.66 \times 10^7) v_o = V_i$$

Solution to characteristic:

Discussion  $v_o = C_1 e^{-2205t} + C_2 e^{-30229t} + C_3$

When  $V_i$ : falling edge

$$V_o(0^+) = V_o(0^-) = 1 \quad V_o(\infty) = 1$$

$$v_o'(0^+) = \frac{i(0^+)}{C} = \frac{i(0^-)}{C} = 0$$

$\therefore$  Solving for  $V_i = 0$  @ falling edge

$$C_3 = V_o(\infty) = 1$$

$$V_o(0) = 1 = C_1 + C_2$$

$$v_o'(0) = 0 = -2205 C_1 - 30229 C_2$$

$$\therefore C_1 = 1.079$$

$$C_2 = -0.079$$

$$\therefore V_o(t) = 1.079 e^{-2205t}$$

- What kind of damping is observed? Verify that this matches with the theoretical expectation.

Over damped.  $\zeta = \frac{\alpha}{\omega_0} = \frac{R}{2L} \cdot \frac{1}{\frac{1}{\sqrt{LC}}} = \frac{R \sqrt{LC}}{2L} = \frac{R \sqrt{C}}{2 \sqrt{L}} =$

$$\frac{4865 \Omega}{2} \sqrt{\frac{0.1 \mu F}{150 \text{ mH}}} = 1.97 \therefore \zeta > 1 \therefore \text{Overdamped.}$$

We can see on the graph that the waveform is overdamped.

### 1.3 Derivation of Output Voltage 8 / 8

✓ + 8 pts Correct

+ 7 pts Slightly Incorrect

+ 6 pts Slightly incorrect


+ 4 pts Incorrect

+ 2 pts Incorrect

+ 0 pts Missing



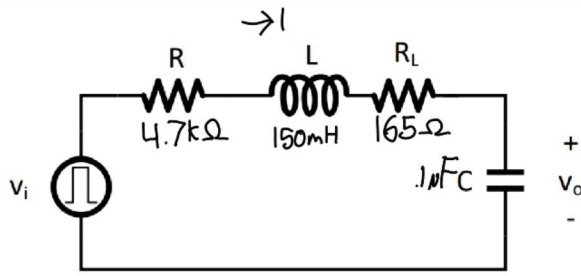- Derive theoretical equation for output voltage  $v_o(t)$  (including  $R_L$ ) across capacitor for your design.



$$V_o = \frac{1}{C} \int i$$

$$i = C v_o'$$

$$V_i - R i' - L i'' - R_L i = \frac{1}{C} \int i$$

$$\therefore V_i - R C v_o' - L C v_o'' - R_L C v_o' = V_o$$

$$L C v_o'' + (R + R_L) C v_o' + V_o = V_i$$

$$\therefore v_o'' + \frac{R + R_L}{L} v_o' + \frac{V_o}{L C} = \frac{V_i}{L C}$$

$$\therefore v_o'' + \frac{4865}{0.15} v_o' + \frac{V_o}{1.5 \times 10^{-8}} = \frac{V_i}{1.5 \times 10^{-8}}$$

$$\therefore v_o'' + 32433 v_o' + (6.66 \times 10^7) v_o = V_i$$

Solution to characteristic:

Discussion  $v_o = C_1 e^{-2205t} + C_2 e^{-30229t} + C_3$

When  $V_i$ : falling edge

$$V_o(0^+) = V_o(0^-) = 1 \quad V_o(\infty) = 1$$

$$v_o'(0^+) = \frac{i(0^+)}{C} = \frac{i(0^-)}{C} = 0$$

$\therefore$  Solving for  $V_i = 0$  @ falling edge

$$C_3 = V_o(\infty) = 1$$

$$V_o(0) = 1 = C_1 + C_2$$

$$v_o'(0) = 0 = -2205 C_1 - 30229 C_2$$

$$\therefore C_1 = 1.079$$

$$C_2 = -0.079$$

$$\therefore V_o(t) = 1.079 e^{-2205t}$$

- What kind of damping is observed? Verify that this matches with the theoretical expectation.

Over damped.  $\zeta = \frac{\alpha}{\omega_0} = \frac{R}{2L} \cdot \frac{1}{\frac{1}{\sqrt{LC}}} = \frac{R \sqrt{LC}}{2L} = \frac{R \sqrt{C}}{2 \sqrt{L}} =$

$$\frac{4865 \Omega}{2} \sqrt{\frac{0.1 \mu F}{150 \text{ mH}}} = 1.97 \therefore \zeta > 1 \therefore \text{Overdamped.}$$

We can see on the graph that the waveform is overdamped.

#### 1.4 Discussion 1 3 / 3


✓ + 3 pts Correct

+ 2 pts Incomplete

+ 1 pts Incomplete

+ 0 pts Missing

## 2. Underdamped RLC Circuit Design

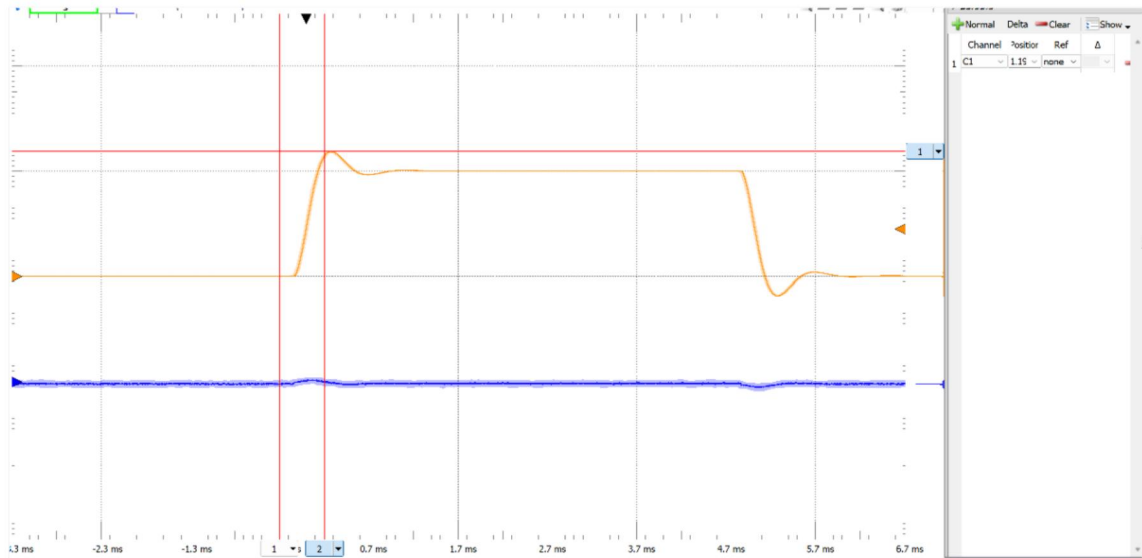

Overshoot Measurement:

Experimental Value of Resistor used ( $\Omega$ )	Overshoot measured (%)
1000	.19%

Damped Frequency Measurement:


Experimental Damped Frequency (Hz)	Theoretical Damped Frequency (Hz)
$1/(2(669\mu\text{s} - 225\mu\text{s})) = 1205\text{ Hz}$	1145 Hz

## 2.1 Waveforms Image 6 / 6

✓ - 0 pts *Correct*

- 1 pts Slightly higher Overshoot
- 3 pts Lower Overshoot
- 1 pts Slightly lower Overshoot
- 3 pts Higher Overshoot
- 6 pts Incorrect

## 2. Underdamped RLC Circuit Design

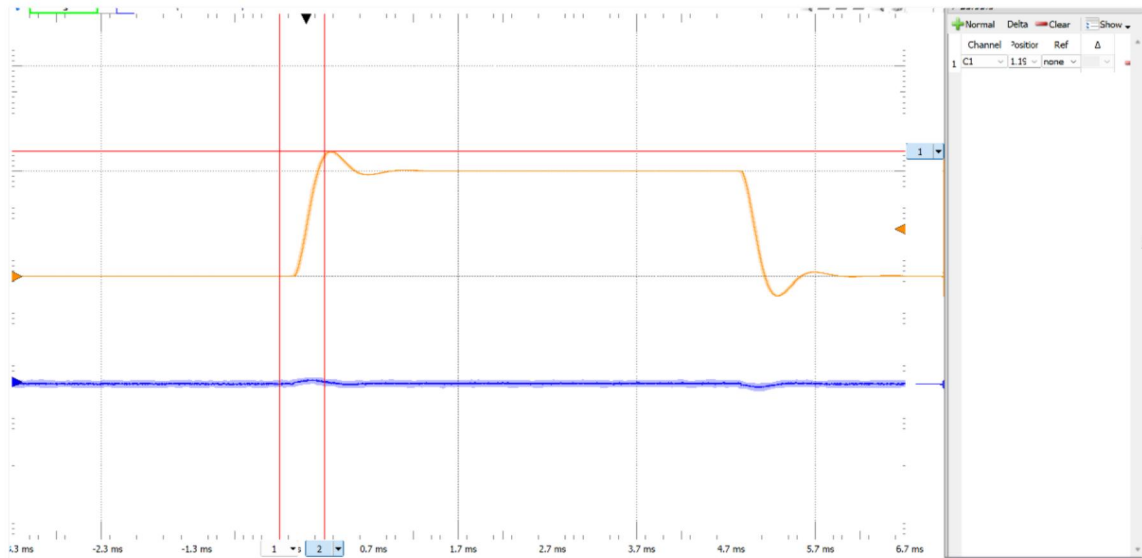

st

Overshoot Measurement:

Experimental Value of Resistor used ( $\Omega$ )	Overshoot measured (%)
1000	.19%

Damped Frequency Measurement:

Experimental Damped Frequency (Hz)	Theoretical Damped Frequency (Hz)
$1/(2(669\mu\text{s} - 225\mu\text{s})) = 1205\text{ Hz}$	1145 Hz

## 2.2 Overshoot measurement 3 / 3

✓ - 0 pts *Correct*

- 2 pts Too high Overshoot


- 3 pts Incorrect

- 1 pts Higher Overshoot

- 1 pts Lower Overshoot

- 3 pts Too Low Overshoot

## 2. Underdamped RLC Circuit Design

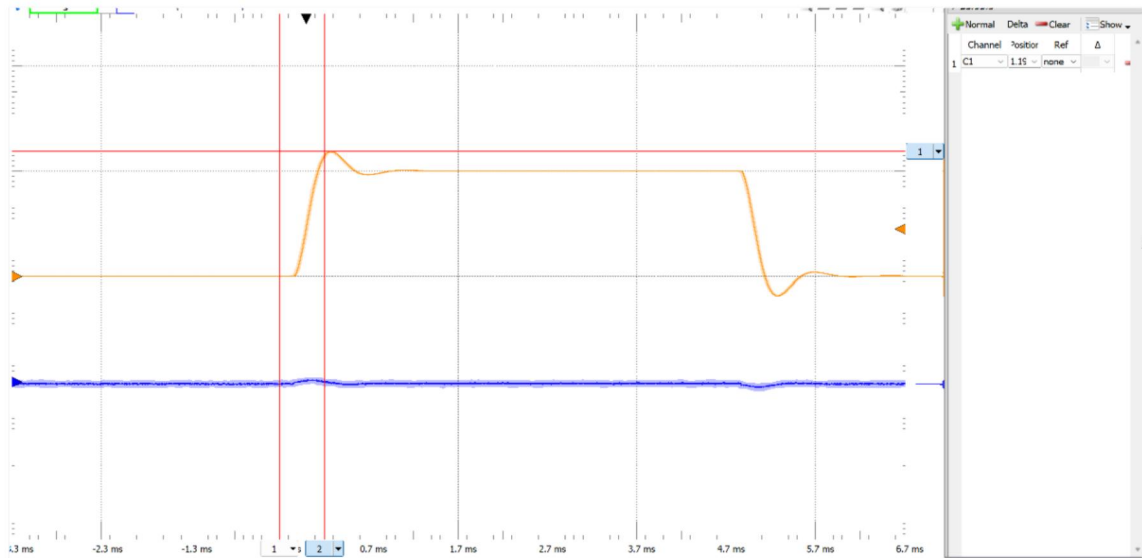

st

Overshoot Measurement:

Experimental Value of Resistor used ( $\Omega$ )	Overshoot measured (%)
1000	.19%

Damped Frequency Measurement:

Experimental Damped Frequency (Hz)	Theoretical Damped Frequency (Hz)
$1/(2(669\mu\text{s} - 225\mu\text{s})) = 1205\text{ Hz}$	1145 Hz

### 2.3 Damped Frequency measurement 3 / 3

✓ - 0 pts *Correct*

- 3 pts *Incorrect*

- 2 pts *Slightly incorrect*

- 2 pts *Partially incorrect*



- Derive theoretical equation for output voltage  $v_o(t)$  (including  $R_L$ ) across capacitor for new design.

$$V_o'' + 7766 V_o' + (6.667 \times 10^7) V_o = 0$$

$$\therefore V_o = C_1 e^{-3883t} \cos(7182t) + C_2 e^{-3883t} \sin(7182t) + 1$$

$$V_o(0^+) = V_o(0^-) = 0$$

$$V_o'(0^+) = V_o'(0^-) = \frac{1(0^-)}{C} = 0$$

$$C_1 = -1$$

$$C_2 = -.5377$$

$$V_o = -e^{-3883t} \cos(7182t) - .5377 e^{-3883t} \sin(7182t) + 1$$

#### Discussion

- How did the experimental damped frequency compare with the theoretical values?

The experimental damped frequency is within 5% of the  
 <Answer in 2-3 lines.>

theoretical,  $\therefore$  It matches the theoretical value correctly.

- What happens if you try to make the overshoot smaller?

To do this we would need to increase the resistance.

<Answer in 1-2 lines.>

If we keep doing this, it will become critically damped

## 2.4 Derivation of Output Voltage 8 / 8

✓ - **0 pts** *Correct*

- **4 pts** Mistake

- **2 pts** Small mistake

- **4 pts** Partial

- **8 pts** Missing

- **4 pts** Derivation Missing

- Derive theoretical equation for output voltage  $v_o(t)$  (including  $R_L$ ) across capacitor for new design.

$$V_o'' + 7766 V_o' + (6.667 \times 10^7) V_o = 0$$

$$\therefore V_o = C_1 e^{-3883t} \cos(7182t) + C_2 e^{-3883t} \sin(7182t) + 1$$

$$V_o(0^+) = V_o(0^-) = 0$$

$$V_o'(0^+) = V_o'(0^-) = \frac{1(0^-)}{C} = 0$$

$$C_1 = -1$$

$$C_2 = -.5377$$

$$V_o = -e^{-3883t} \cos(7182t) - .5377 e^{-3883t} \sin(7182t) + 1$$

#### Discussion

- How did the experimental damped frequency compare with the theoretical values?

The experimental damped frequency is within 5% of the  
 <Answer in 2-3 lines.>

theoretical,  $\therefore$  It matches the theoretical value correctly.

- What happens if you try to make the overshoot smaller?

To do this we would need to increase the resistance.

<Answer in 1-2 lines.>

If we keep doing this, it will become critically damped

## 2.5 Discussion 1 3 / 3

✓ - **0 pts** *Correct*

- **3 pts** *Incorrect*

- **1 pts** *Partially correct*

- Derive theoretical equation for output voltage  $v_o(t)$  (including  $R_L$ ) across capacitor for new design.

$$V_o'' + 7766 V_o' + (6.667 \times 10^7) V_o = 0$$

$$\therefore V_o = C_1 e^{-3883t} \cos(7182t) + C_2 e^{-3883t} \sin(7182t) + 1$$

$$V_o(0^+) = V_o(0^-) = 0$$

$$V_o'(0^+) = V_o'(0^-) = \frac{1(0^-)}{C} = 0$$

$$C_1 = -1$$

$$C_2 = -.5377$$

$$V_o = -e^{-3883t} \cos(7182t) - .5377 e^{-3883t} \sin(7182t) + 1$$

#### Discussion

- How did the experimental damped frequency compare with the theoretical values?

The experimental damped frequency is within 5% of the  
<Answer in 2-3 lines.>

theoretical,  $\therefore$  It matches the theoretical value correctly.

- What happens if you try to make the overshoot smaller?

To do this we would need to increase the resistance.

<Answer in 1-2 lines.>

If we keep doing this, it will become critically damped


## 2.6 Discussion 2 3 / 3

✓ - **0 pts** *Correct*

- **3 pts** *Incorrect*

- **1 pts** *Partial explanation*

### 3. Critically Damped RLC Circuit

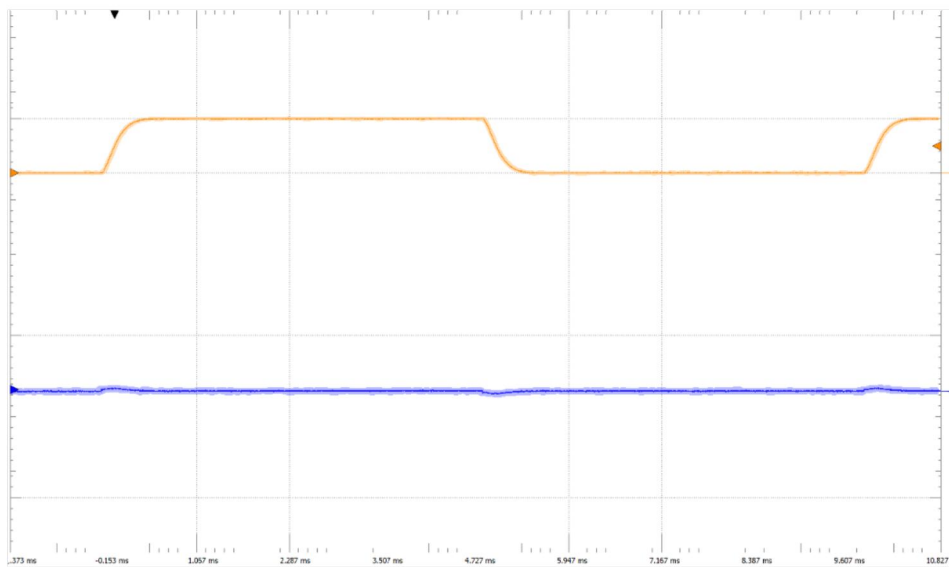

apacitor.>  
critical damping

- What is the potentiometer resistance for critical damping?

$$R_{\text{potentiometer}} = 2.246 \text{ k}\Omega$$

- Derive theoretical resistance needed for critical damping. (Include the effect of  $R_L$ )

$$\gamma = 1 = \frac{R + R_L}{2} \sqrt{\frac{C}{L}}$$

$$\therefore R = 2\sqrt{\frac{L}{C}} - R_L = 2279 \Omega$$

### 3.1 Waveforms Image 6 / 6

✓ + 6 pts Correct

+ 5 pts Slightly Incorrect.


+ 4 pts Slightly Incorrect

+ 3 pts Incorrect

+ 0 pts Missing



### 3. Critically Damped RLC Circuit

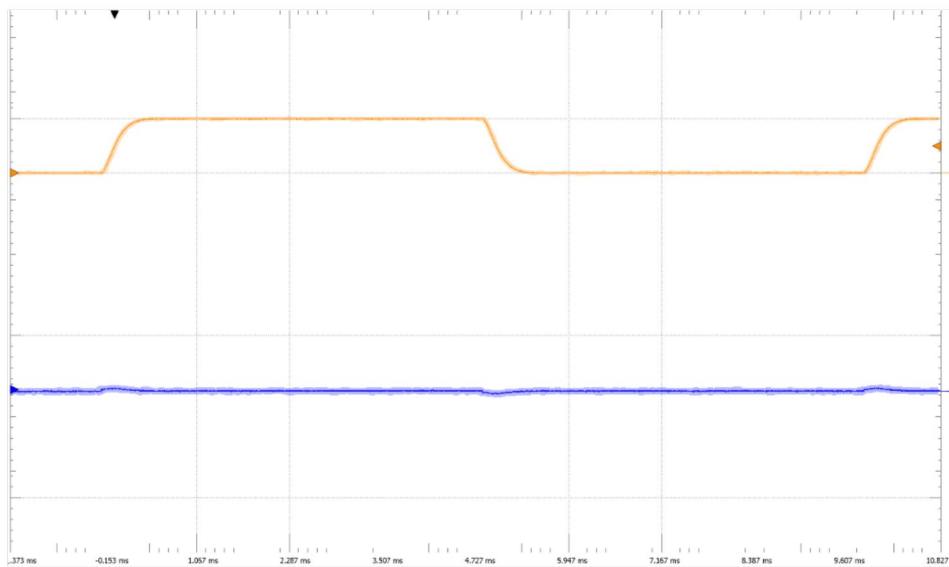

apacitor.>  
critical damping

- What is the potentiometer resistance for critical damping?

$$R_{\text{potentiometer}} = 2.246 \text{ k}\Omega$$

- Derive theoretical resistance needed for critical damping. (Include the effect of  $R_L$ )

$$\zeta = 1 = \frac{R + R_L}{2} \sqrt{\frac{C}{L}}$$

$$\therefore R = 2\sqrt{\frac{L}{C}} - R_L = 2279 \Omega$$

### 3.2 Potentiometer resistance 3 / 3


✓ + 3 pts *Correct*

+ 1 pts *Incorrect*

+ 0 pts *Missing*

+ 2 pts *Slightly incorrect*

### 3. Critically Damped RLC Circuit

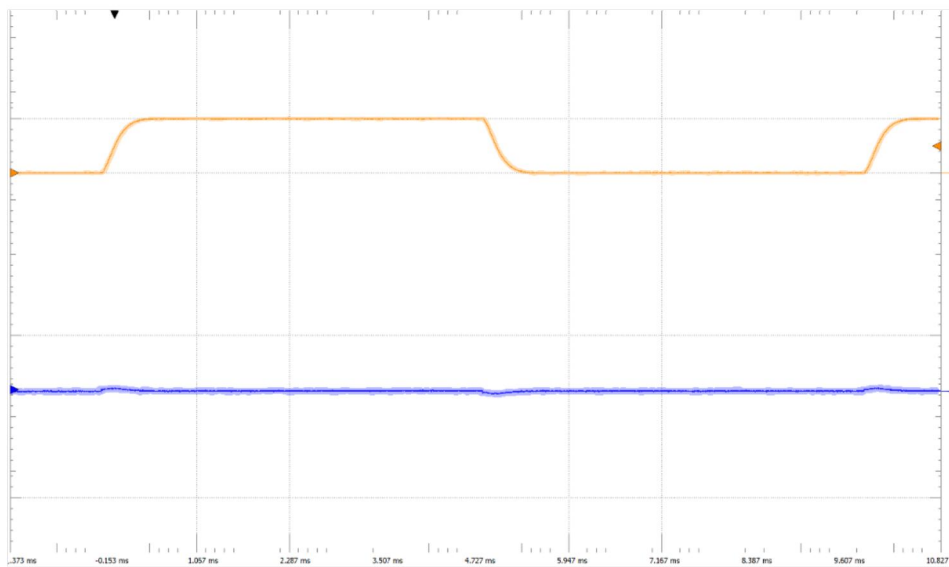

apacitor.>  
critical damping

- What is the potentiometer resistance for critical damping?

$$R_{\text{potentiometer}} = 2.246 \text{ k}\Omega$$

- Derive theoretical resistance needed for critical damping. (Include the effect of  $R_L$ )

$$\gamma = 1 = \frac{R + R_L}{2} \sqrt{\frac{C}{L}}$$

$$\therefore R = 2\sqrt{\frac{L}{C}} - R_L = 2279 \Omega$$

### 3.3 Derivation of Critical Damping Resistance 4 / 4

✓ + 4 pts Correct

+ 3 pts Slightly Incorrect

+ 2 pts Incorrect

+ 0 pts Missing

## Discussion

- How close was the value of resistance you ended up with when using the potentiometer to obtain a critically damped response, to the theoretical value you have derived? Consider the effects of inductor resistance as well.

It was within 5% of the theoretically derived value.

<Answer in 1-3 lines. >

The error may be a result of tuning the pot.

- What did you observe in the output waveform as resistance varied?

<Answer in 1-2 lines. >

The Resistance controls the behavior of dampening of the circuit

Under damped	Low R
Critically Damped	Mid R
Overdamped	High R.

### 3.4 Discussion 1 3 / 3

✓ + **3 pts** *Correct*

+ **2 pts** Slightly incorrect

+ **0 pts** Missing

## Discussion

- How close was the value of resistance you ended up with when using the potentiometer to obtain a critically damped response, to the theoretical value you have derived? Consider the effects of inductor resistance as well.

It was within 5% of the theoretically derived value.

<Answer in 1-3 lines. >

The error may be a result of tuning the pot.

- What did you observe in the output waveform as resistance varied?

<Answer in 1-2 lines. >

The Resistance controls the behavior of dampening of the circuit

Under damped	Low R
Critically Damped	Mid R
Overdamped	High R.

### 3.5 Discussion 2 3 / 3

✓ + 3 pts *Correct*

+ 2 pts Slightly Incorrect/Incomplete.

+ 0 pts Missing



# **University of California, Los Angeles**

**School of Engineering and Applied Science**

**Department of Electrical and Computer  
Engineering**

**Name:** Sanjit Sarda

**UID:** 805964031

**Experiment 4: Transient Response of the 2<sup>nd</sup>-Order  
Circuits**

## **ECE11L Lab**

**Instructor: Sudhakar Pamarti**